

# Tutorial 4 (DEC)

Time limit: 20 min

1. a) Find the base (or radix ) of the number system for which the equation  $\frac{312}{20} = 13.1$  holds true.


b) If  $(1110212.20211)_3 = (X)_9$  then, find out X.

c)  $(235)_a = (565)_{10} = (1065)_b$  Choose the correct options for (a,b) values:

[A] (a,b)=(3,7) [B] (a,b)=(16,8)


[C] (a,b)=(7,3) [D] (a,b)=(8,16)

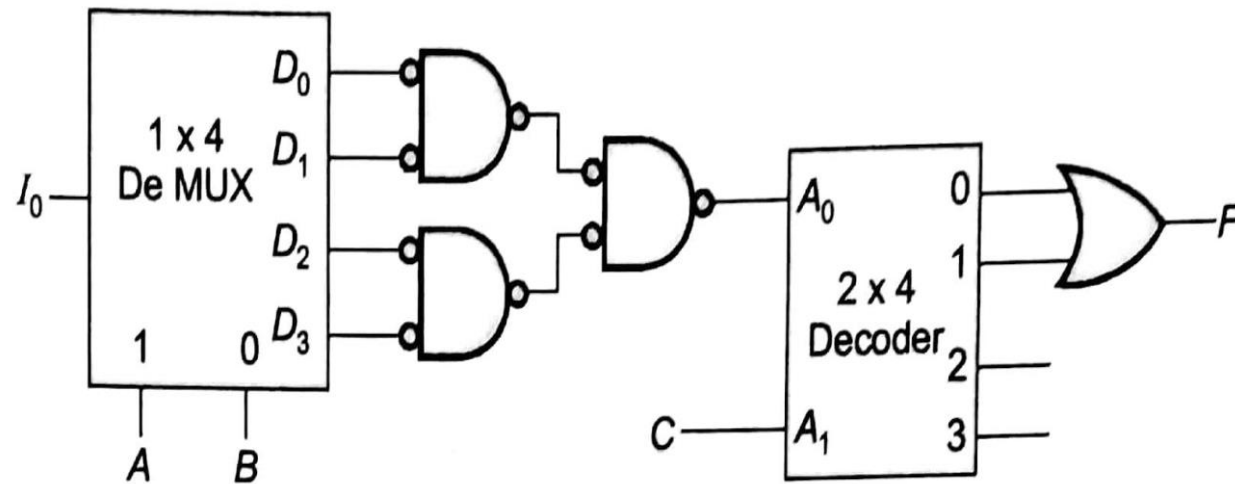2. Find out the minimized expression of F in the below diagram.



3. a) What is the decimal value representations of binary number 10001001 using *fixed(8,4)* and *fixed(8,2)* point representations?
- b) Write the precision and range of values (in decimal) that can be represented by *fixed(16,8)* point representation.
4. Implement a 4:2 priority encoder using only 2:1 MUX.
5. What should be the min-term expression at the output of the given circuit?

**Time limit: 25 min**

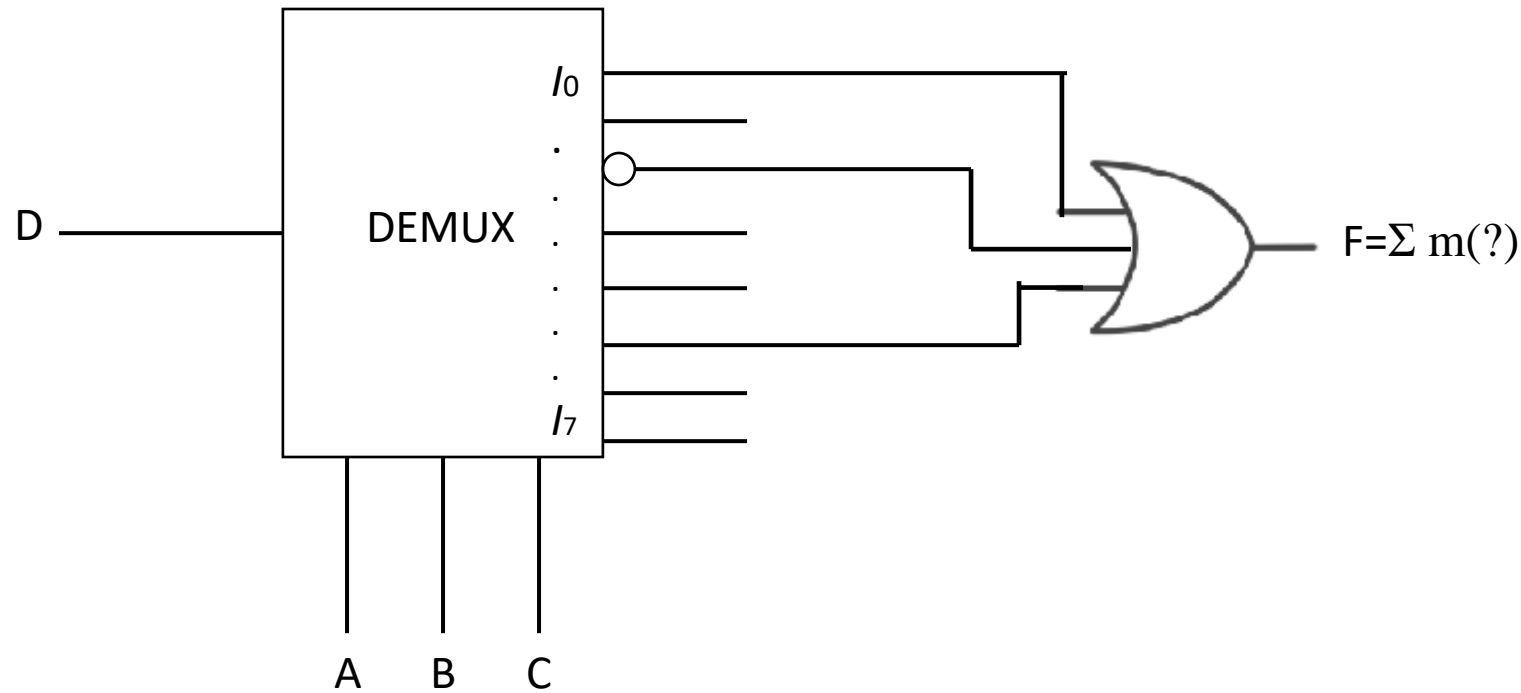

# Solutions

1. a) Find the base (or radix ) of the number system for which the equation  $\frac{312}{20} = 13.1$  holds true.

Q1a) Symbols used in this equation are 0,1,2,3 Hence base or radix can be 4 or higher

$$(312)_x = (20)_x (13.1)_x$$

$$3x^2 + 1x + 2x^0 = (2x+0) (x+3x^0+x^{-1})$$

$$3x^2+x+2 = (2x) \left( x + 3 + \frac{1}{x} \right)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$x(x - 5) = 0$$

$$x = 0 \text{ (or) } x = 5$$

But  $x$  must be greater than 3. So  $x = 5$

1b) If  $(1110212.20211)_3 = (X)_9$ , then, find out X.

1c)  $(235)_a = (565)_{10} = (1065)_b$  Choose the correct options for (a,b) values:

[A]  $(a,b) = (3,7)$  [B]  $(a,b) = (16,8)$  [C]  $(a,b) = (7,3)$  [D]  $(a,b) = (8,16)$

1b) For base 3, digits are 0, 1, 2, 10, 11, 12, 20, 21, ...

Q1b,c)

Base 3	Base 9
00	0
01	1
02	2
10	3
11	4
12	5
20	6
21	7
22	8

$\rightarrow (1110212.20211)_3$

$= (01\ 11\ 02\ 12.20\ 21\ 10)_3$

$= (1425.673)_9$

Alternative


$(1110212.20211)_3 \rightarrow (1076.7572 \dots)_{10}$

$\downarrow$   
 $(1425.673)_9$

1c) Given,  $(235)_a = (565)_{10} = (1065)_b$

$\hookrightarrow$  Since,  $235 < 565 \rightarrow a > 10$  only option [B] satisfies this condition  
 $1065 > 565 \rightarrow b < 10$

Q2)

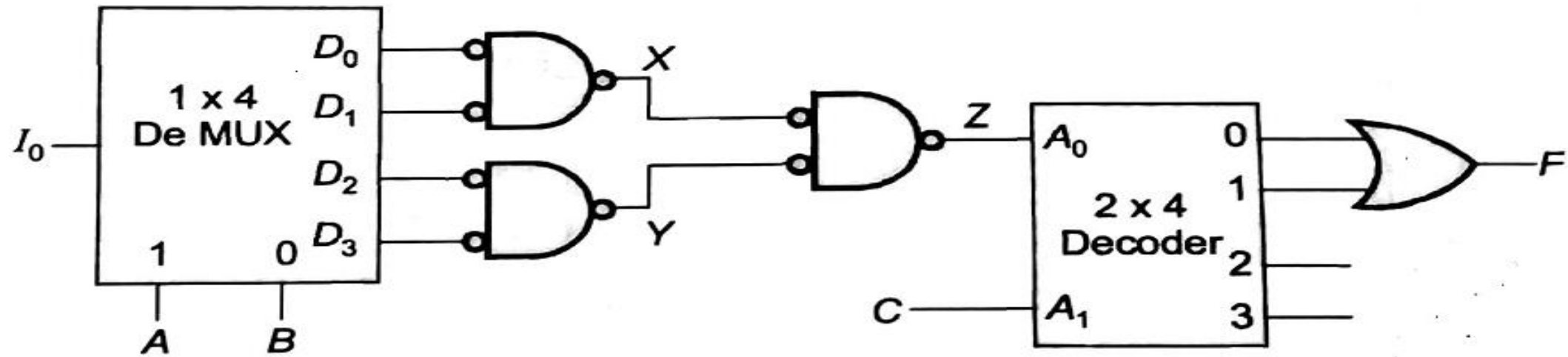

$$X = \overline{\overline{D_0} \overline{D_1}} I_0 = (D_0 + D_1) I_0 = (\overline{A} \overline{B} + \overline{A} B) I_0 = \overline{A} I_0$$

$$Y = \overline{\overline{D_2} \overline{D_3}} I_0 = (D_2 + D_3) I_0 = (A \overline{B} + A B) I_0 = A I_0$$

$$Z = (\overline{\overline{X}} \cdot \overline{\overline{Y}}) = X + Y = \overline{A} \cdot I_0 + A I_0 = I_0$$

$$F = (\overline{\overline{Z} \overline{C}} + \overline{Z \overline{C}}) = \overline{C} (\overline{I_0} + I_0) = \overline{C}$$

3. a) What is the decimal value representations of binary number 10001001 using *fixed(8,4)* and *fixed(8,2)* point representations?

b) Write the precision and range of values (in decimal) that can be represented by *fixed(16,8)* point representation.

Q3a)

$$\text{fixed}(8,4): 1000.1001 = (1 \times 2^3 + 1 \times 2^{-1} + 1 \times 2^{-4})_{10} = (8.5625)_{10}$$

$$\text{fixed}(8,2): 100010.01 = (1 \times 2^5 + 1 \times 2^1 + 1 \times 2^{-2})_{10} = (34.25)_{10}$$

Q3b)

$$\text{Precision} = 2^{-8} = 0.00390625$$

$$\begin{aligned} \text{Fixed}(16,8) \text{ representation range} &= (00000000.00000000 \text{ to } 11111111.11111111)_2 \\ &= (0 \text{ to } 255.99609375)_{10} \end{aligned}$$

$$\text{Or } (0 \text{ to } 2^8 - 2^{-8} = 255.99609375)_{10}$$

Q4) Implement a 4:2 priority encoder using only 2:1 MUX

## Concept of Priority Encoder

4x2 Priority encoder:

$D_3$	$D_2$	$D_1$	$D_0$	$Y_1$	$Y_0$
1	X	X	X	1	1
0	1	X	X	1	0
0	0	1	X	0	1
0	0	0	1	0	0

$$Y_1 = D_3 + \bar{D}_3 D_2$$


$$Y_0 = D_3 + \bar{D}_3 \bar{D}_2 D_1$$

$$A + A'B = A + B$$

$$C_1 = D_3 + D_2$$


$$C_0 = D_3 + D_2' D_1$$

( $D_1$  if not  $D_2$ , due to priority)

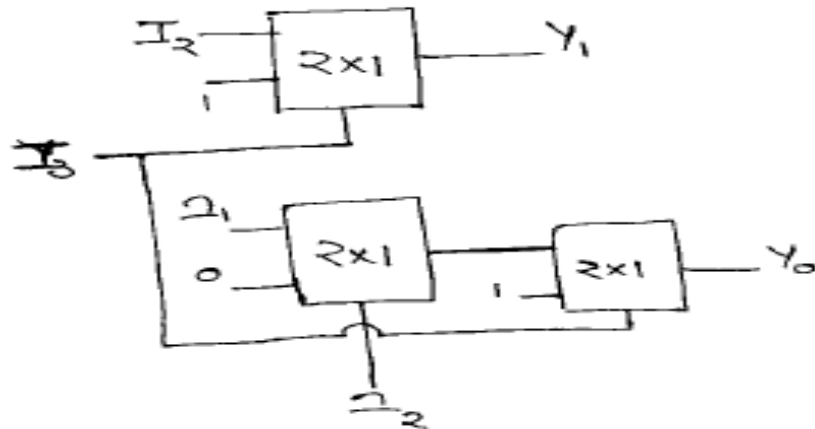

Using 2-to-1 MUX, the obtained function can be realized in the above fashion.

$D_3$	$D_2$	$D_1$	$D_0$	$C_1$	$C_0$
1	X	X	X	1	1
0	1	X	X	1	0
0	0	1	X	0	1
0	0	0	1	0	0

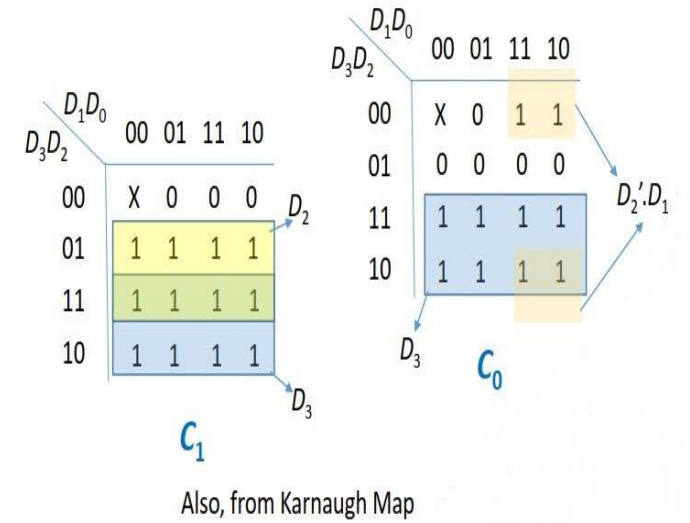

Q5) The output expression F is,

A	B	C	F
0	0	0	<b>D</b>
0	0	1	0
0	1	0	<b>D'</b>
0	1	1	0
1	0	0	0
1	0	1	<b>D</b>
1	1	0	0
1	1	1	0



A	B	C	D	F
0	0	0	0	0
<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
0	0	1	0	0
0	0	1	1	0
<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0



$$F = \Sigma m(1,4,11)$$

