


Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 2

Propagation Delay

 - Due to finite switching speed of transistors and circuit capacitances



t_{PHL} : Delay in changing output from H to L

t_{PLH} : Delay in changing output from L to H

Propagation delay, $t_{PD} = (t_{PHL} + t_{PLH})/2$

t_r : Rise time → 10% to 90% of max.

t_f : Fall time → 90% to 10% ...

Power dissipation

- **Static power dissipation**
 - when transistor is either ON or OFF
 - depends on current drawn in each case
 - power dissipation, P_D is average of these two
 - significant in switching of Bipolar Junction Transistor
- **Dynamic power dissipation**
 - when transistor switches
 - depends on switching speed
 - significant in switching of CMOS Transistor



Figure of Merit,

$$F = P_D \times t_{PD}$$

The lower the F, the better.

RTL NOR Gate



RTL: Resistance Transistor Logic

  

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

- For 3 input NOR gate, another input would come in parallel with A and B .
- More no. of inputs increases delay
- *Fan-in*: Max. number of inputs a gate can handle

RTL NAND Gate

  

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


It will be shown that any other logic gates can be obtained using only NAND gate or NOR gate.

From Archive (Motorola datasheet)

DUAL 3-INPUT GATES

PLASTIC MRTL MC700P/800P series

MC715P • MC815P

 

Two 3-input NOR gates

$R1 = 450\Omega$, $R2 = 640\Omega$


$P_D = 55 \text{ mW}$ (input H), 15 mW (input L)

$t_{PD} = 12 \text{ ns}$


The MRTL family of resistor-transistor logic offers the industry's broadest line of digital circuits. Devices in this section are medium-power circuits; low-power mW MRTL circuits are also available.

DTL NAND Gate

DTL: Diode Transistor Logic


 


 - D_1, D_2, R_1, V_{CC} : AND logic at P.
- D_3 and D_4 are level shifters ($V_p = 3 \times 0.7V$ turns ON transistor.)
- R_3 provides discharge path of stored charge at BE junction that reduces t_{PLH} .
- Any of A or B low (0.2 V), $V_p = 0.9$ V, insufficient to turn ON the transistor.



TTL: Transistor Transistor Logic



NAND Gate

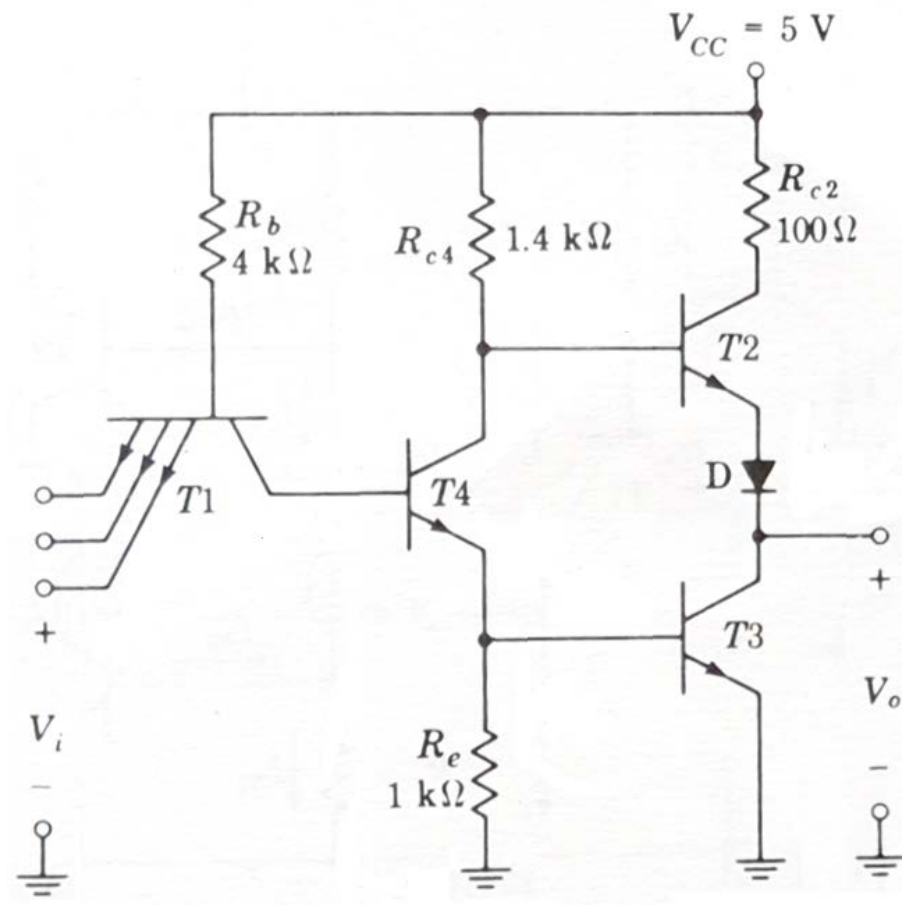 

- Totem pole output reduces output resistance when at H.
- R_3 cannot be made zero.
- D_1 to avoid indeterminate output.

TTL: Transistor Transistor Logic

NAND Gate

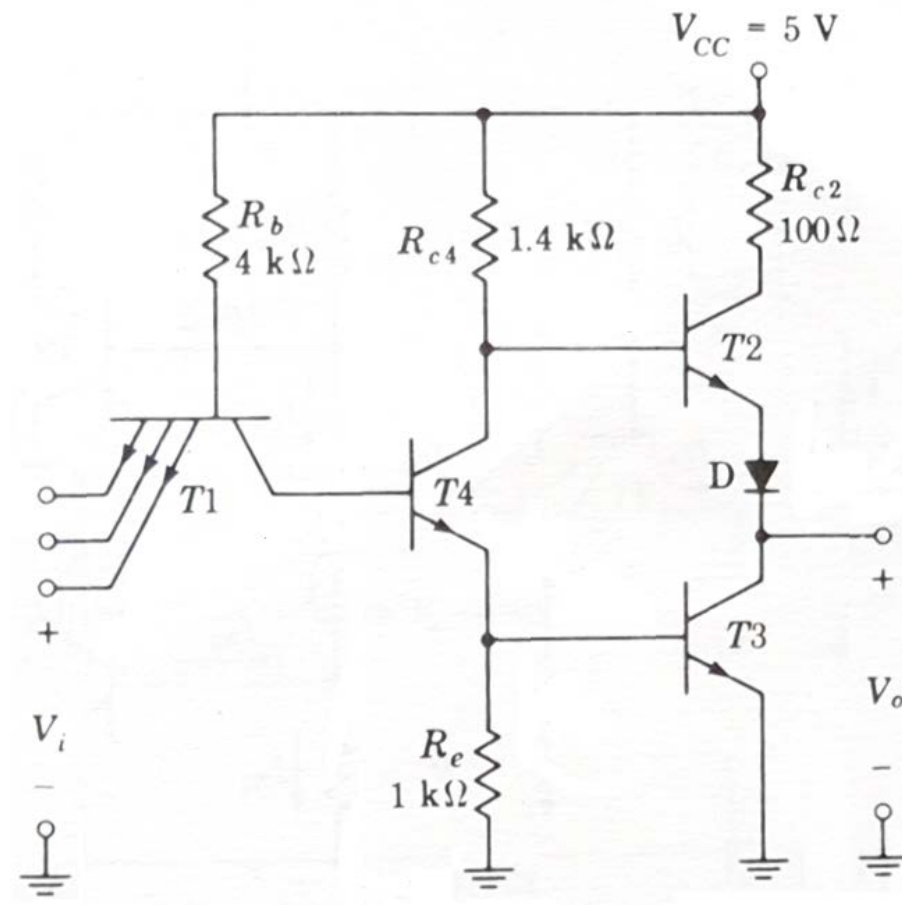 

- Totem pole output reduces output resistance when at H.
- R_{c2} cannot be made zero.
- D_1 to avoid indeterminate output.

References:

- ❑ Grinich, V.H., and H.G. Jackson, Introduction to Integrated Circuits, McGraw-Hill
- ❑ Herbert Taub, and Donald Schilling, Digital Integrated Electronics, McGraw Hill
- ❑ Motorola Datasheet accessed on Oct. 08, 2018 from
http://willowdaledesign.com/17_MRTL_700P_800P_text.pdf