
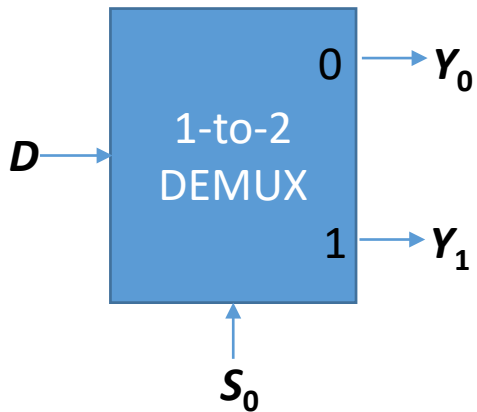
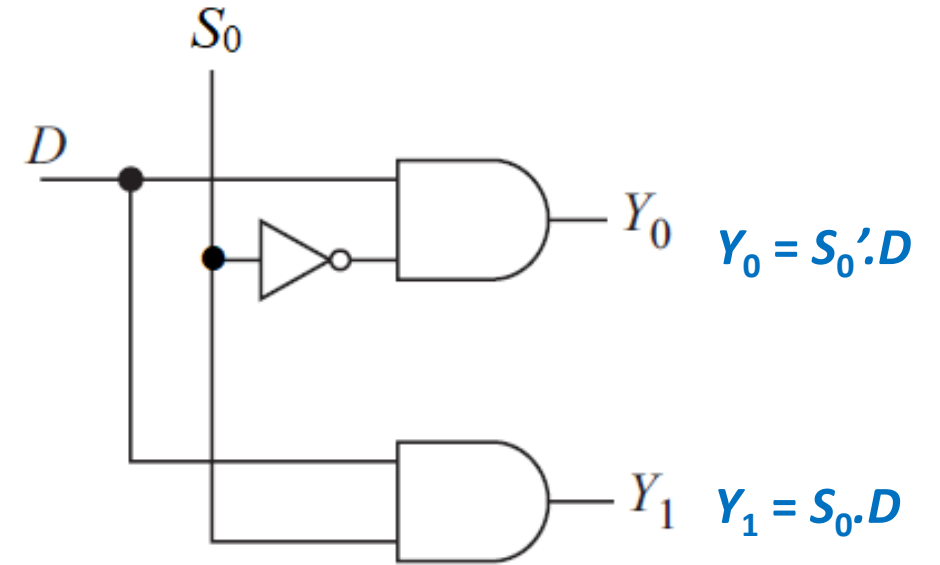


# **Digital Electronic Circuits**

## **Section 1 (EE, IE)**

### **Lecture 12**


# Demultiplexer

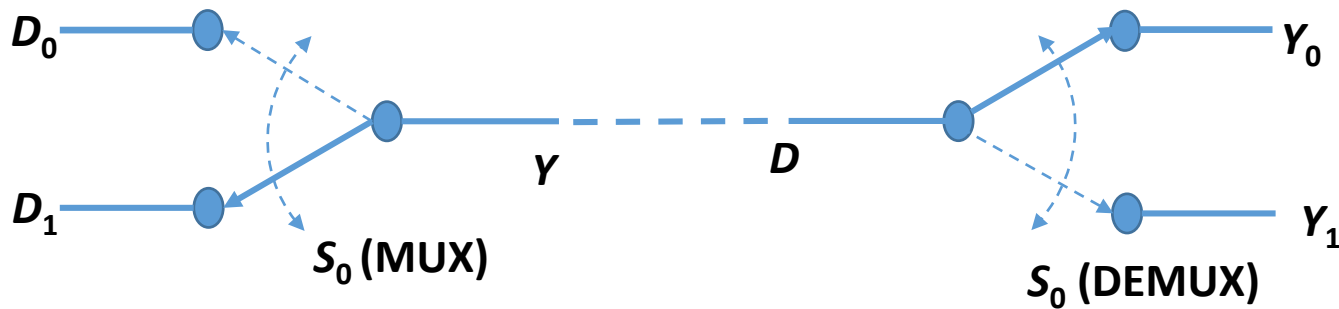

$S_0$	$Y_0$	$Y_1$
0	$D$	0
1	0	$D$

A demultiplexer steers the input to one of the many outputs based on control input(s).

# 1-to-4 Demultiplexer

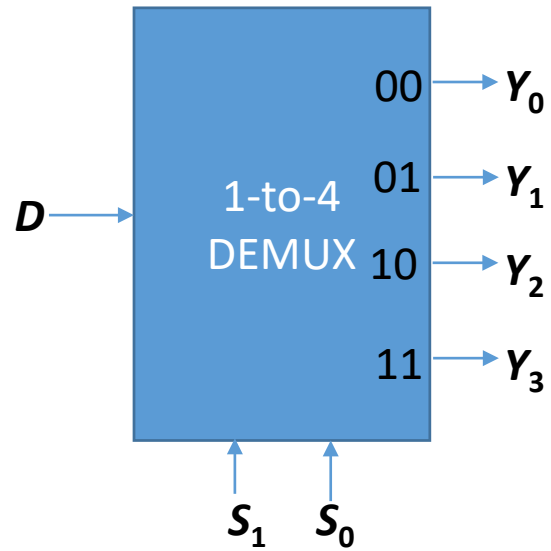

$$Y_0 = S_1' S_0' . D$$


$$Y_1 = S_1' S_0 . D$$

$$Y_2 = S_1 S_0' . D$$

$$Y_3 = S_1 S_0 . D$$

$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	<b><math>D</math></b>	0	0	0
0	1	0	<b><math>D</math></b>	0	0
1	0	0	0	<b><math>D</math></b>	0
1	1	0	0	0	<b><math>D</math></b>

# IC 74155

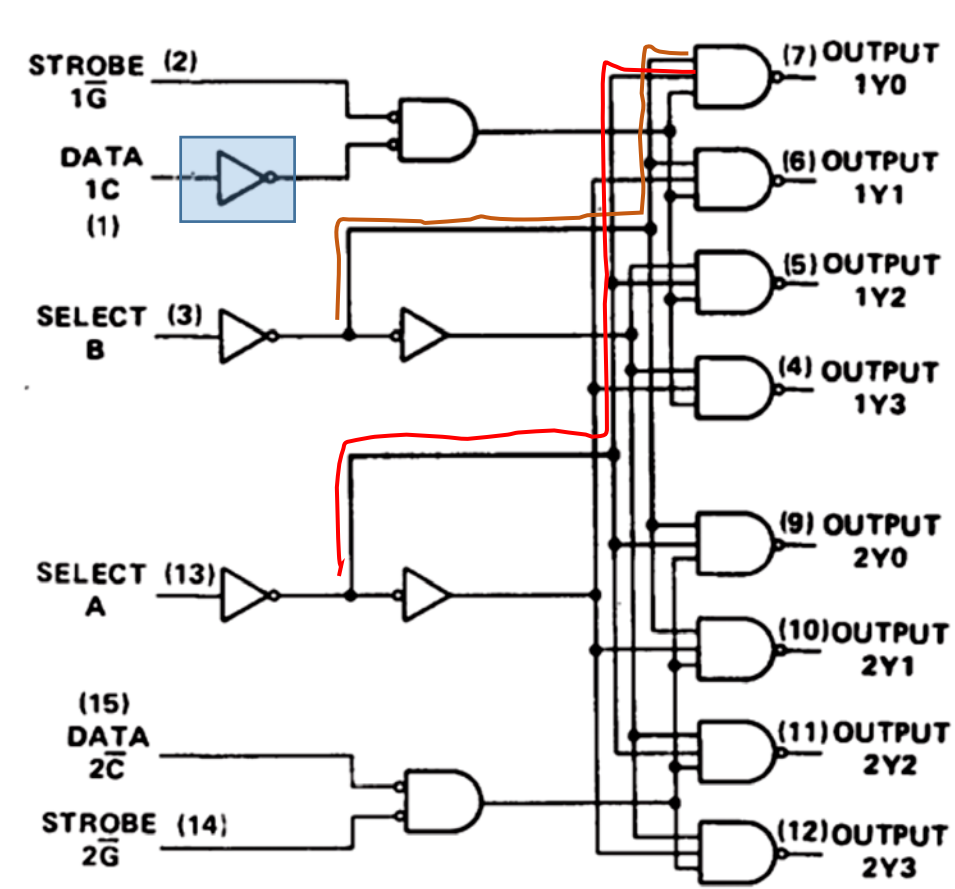

B	A	G <sub>1</sub>	C <sub>1</sub>	1Y <sub>0</sub>	1Y <sub>1</sub>	1Y <sub>2</sub>	1Y <sub>3</sub>
X	X	H	X	H	H	H	H
X	X	X	L	H	H	H	H
L	L	L	H	L	H	H	H
L	H	L	H	H	L	H	H
H	L	L	H	H	H	L	H
H	H	L	H	H	H	H	L

B	A	G <sub>2</sub>	C <sub>2</sub>	2Y <sub>0</sub>	2Y <sub>1</sub>	2Y <sub>2</sub>	2Y <sub>3</sub>
L	L	L	L	L	H	H	H
.....							

IC 74155: Dual 1-to-4 DEMUX

$1Y_0 = (B'A'.G_1'.1C)'$

$1Y_1 = (B'A.G_1'.1C)'$


.....

$2Y_0 = (B'A'.G_2'.2C')$

$2Y_1 = (B'A.G_2'.2C')$

.....

# 1-to-16 Demultiplexer

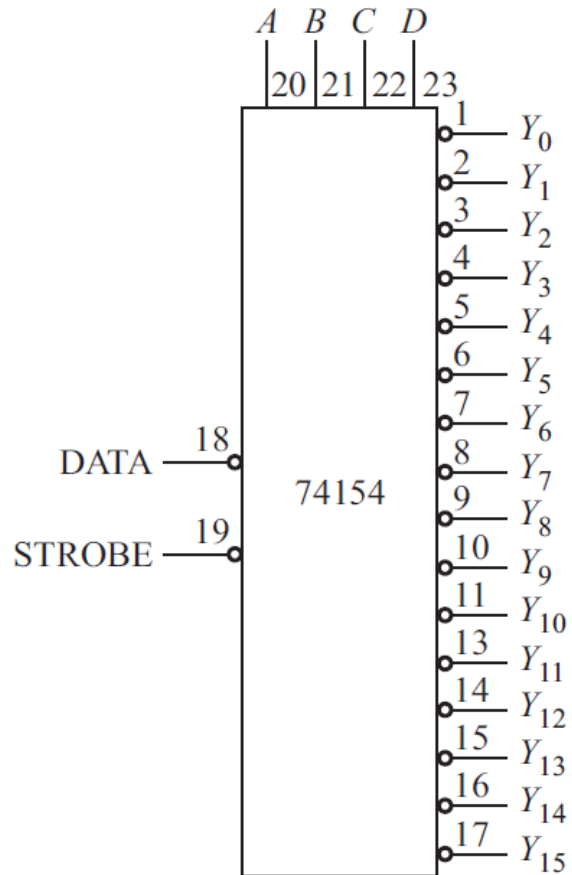

Strobe	Data	A	B	C	D	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	·	Y <sub>14</sub>	Y <sub>15</sub>
L	L	L	L	L	L	L	H	H	·	H	H
L	L	L	L	L	H	H	L	H	·	H	H
L	L	L	L	H	L	H	H	L	·	H	H
L	L	L	L	H	H	H	H	H	·	H	H
L	L	L	H	L	L	H	H	H	·	H	H
L	L	L	H	L	H	H	H	H	·	H	H
L	L	L	H	H	L	H	H	H	·	H	H
L	L	L	H	H	H	H	H	H	·	H	H
L	L	H	L	L	L	H	H	H	·	H	H
L	L	H	L	L	H	H	H	H	·	H	H
L	L	H	L	H	L	H	H	H	·	H	H
L	L	H	L	H	H	H	H	H	·	H	H
L	L	H	H	L	L	H	H	H	·	H	H
L	L	H	H	L	H	H	H	H	·	H	H
L	L	H	H	H	L	H	H	H	·	L	H
L	L	H	H	H	H	H	H	H	·	H	L
L	H	X	X	X	X	H	H	H	·	H	H
H	L	X	X	X	X	H	H	H	·	H	H
H	H	X	X	X	X	H	H	H	·	H	H

## IC 74154: 1-to-16 DEMUX



$$Y_0 = (A'B'C'D'.DATA'.STROBE')'$$

$$Y_1 = (A'B'C'D.DATA'.STROBE')'$$


$$Y_{15} = (ABCD.DATA'.STROBE')'$$

If STROBE = 0 and A = 0,  
select inputs *BCD* steers  
*DATA* to one of *Y*<sub>0</sub> ... *Y*<sub>7</sub>  
outputs: **1-to-8 DEMUX.**

# Higher order DEMUX from lower order

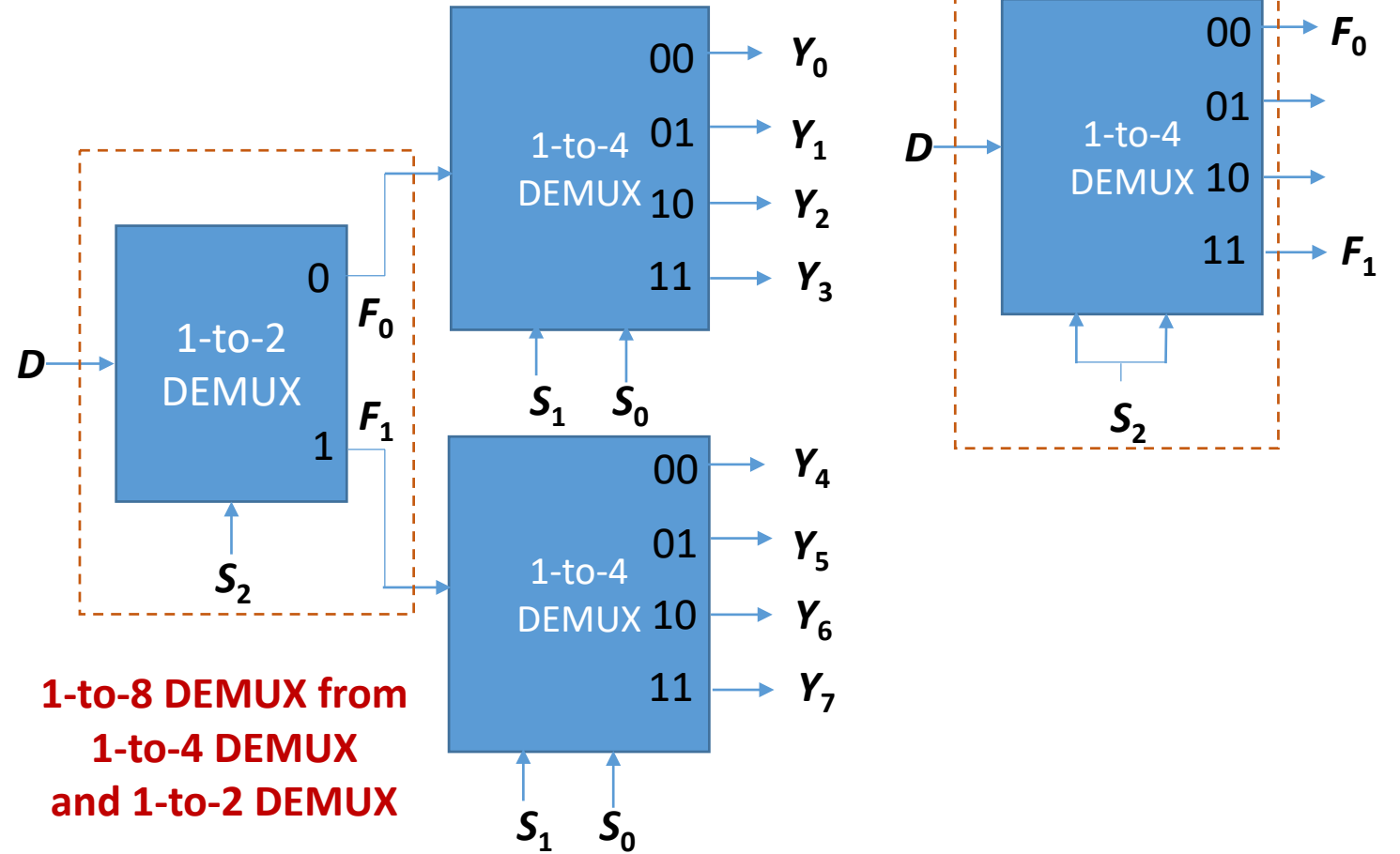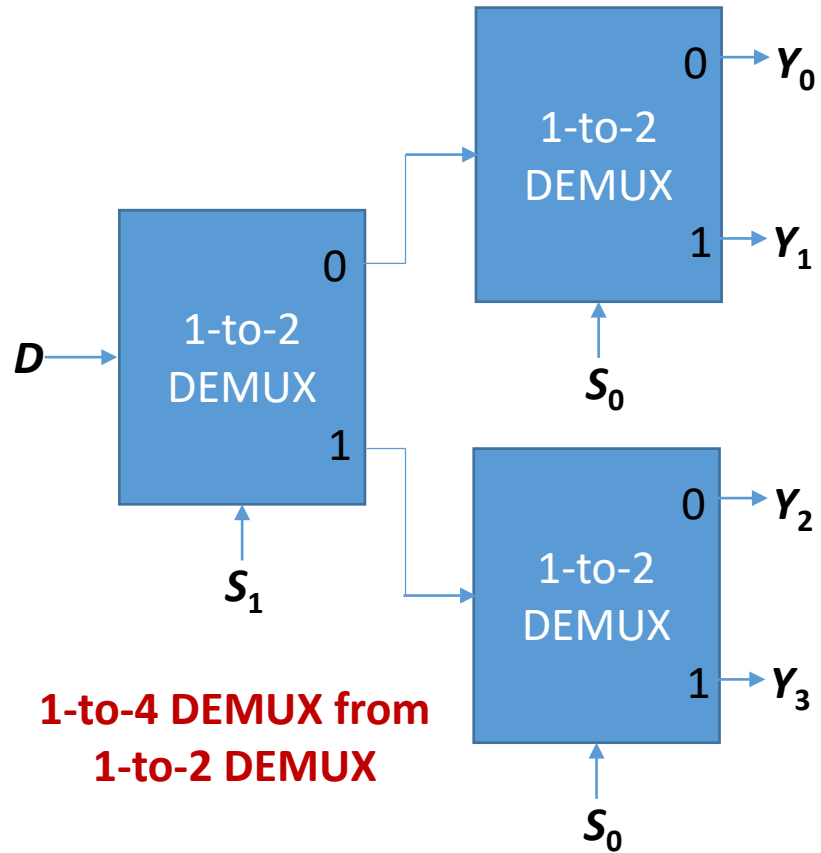

# Higher order DEMUX using Strobe

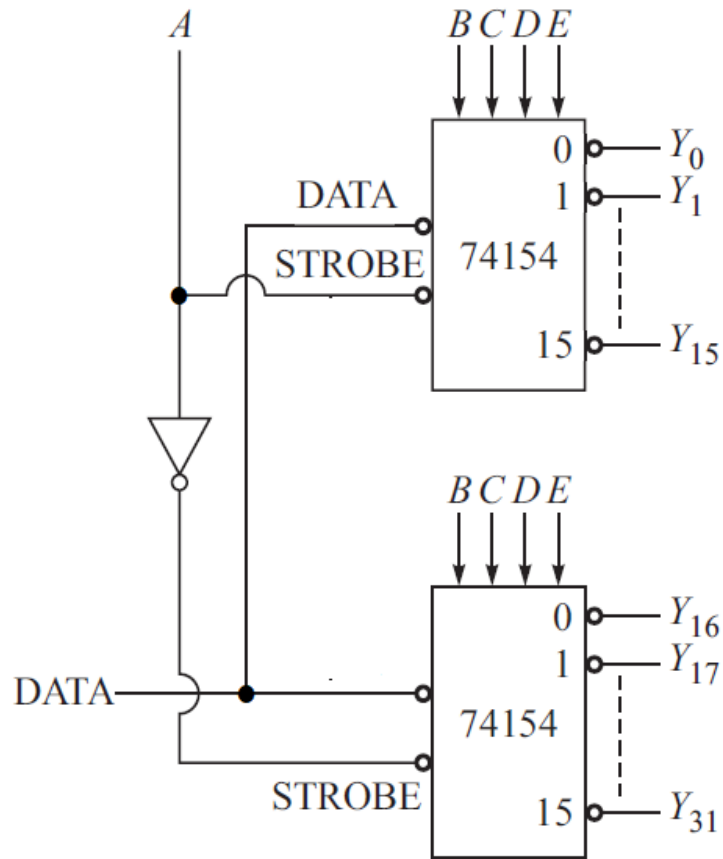


$$Y_0 = (B'C'D'E'.DATA'.A)'$$

$$Y_1 = (B'C'D'E'.DATA'.A)'$$

$$Y_{16} = (B'C'D'E'.DATA'.A)'$$

$$Y_{31} = (BCDE.DATA'.A)'$$

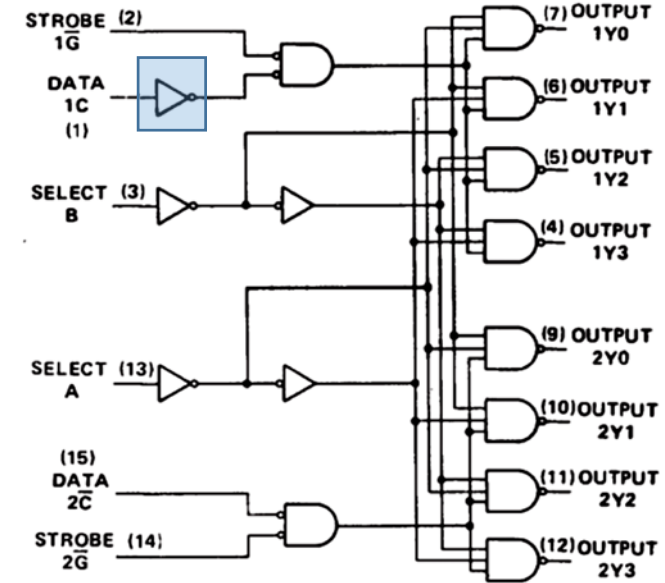


**IC 74155:** 1-to-8  
from dual 1-to-4  
Select = 1C = 2C'  
Data = 1G = 2G

# Decoder




A decoder decodes input bit pattern by appropriate logic and activates the output when specific combination is present.

To decode  $AB = 01$

(active HIGH)

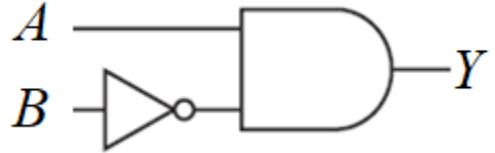

To decode  $AB = 11$

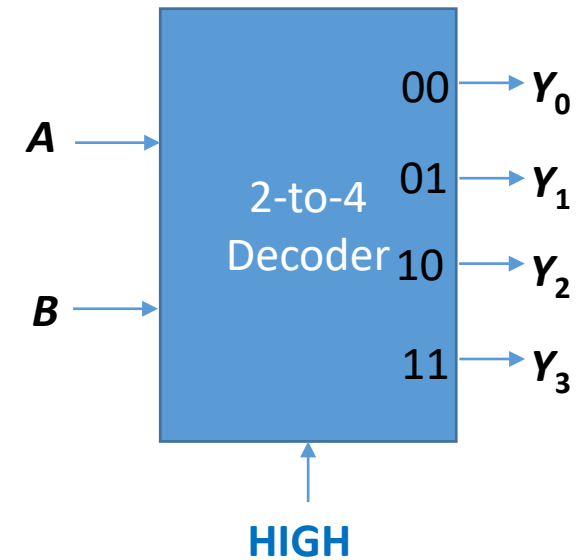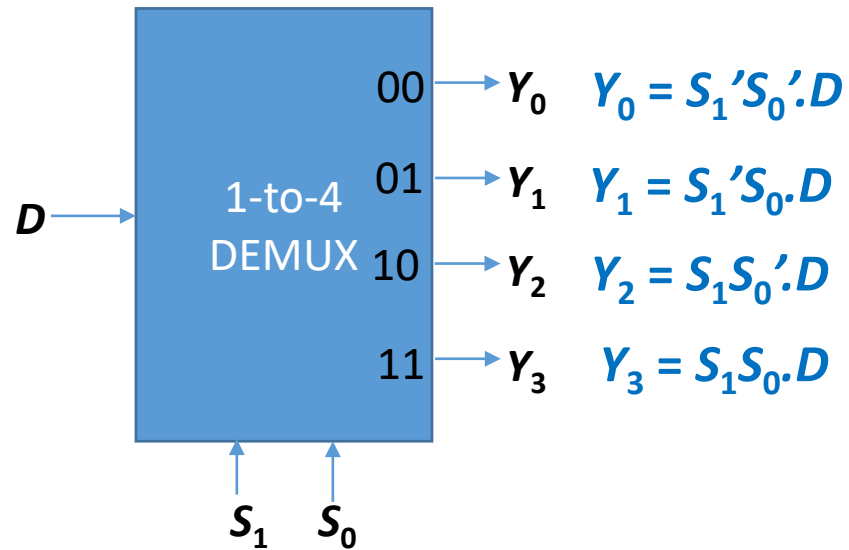
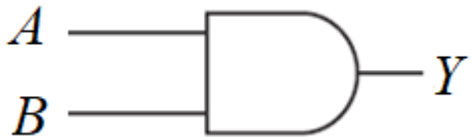




# IC 74154 as Decoder


IC 74154 as  
4-to-16 Decoder

Output  
Active LOW

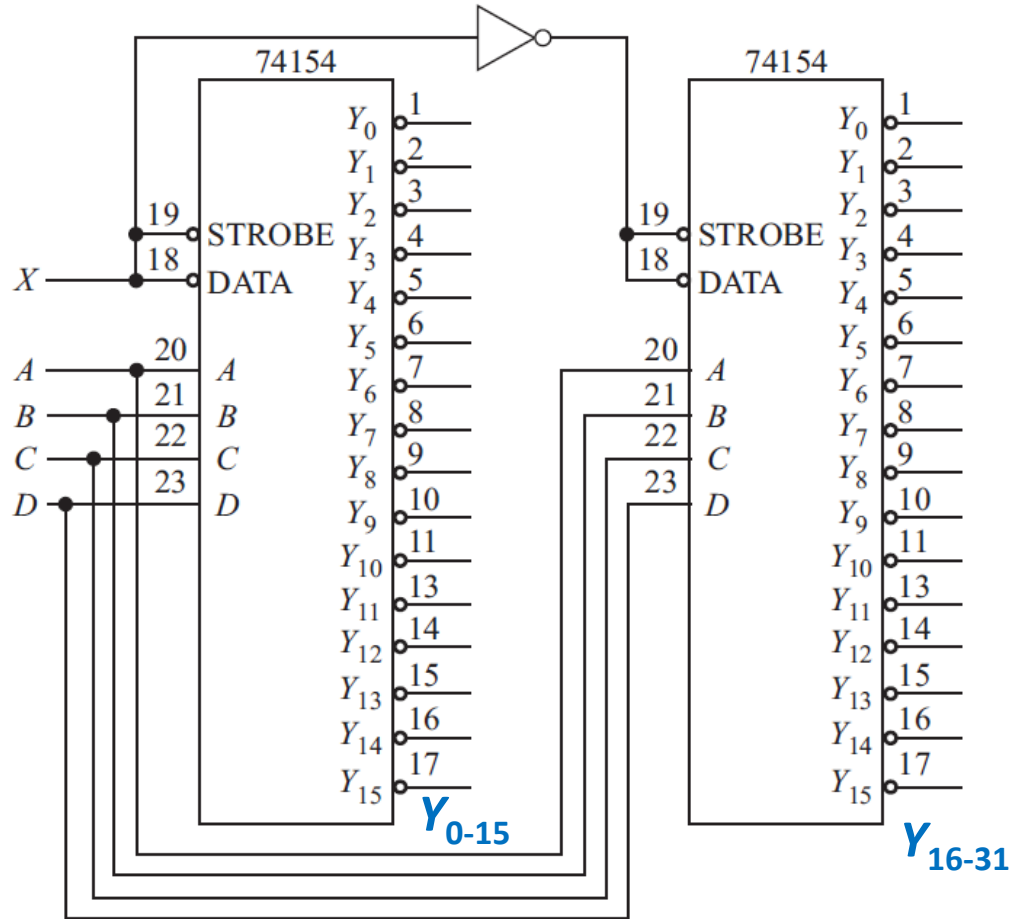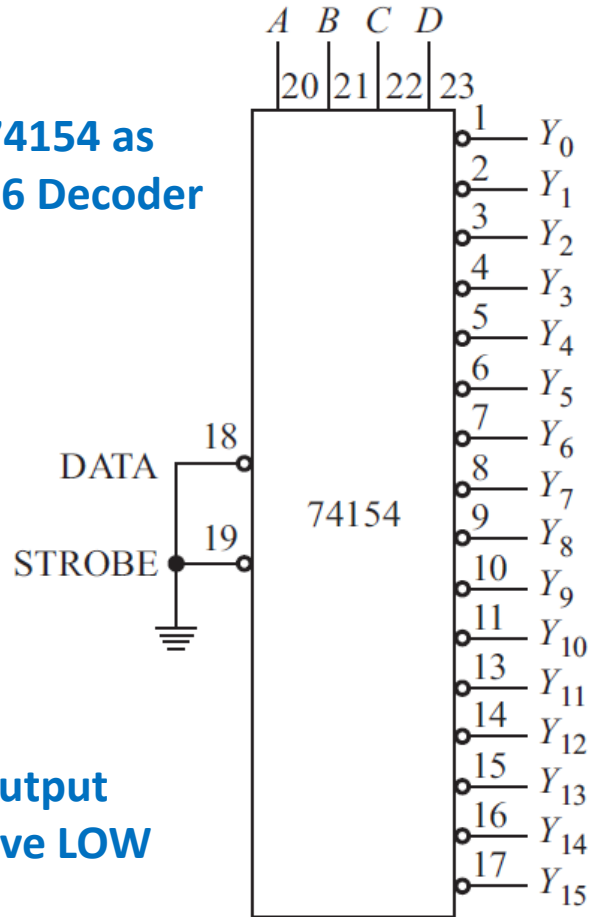

Chip expansion /  
Higher order from  
lower order:  
Similar to DEMUX

# Decoder for Multiple Output

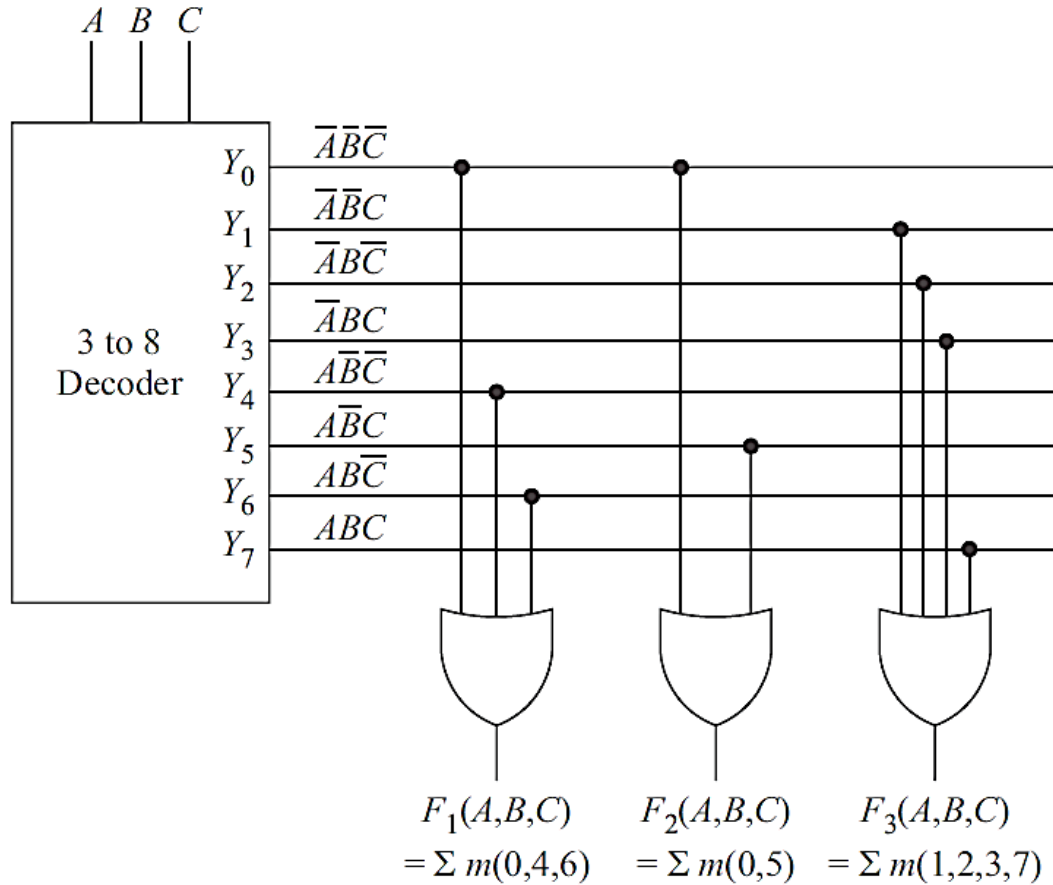

- Decoder generates all the minterms.
- OR gate sums up minterms defining a function.

## References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ Technical documents from <http://www.ti.com> accessed on Oct. 08, 2018