 


Digital Electronic Circuits


Section 1 (EE, IE)

Lecture 10

Static 0 Hazard




 In Static 0 Hazard, output should remain static at 0 according to Boolean Logic but glitch occurs under certain input condition.



τ_1 = NOT gate delay

τ_2 = AND gate delay

 

$$Y = (A + C).(A' + B)$$

$B = 0, C = 0$

$A : 0 \rightarrow 1$

Glitch occurs

Detecting Static 0 Hazard

- Two logically adjacent cells with output 0 in K-Map not covered by a common sum term.
- Boolean expression $(A.A')$ for certain condition.

		BC			
		00	01	11	10
A	0	0	1	0	0
	1	0	1	1	1

$$Y = (A + B').(B + C)$$

Glitch, $ABC : 000 \rightarrow 010$

Static 0 Hazard

		BC			
		00	01	11	10
A	0	0	1	0	1
	1	0	1	0	1

$$Y = (B + C).(B' + C')$$

No Hazard for one variable changing

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	1	1
	11	1	0	1	1
	10	1	0	0	0

$$Y = (A + C).(C + D').(B + C')$$

Glitch: Static 0 Hazard

$ABCD : 0001 \rightarrow 0011$

$1001 \rightarrow 1011$

$0000 \rightarrow 0010$


Static 0 Hazard and its Cover

A \ BC	00	01	11	10
	0	1	1	0
0	0	1	1	0
1	0	0	1	1

$$Y = (A + C).(A' + B).(B + C)$$

$(B + C) = 0$ for $B = 0, C = 0$

 This OR gate output when fed to AND gate, suppresses glitch.




Hazard-free circuit

AB \ CD	00	01	11	10
	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	1	0	1	1
10	1	0	0	0

$$Y = (A + C).(C + D').(B + C') \\ .(B + D').(A + B)$$

Hazard-free by covering logically adjacent 0s with common sum term

Hazard in NAND-NAND, NOR-NOR Circuit

 


$$Y = A'.C + A.B$$

$$B = 1, C = 1$$

$$A : 1 \rightarrow 0$$

Glitch occurs

 Cover: $(B.C)'$ as
3rd input to
output NAND



$$Y = (A + C).(A' + B)$$

$$B = 0, C = 0$$

$$A : 0 \rightarrow 1$$


Glitch occurs

Cover: $(B + C)'$
as 3rd input to
output NOR



Static 1 and Static 0 Hazards can also be avoided by adding delay (controlled) in the transition path.

Dynamic Hazard

 - Potential for multiple transitions before settling to final value while Boolean logic asks for only one transition.
- One input variable is to have three or more paths to the output.
- No. of levels three or more.
- For specific combination of input variables, Boolean expression reduces to $(A + A').A$ or $A + A'.A$



Dynamic Hazard: Example

 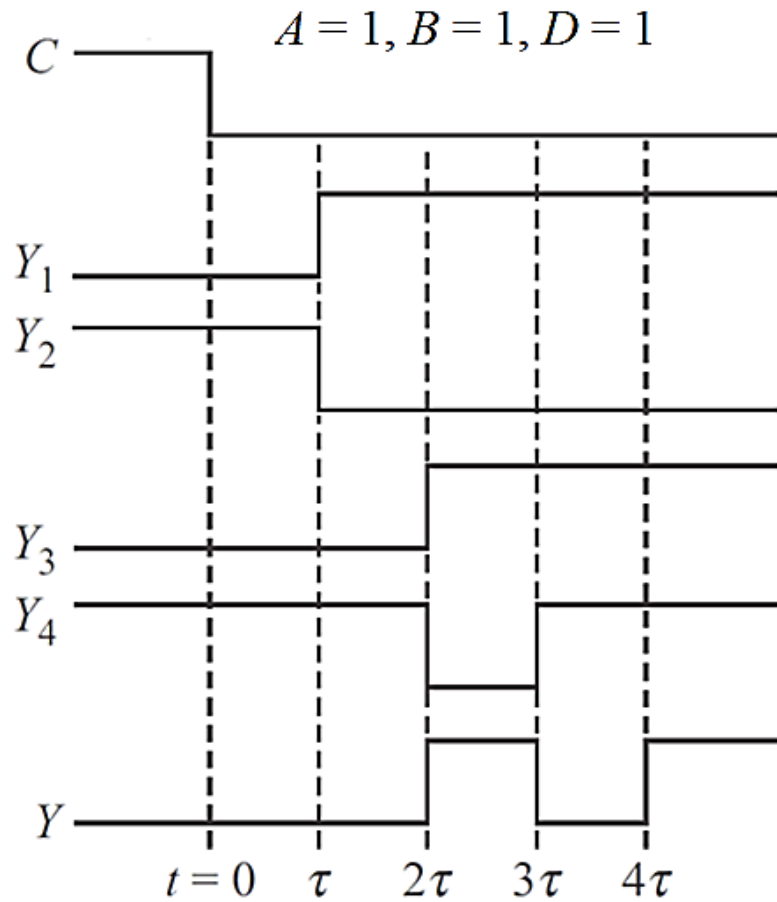

$$Y = (A.C + B.(C.D)') . (C.D)'$$

Covering Dynamic Hazard

Consider,

$$Y = (A.C + B.C').(CD)'$$

For, $A = 1, B = 1, D = 1$

$$Y = (C + C').C' \rightarrow \text{Multiple transition at } Y \text{ for } C: 1 \rightarrow 0$$

To prevent, cover implicit Static 1 or 0 hazard

$$Y = (A.C + B.C' + A.B).(CD)'$$

For, $A = 1, B = 1, D = 1$

$$Y = (C + C' + 1).C' = C' \rightarrow \text{Single transition}$$

Alternatively, convert multiple-level to 2-level circuit and cover hazard, if any.


Digital Building Blocks: **Beyond Basic Gates**

If-Then-Else

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Y = A'.C + A.B$$

<i>BC</i>		00	01	11	10
<i>A</i>	0	0	1	1	0
	1	0	0	1	1

 

If **A** (i.e. $A = 1$)
Then, $Y = B$
Else, $Y = C$

<i>A</i>	<i>Y</i>
0	<i>C</i>
1	<i>B</i>



Multiplexer

$$Y = A'.C + A.B$$

Consider,
A = Control (Select)
input, S_0
B = Data input, D_1
C = Data input, D_0

$$Y = S_0'.D_0 + S_0.D_1$$

S_0	Y
0	D_0
1	D_1

  

A multiplexer steers one of the many inputs to an output based on control input(s).




Consider, $S_0 = A$, $D_0 = B$, $D_1 = B'$
then, $Y = A'.B + A.B' = A \text{ XOR } B$

How to get $Y = A.B$?

4-to-1 Multiplexer


S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3
   
$$Y = S_1'S_0'D_0 + S_1'S_0D_1 + S_1S_0'D_2 + S_1S_0D_3$$






4-to-1 MUX from 2-to-1 MUX


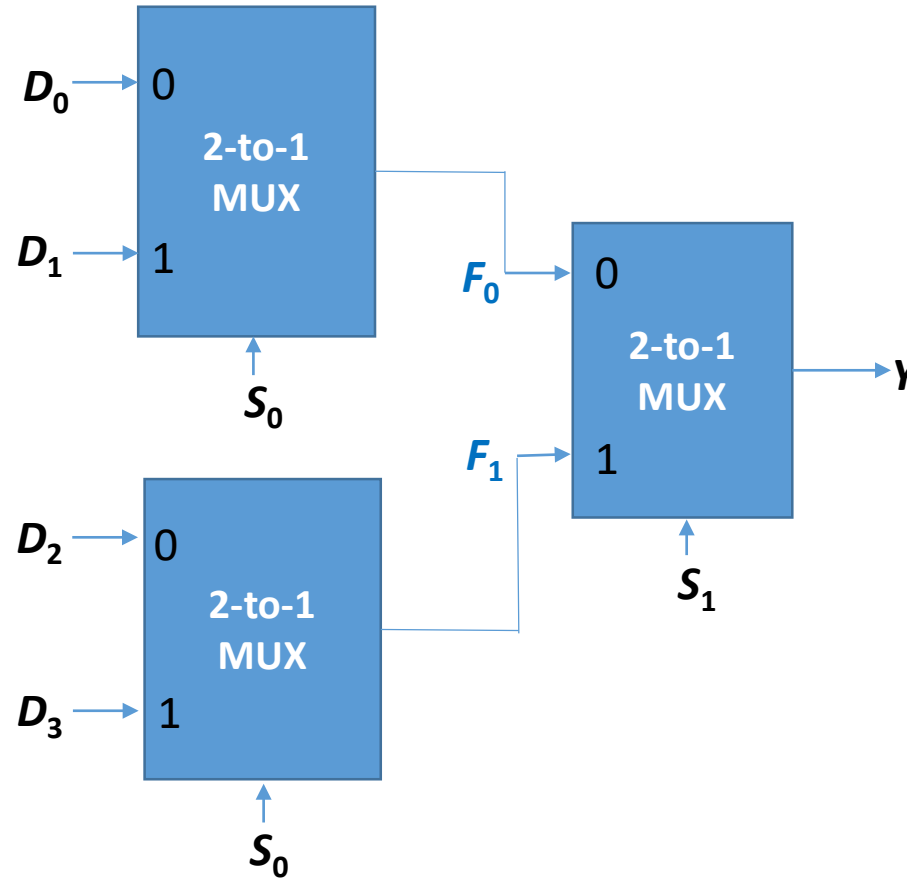
$$\begin{aligned} Y &= S_1'S_0'D_0 + S_1'S_0D_1 + S_1S_0'D_2 + S_1S_0D_3 \\ &= S_1'.(\textcolor{blue}{S_0}'D_0 + \textcolor{blue}{S_0}D_1) + S_1.(\textcolor{green}{S_0}'D_2 + \textcolor{green}{S_0}D_3) \\ &= S_1'.\textcolor{blue}{F_0} + S_1.\textcolor{green}{F_1} \end{aligned}$$



Higher order MUX from lower order

  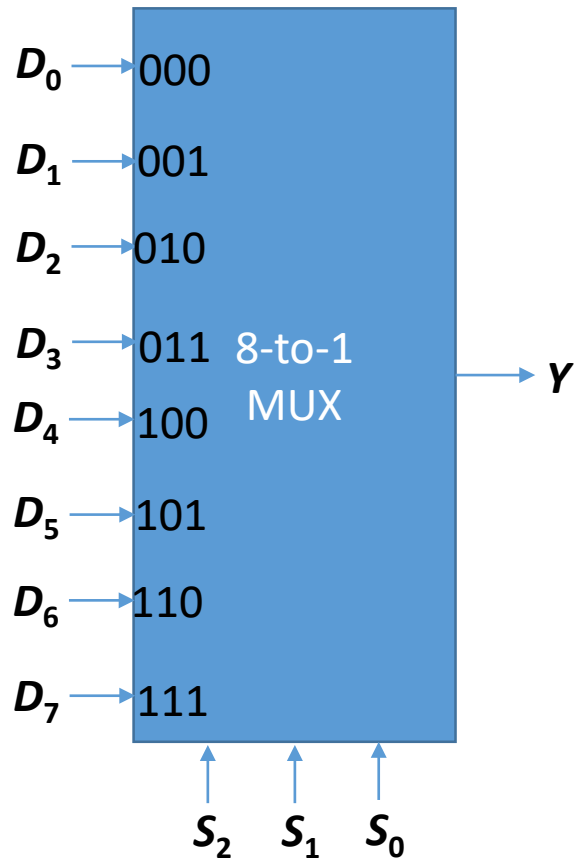

Higher order MUX from lower order

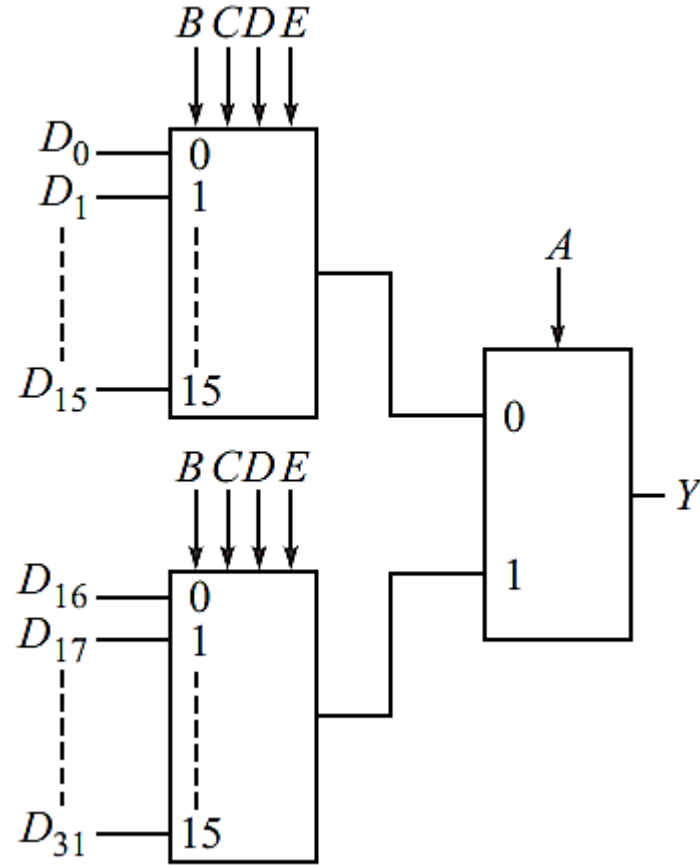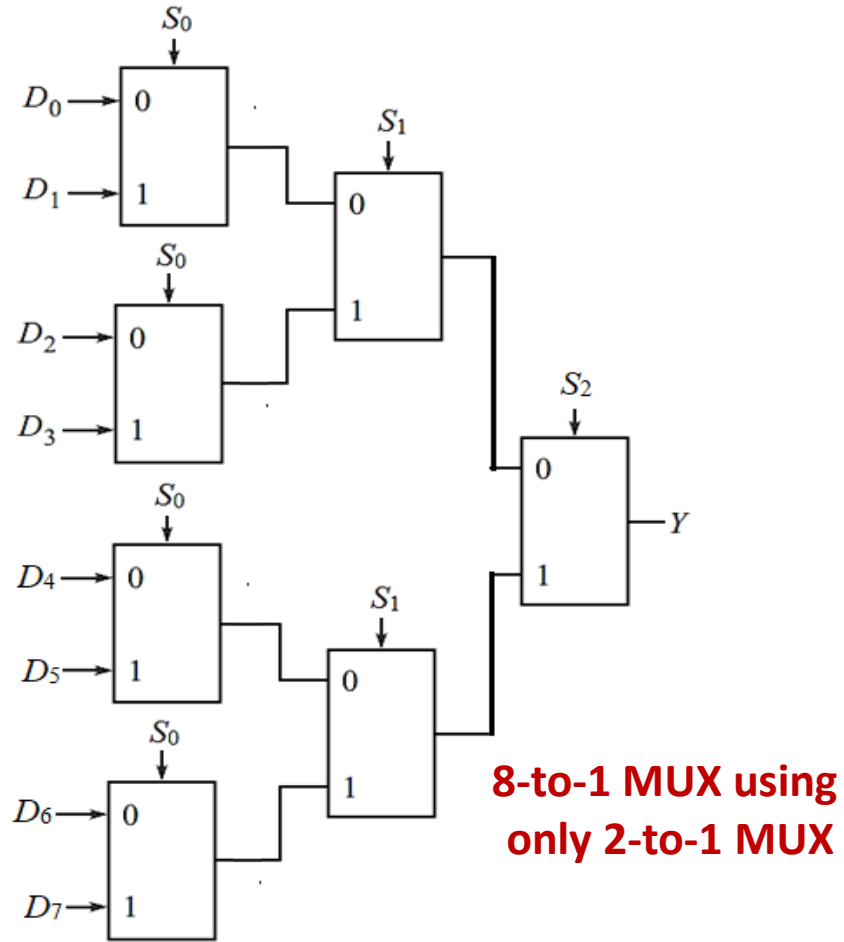

**32-to-1 MUX from
16-to-1 MUX
and 2-to-1 MUX**




Shanon's Expansion Theorem and MUX

Shanon's Expansion Theorem: (inherent If-Then-Else)


$$F(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot F(0, x_2, x_3, \dots, x_N) + x_1 \cdot F(1, x_2, x_3, \dots, x_N)$$

$$\begin{aligned} Y &= S_1' S_0' D_0 + S_1' S_0 D_1 + S_1 S_0' D_2 + S_1 S_0 D_3 \\ &= S_1' \cdot [0' \cdot S_0' D_0 + 0' \cdot S_0 D_1 + 0 \cdot S_0' D_2 + 0 \cdot S_0 D_3] + S_1 \cdot [1' \cdot S_0' D_0 + 1' \cdot S_0 D_1 + 1 \cdot S_0' D_2 + 1 \cdot S_0 D_3] \\ &= S_1' \cdot (S_0' D_0 + S_0 D_1) + S_1 \cdot (S_0' D_2 + S_0 D_3) \end{aligned}$$
 
$$\begin{aligned} F(x_1, x_2, x_3, \dots, x_N) &= x_1' \cdot [x_2' \cdot F(0, 0, x_3, \dots, x_N) + x_2 \cdot F(0, 1, x_3, \dots, x_N)] \\ &\quad + x_1 \cdot [x_2' \cdot F(1, 0, x_3, \dots, x_N) + x_2 \cdot F(1, 1, x_3, \dots, x_N)] \end{aligned}$$




Shanon's Expansion Theorem and MUX

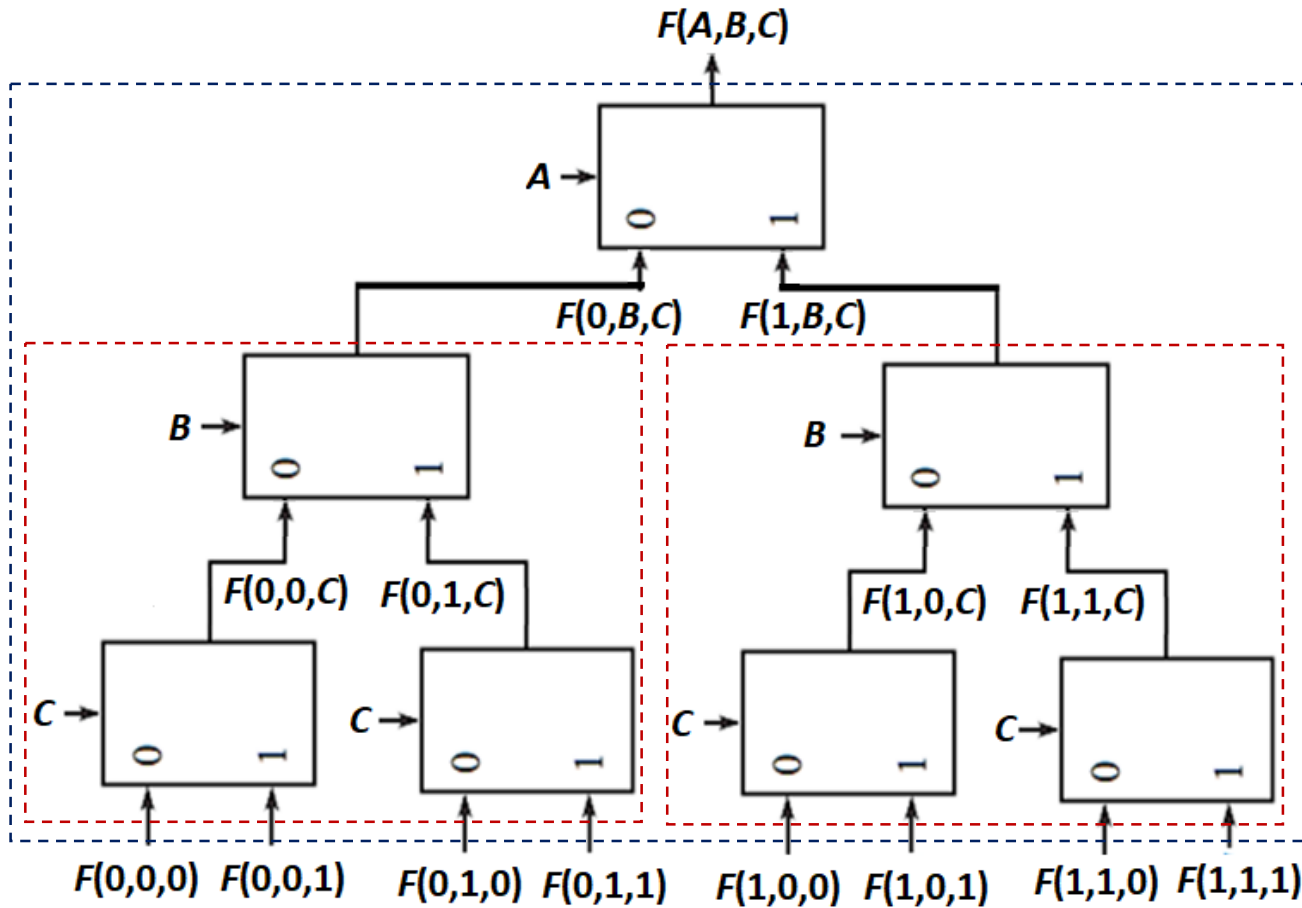

$$F(A,B,C) = A'B'C'.D_0 + A'B'C.D_1 + A'BC'.D_2 + A'BC.D_3 + AB'C'.D_4 + AB'C.D_5 + ABC'.D_6 + ABC.D_7$$


A	B	C	$F(A,B,C)$	
0	0	0	1	$D_0 = 1$
0	0	1	0	$D_1 = 0$
0	1	0	0	$D_2 = 0$
0	1	1	1	$D_3 = 1$
...	

IC 74153

 

IC 74153
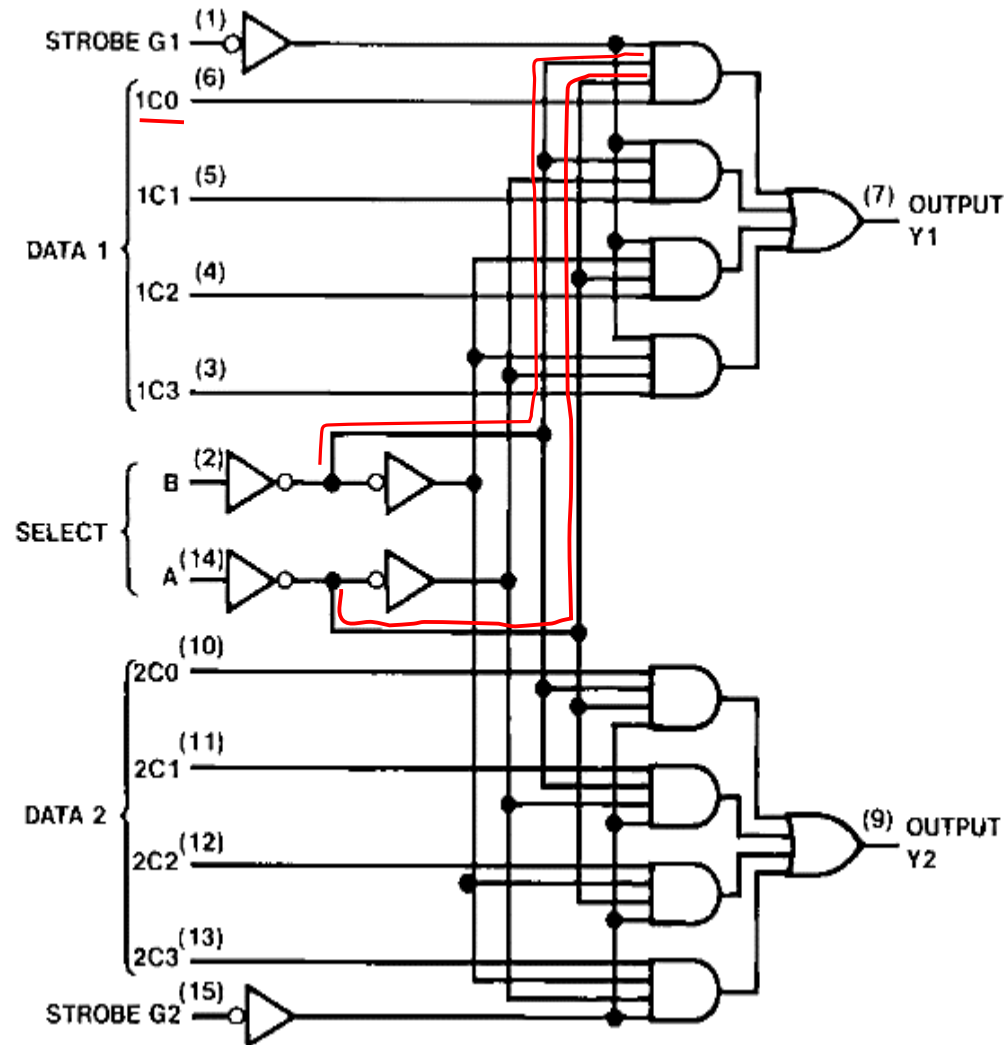
$$Y = E' \cdot [(B' \cdot A') \cdot C0 + (B' \cdot A) \cdot C1 + (B \cdot A') \cdot C2 + (B \cdot A) \cdot C3]$$



STROBE (G)	B	A	Y
H	X	X	L
L	L	L	C0
L	L	H	C1
L	H	L	C2
L	H	H	C3

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill