

# **Digital Electronic Circuits**

## **Section 1 (EE, IE)**


### **Lecture 1**

# Why Digital?

- Popular terms of current times:
  - Digital Clock, Digital Camera, Digital Money, Digital Media, ...
- Prefix 'Digital' associates a term with digital technology.
- Digital technology is considered more efficient for reasons such as:
  - Easy to store, copy, compress
  - Various transmission options
  - Flexibility in processing
  - Inexpensive building block
  - Immunity: noise, interference
  - Error correction, encryption
  - Analysis of data
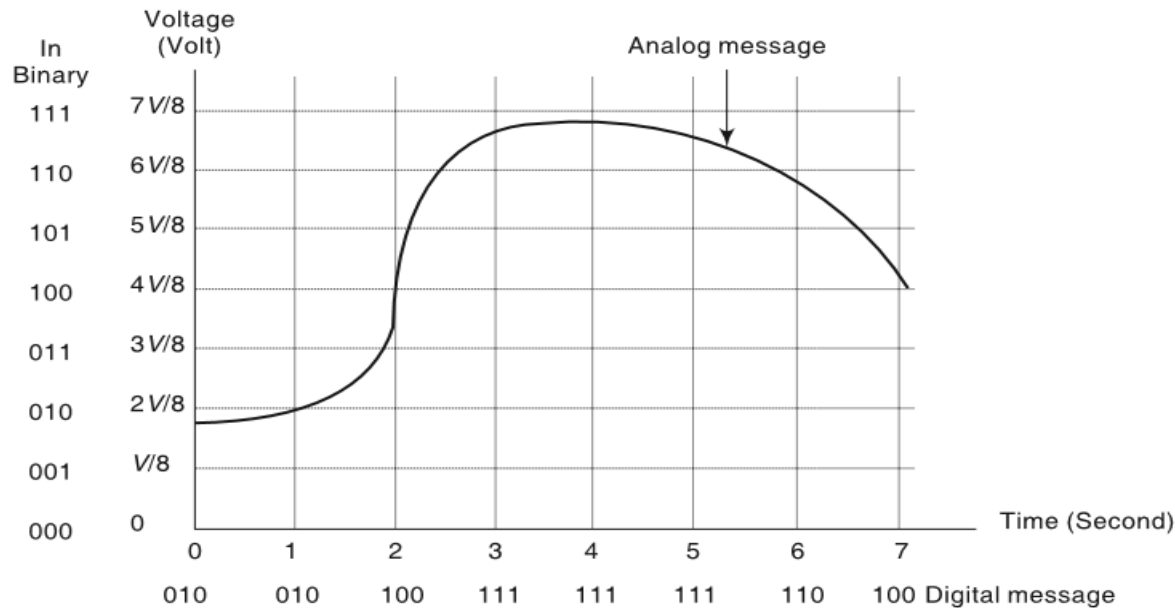
# What is Digital?


- Digital signals represent only finite number of discrete values (2 valued: Binary).
  - Signal is discrete by nature
  - Signal, analog by nature, converted to discrete



- Digital systems represent and manipulate digital signals.

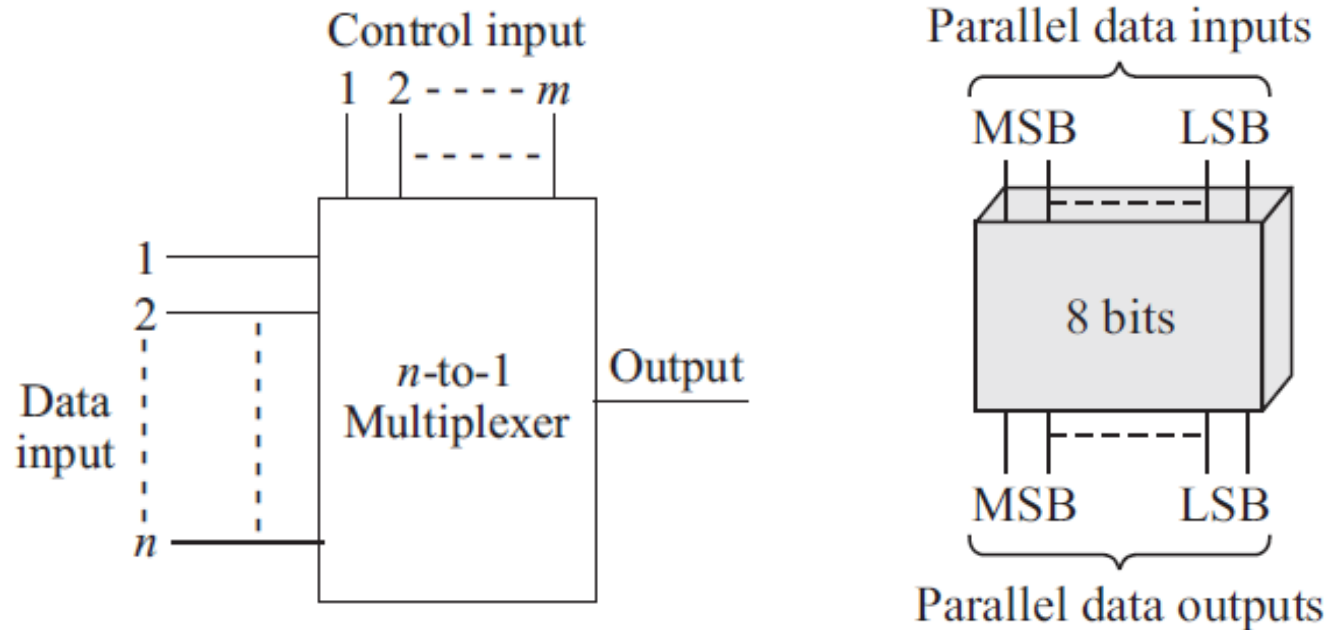
# Manipulation of Digital Signals

- Switching is key to manipulation of digital signals.
- Digital data storage involves switching.




# Switching & Logic Operation

## Realization of AND

 


$V_1$	$V_2$	$V_o$
$L$	$L$	$L$
$H$	$L$	$L$
$L$	$H$	$L$
$H$	$H$	$H$

 

# Switching & Logic Operation

## Realization of OR

 


$V_1$	$V_2$	$V_o$
$L$	$L$	$L$
$H$	$L$	$H$
$L$	$H$	$H$
$H$	$H$	$H$





# Switching & Logic Operation

## Realization of NOT

 


$V_i$	$V_o$
L	H
H	L

  


# Switching Circuits

## Realization of Tristate

 



$V_i$	$G$	$V_o$
$L$	$L$	Open
$H$	$L$	Open
$L$	$H$	$L$
$H$	$H$	$H$

 



# Diode as a switch



- Realization of AND, OR logic

  

- Possibility of realizing NOT logic

# Transistor as a switch
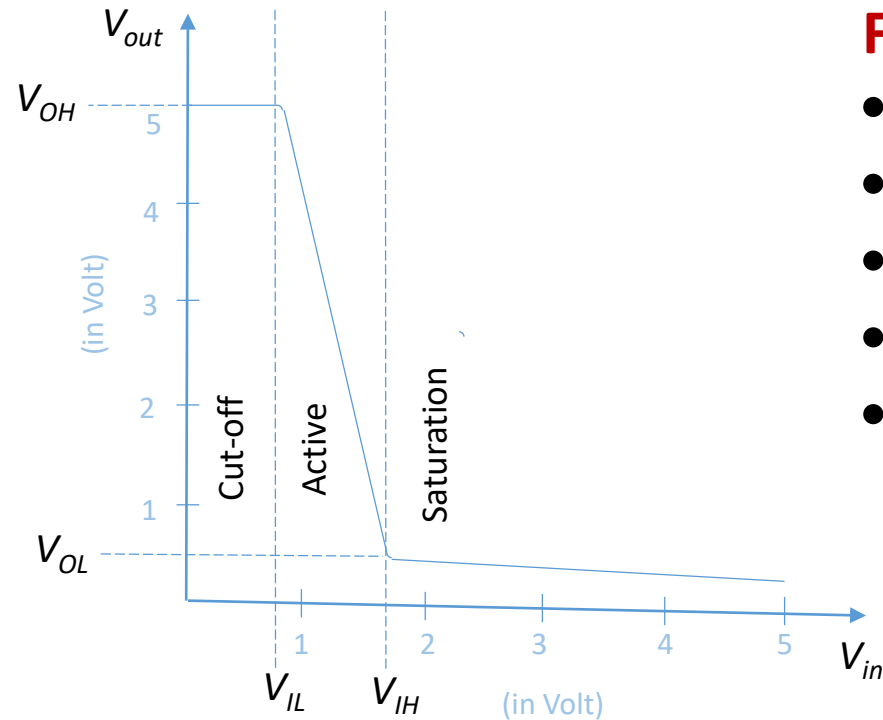 
## Realization of NOT gate (inverter), Input-Output Characteristics




### For quantitative analysis:

- $R_B = 10 \text{ k}\Omega$
- $R_C = 1 \text{ k}\Omega$
- $\beta_F = 50$
- $V_{BE(ON)} = V_{BE(Sat)} = 0.7V$
- $V_{CE(Sat)} = 0.2V$

# Transistor as a switch
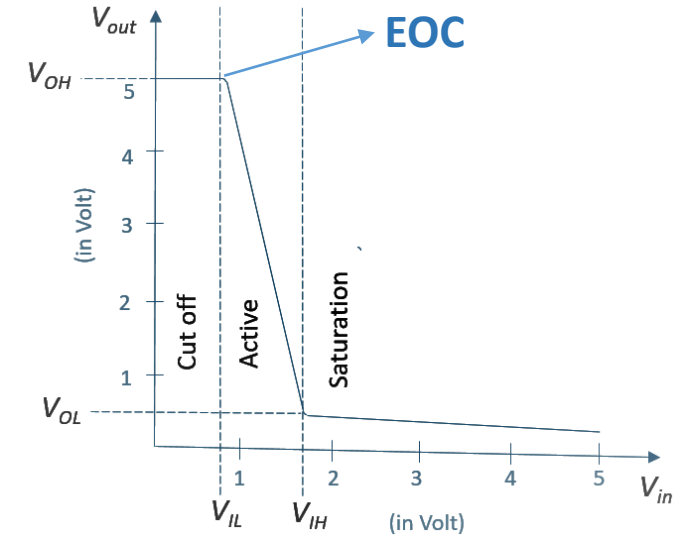
## Cut-off region


- Base current  $I_B = 0$  till  $V_{BE} < 0.7V$  i.e.  $V_{in} < 0.7V$ .
- Transistor is *cut off* and  $I_C = 0$  with  $V_{out} = 5V$  over entire range.
- When  $V_{in}$  is increased beyond  $0.7V$ , base current begins to flow and the transistor moves from *cut off* region to *normal active* region.
- The coordinate,  $V_{in} = 0.7V$ ,  $V_{out} = 5V$  mark first transition point in the transfer function of this circuit. This is also termed as *breakpoint* or *edge of cutoff* (EOC).



# Transistor as a switch
 
## Active region

- Applying KVL along  $V_{in}$ ,  $R_B$ ,  $V_{BE}$ , Ground  
$$I_B = (V_{in} - V_{BE(on)})/R_B$$
- In active region,  $I_C = \beta_F I_B$  (as long as  $V_{CE} < V_{CE(sat)}$ )
- Applying KVL along  $V_{CC}$ ,  $R_C$ ,  $V_{CE}$ , Ground  
$$V_{out} = V_{CC} - I_C R_C = V_{CC} - \beta_F I_B R_C$$
- Combining,  
$$V_{out} = V_{CC} - \beta_F R_C (V_{in} - V_{BE(on)})/R_B$$



# Transistor as a switch

## Saturation region


- As  $V_{in}$  (or  $I_B$ ) is increased a second transition point is reached when  $V_{out} = V_{CE(sat)}$ .
- The values of  $I_C$  and  $I_B$  for this condition (the subscript EOS means *edge of saturation*):

$$I_{C(EOS)} = (V_{CC} - V_{CE(sat)})/R_C = (5-0.2)/1 = 4.8\text{mA}$$

$$\text{and } I_{B(EOS)} = I_{C(EOS)}/\beta_F = 4.8/50 = 0.096\text{mA}$$


$$\text{Then } V_{in(EOS)} = V_{BE(on)} + I_{B(EOS)} R_B = 0.7 + (0.096)(10) = 1.66\text{V}$$

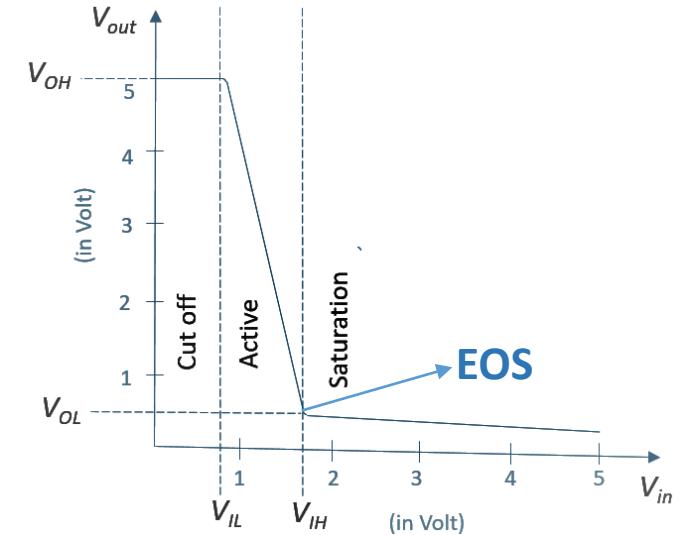- Thus  $V_{in} \geq 1.66\text{V}$  the transistor saturates. (Saturating Logic)



# Input-Output Mapping
 
## Noise Margin, Transition width and Logic swing



$$NM_L = V_{IL} - V_{OL} = 0.7 - 0.2 = 0.5V$$


$$NM_H = V_{OH} - V_{IH} = 5.0 - 1.66 = 3.34V$$

$$\begin{aligned} \text{Transition width} &= V_{IH} - V_{IL} \\ &= 1.66 - 0.7 = 0.96V \end{aligned}$$

$$\begin{aligned} \text{Logic swing} &= V_{OH} - V_{OL} \\ &= 5 - 0.2 = 4.8V \end{aligned}$$

# Fanout

## Input to driver transistor: HIGH

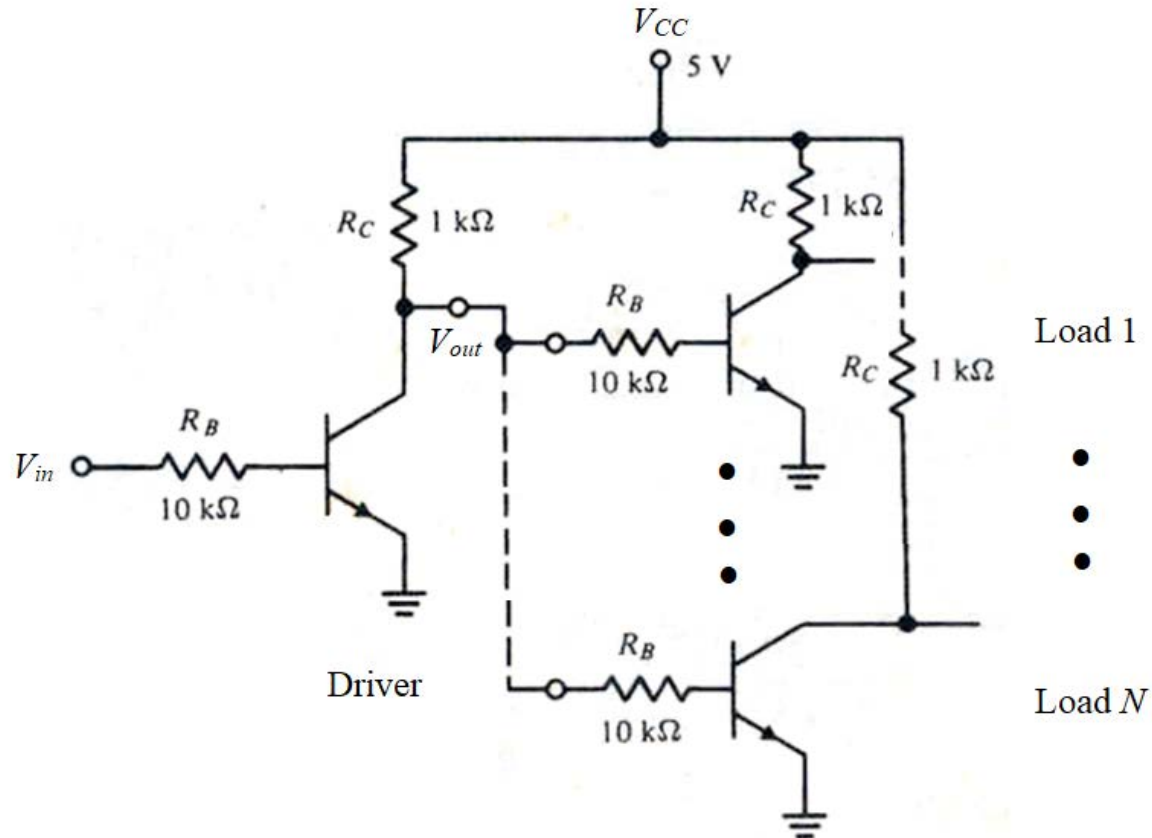


- When  $V_{in}$  is HIGH, driver transistor is saturated and  $V_{out}$  will be LOW.
- With  $V_{CE(sat)} = 0.2V$  all the load gates will be in the OFF state.
- No restriction on number of load gates

# Fanout
 
## Input to driver transistor: LOW

- When  $V_{in}$  is LOW, driver transistor will be OFF and  $V_{out}$  will be at HIGH level.
  - A limit in the fanout is set when the voltage at  $V_{out}$  is insufficient to saturate load gate transistors.
  - Note that  $V_{IH} = 1.66V$
  - For driver,  $I_{C(driver)} = (V_{CC} - V_{out})/R_C = (5 - 1.66)/1 = 3.34 \text{ mA}$
  - For load,  $I_{B(load)} = (V_{out} - V_{BE(sat)})/R_B$   
 $= (1.66 - 0.7)/10 = 0.096 \text{ mA}$
- $$N = I_{C(driver)}/I_{B(load)} = 34.79 \rightarrow 34$$





# Fanout

## Effect of noise margin

- For a 0.5V noise margin,

Minimum HIGH level voltage at  $V_{out}$

$$V_{OH} = V_{IH} + NM_H = 1.66 + 0.5 = 2.16V$$

- Similar calculation as before with  $V_{out}$  at 2.16V gives

$$I_{C(driver)} = (V_{CC} - V_{out})/R_C = (5 - 2.16)/1 = 2.84 \text{ mA}$$

$$I_{B(load)} = (V_{out} - V_{BE(sat)})/R_B = (2.16 - 0.7)/10 = 0.15 \text{ mA}$$

$$N = I_{C(driver)}/I_{B(load)} = 19.4 \rightarrow 19$$

- An increased  $NM_H$  reduces fanout even further

### Other factors:

Variation in  $\beta_F$ ,  $V_{BE(sat)}$ ,  
 $V_{CE(sat)}$ ,  $V_{CC}$ ,  $R_C$ ,  $R_B$ .

## References:

- ❑ Grinich, V.H., and H.G. Jackson, Introduction to Integrated Circuits, McGraw-Hill
- ❑ Donald P. Leach, Albert P. Malvino and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ Herbert Taub, and Donald Schilling, Digital Integrated Electronics, McGraw Hill
- ❑ M. Morris Mano, and Michael D. Ciletti, Digital Design 5e, Pearson