


# **Digital Electronic Circuits**

## **Section 1 (EE, IE)**

### **Lecture 27**

 
# Algorithmic State Machine (ASM) Chart

- State Transition Diagram though compact is unsuitable for describing large state machines.
- Algorithmic State Machine (ASM) chart is a flow diagram like representation to design sequential digital electronic circuits.




$n$  input:  $2^n$  branch at each state


## Basic Components:

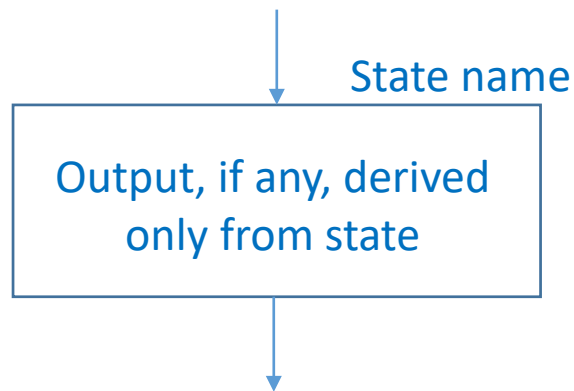

State Box

 

Conditional Output Box

 

Decision Box


# ASM Chart: Mealy Model - Part 1

## Problem Statement:

Design circuit for a vending machine that takes only Rs. 5 and Rs. 10 coin as inputs to deliver a product that is priced Rs. 15. Coin sensing is as follows.

<i>I</i>	<i>J</i>	Activity
0	X	No coin deposited
1	0	Rs. 5 deposited
1	1	Rs. 10 deposited

 Other than the output, *X* for product, there is another output, *Y* to return Rs. 5 if Rs. 20 is received by the machine anyhow.



At every clock trigger, *I* is sensed. If *I* = 0, state is maintained. Both output are 0.

## State Definition:

*a*: Initial state i.e. money accumulated is zero.


*b*: Rs. 5 accumulated.

*c*: Rs. 10 accumulated.
 
# Part 2

At state  $a$ , If  $I = 1$ , a coin has been deposited.

Then decision is taken on  $J = 0 / J = 1$  whether the circuit goes to state  $b$  / state  $c$ , at next clock trigger.



## State Definition:

$a$ : Initial state i.e. money accumulated is zero.

$b$ : Rs. 5 accumulated.


$c$ : Rs. 10 accumulated.

At state  $a$ , if  $IJ = 11$ , then, output  $XY = 00$ .
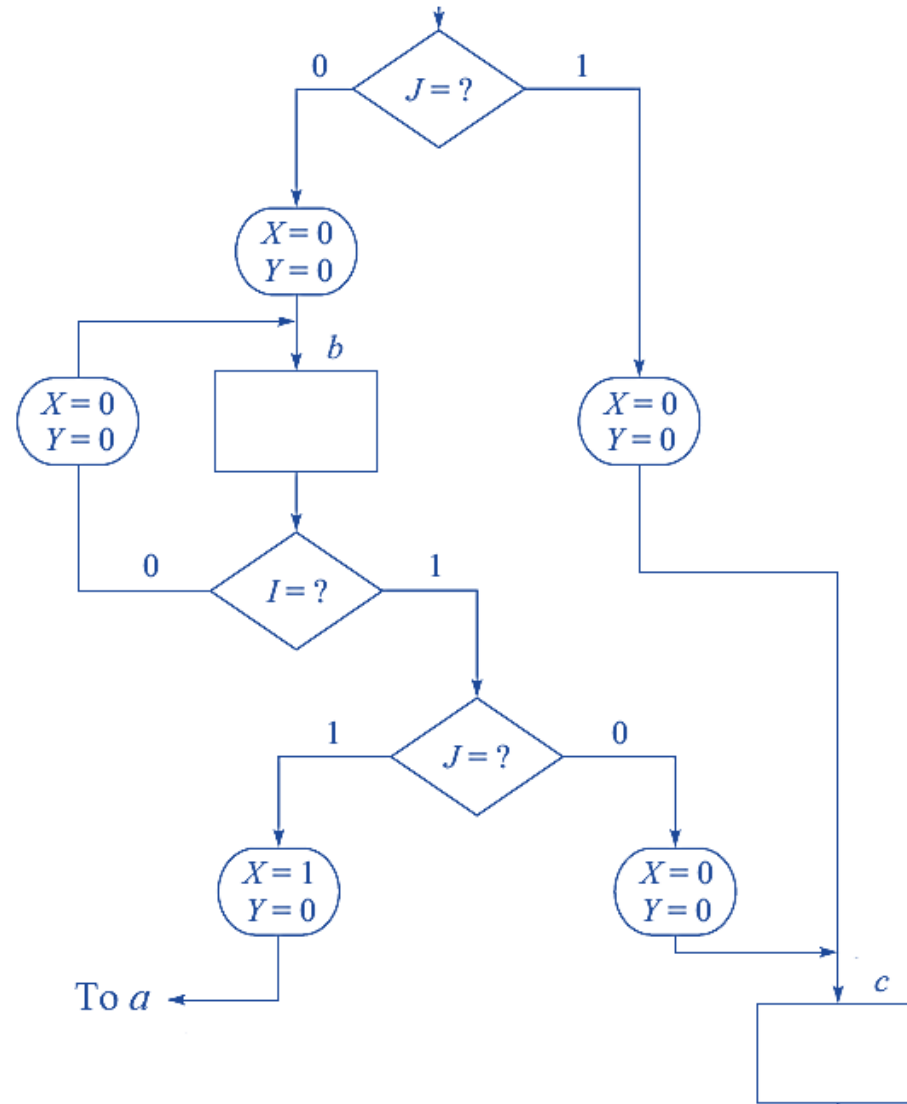
# Part 3

At state *b*, If  $I = 1$ , a coin has been deposited.

Then decision is taken on  $J = 0 / J = 1$  whether the circuit goes to state *c* with  $XY = 00$  / delivers product with  $XY = 10$  and goes to state *a*, at next clock trigger.



## State Definition:

*a*: Initial state i.e. money accumulated is zero.


*b*: Rs. 5 accumulated.

*c*: Rs. 10 accumulated.
 
# Part 4

At state  $c$ , If  $I = 1$ , a coin has been deposited.

Then decision is taken on  $J = 0 / J = 1$  whether only product is delivered with  $XY = 10$  to go to state  $a$  / product delivery and Rs. 5 return happen with  $XY = 11$  and circuit goes to state  $a$ , at next clock trigger.



## State Definition:


$a$ : Initial state i.e. money accumulated is zero.

$b$ : Rs. 5 accumulated.

$c$ : Rs. 10 accumulated.
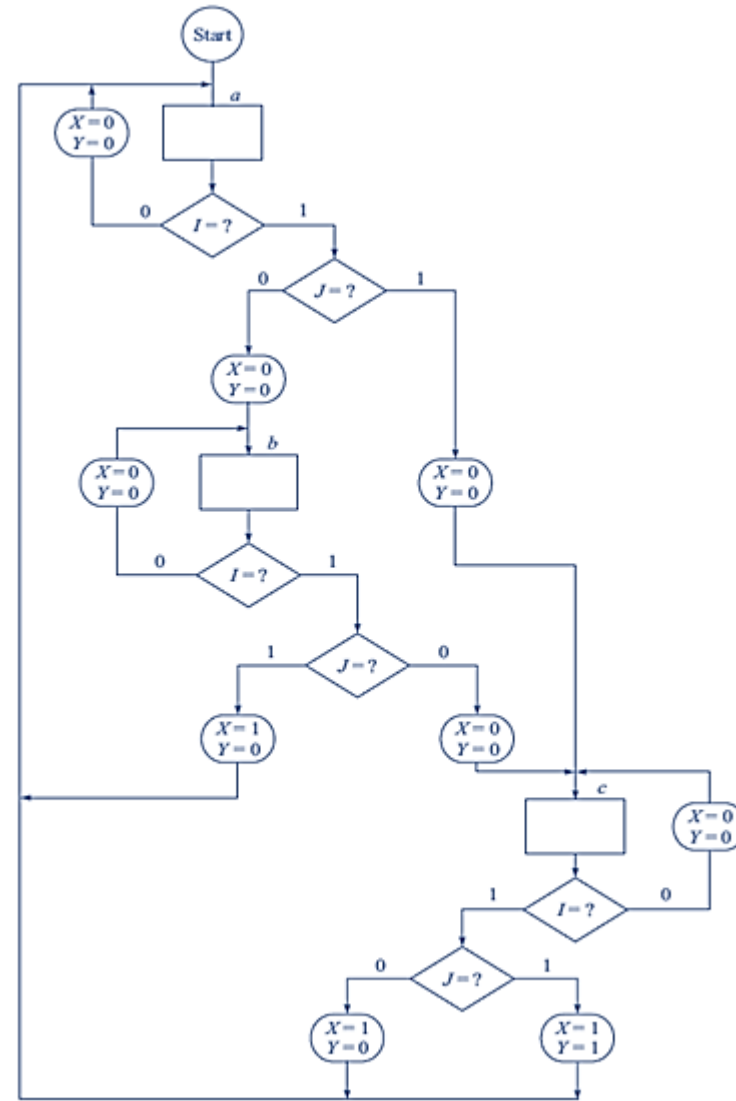
# Full ASM Chart

Full ASM Chart for the vending machine example.





# ASM Chart: Moore Model

## Problem Statement:

A sequence detector for '110' from a binary data stream is to be designed.

ASM Chart

 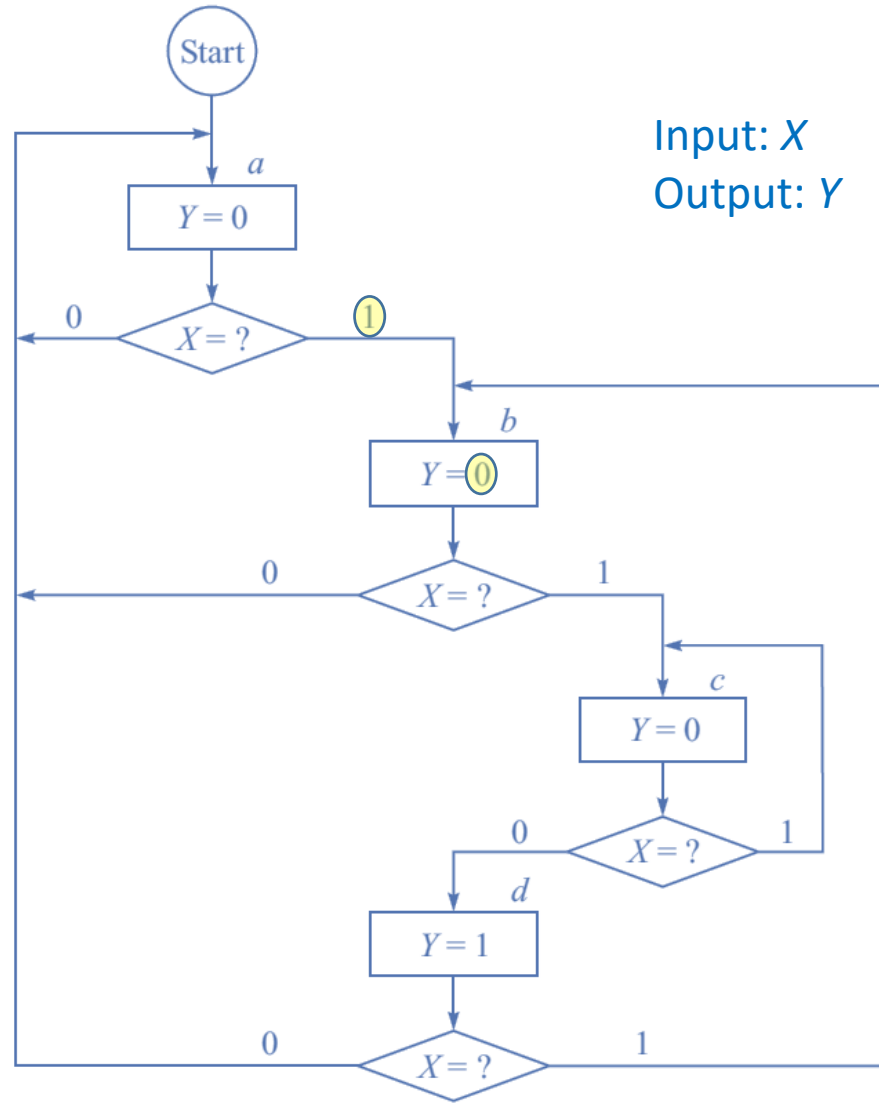

State Transition Diagram




# State Assignment

## Problem Statement:

Design circuit for a vending machine that takes only Rs. 5 and Rs. 10 coin as inputs to deliver a product that is priced Rs. 15. Coin sensing is as follows.

$I$	$J$	Activity
0	X	No coin deposited
1	0	Rs. 5 deposited
1	1	Rs. 10 deposited

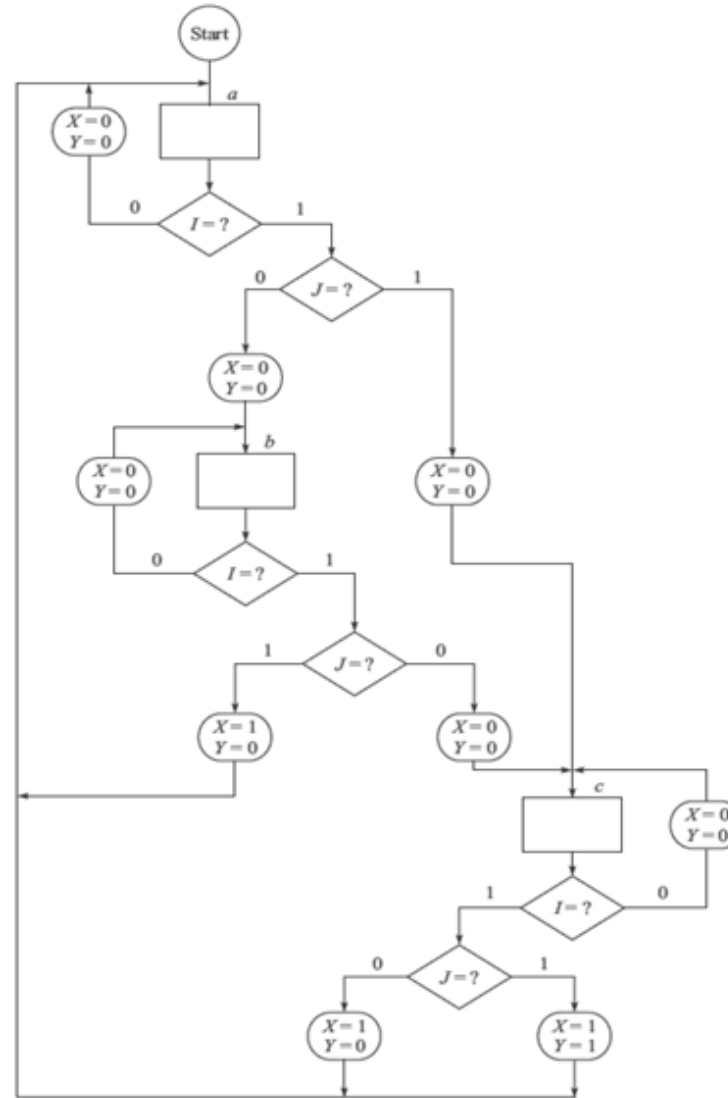Other than the output,  $X$  for product , there is another output,  $Y$  to return Rs. 5 if Rs. 20 is reached anyhow.



$a$ : Initial state i.e. money accumulated is zero.

***b***: Rs. 5 accumulated.

**c:** Rs. 10 accumulated.

## Two flip-flops: $BA$

State	$B$	$A$
$a$	0	0
$b$	0	1
$c$	1	0

# State Table

Present State		Input		Next State		Output		$D_B$	$D_A$
$B_n$	$A_n$	$I$	$J$	$B_{n+1}$	$A_{n+1}$	$X$	$Y$		
0	0	0	0	0	0	0	0	0	0
		0	1	0	0	0	0	0	0
		1	0	0	1	0	0	0	1
		1	1	1	0	0	0	1	0
0	1	0	0	0	1	0	0	0	1
		0	1	0	1	0	0	0	1
		1	0	1	0	0	0	1	0
		1	1	0	0	1	0	0	0
1	0	0	0	1	0	0	0	1	0
		0	1	1	0	0	0	1	0
		1	0	0	0	1	0	0	0
		1	1	0	0	1	1	0	0

- $a$ : Initial state i.e. money accumulated is zero.
- $b$ : Rs. 5 accumulated.
- $c$ : Rs. 10 accumulated.

State	$B$	$A$
$a$	0	0
$b$	0	1
$c$	1	0

# Design Equations

$B_n A_n$					
		0 0	0 1	1 1	1 0
$IJ$	0 0	0	0	×	1
	0 1	0	0	×	1
	1 1	1	0	×	0
	1 0	0	1	×	0

$$D_B = \overline{I}B_n + I\overline{J}A_n + IJ\overline{B}_n\overline{A}_n$$

$IJ \backslash B_n A_n$					
		0 0	0 1	1 1	1 0
0 0	0	1	×	0	
0 1	0	1	×	0	
1 1	0	0	×	0	
1 0	1	0	×	0	

$$D_A = \overline{I}A_n + I\overline{J}\overline{B}_n\overline{A}_n$$

Present State		Input		Next State		Output		$D_B$	$D_A$
$B_n$	$A_n$	$I$	$J$	$B_{n+1}$	$A_{n+1}$	$X$	$Y$		
0	0	0	0	0	0	0	0	0	0
		0	1	0	0	0	0	0	0
		1	0	0	1	0	0	0	1
		1	1	1	0	0	0	1	0
0	1	0	0	0	1	0	0	0	1
		0	1	0	1	0	0	0	1
		1	0	1	0	0	0	1	0
		1	1	0	0	1	0	0	0
1	0	0	0	1	0	0	0	1	0
		0	1	1	0	0	0	1	0
		1	0	0	0	1	0	0	0
		1	1	0	0	1	1	0	0

# Design Equations

$IJ \backslash B_n A_n$					
		0 0	0 1	1 1	1 0
0 0	0	0	×	0	
0 1	0	0	×	0	
1 1	0	1	×	1	
1 0	0	0	×	1	


$$X = IB_n + IJA_n$$

$IJ \backslash B_n A_n$					
		0 0	0 1	1 1	1 0
0 0	0	0	×	0	
0 1	0	0	×	0	
1 1	0	0	×	1	
1 0	0	0	×	0	

$$Y = IJB_n$$

Present State		Input		Next State		Output		$D_B$	$D_A$
$B_n$	$A_n$	$I$	$J$	$B_{n+1}$	$A_{n+1}$	$X$	$Y$		
0	0	0	0	0	0	0	0	0	0
		0	1	0	0	0	0	0	0
		1	0	0	1	0	0	0	1
		1	1	1	0	0	0	1	0
0	1	0	0	0	1	0	0	0	1
		0	1	0	1	0	0	0	1
		1	0	1	0	0	0	1	0
		1	1	0	0	1	0	0	0
1	0	0	0	1	0	0	0	1	0
		0	1	1	0	0	0	1	0
		1	0	0	0	1	0	0	0
		1	1	0	0	1	1	0	0

# Circuit Diagram

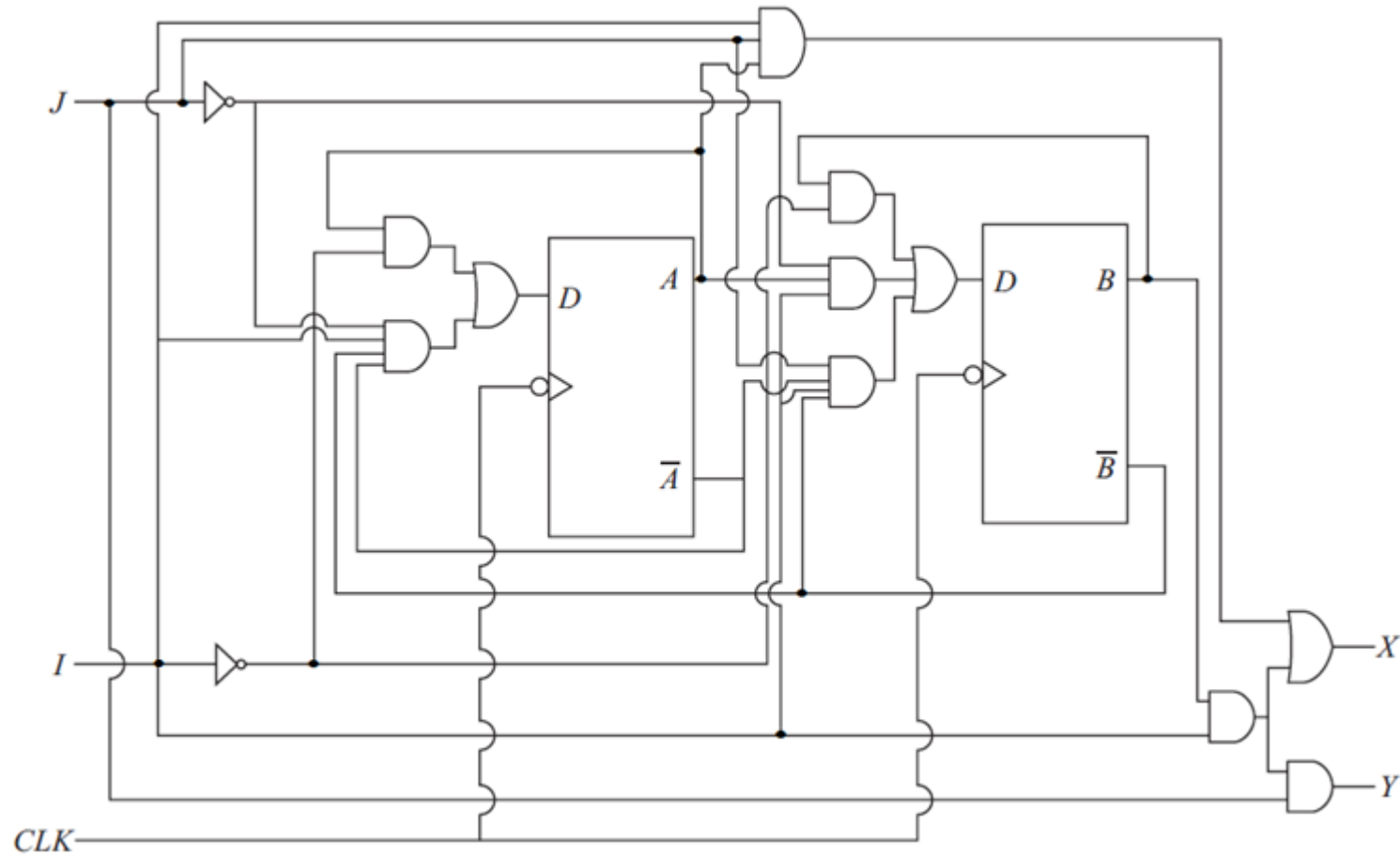

$$D_B = \bar{I}B_n + I\bar{J}A_n + IJ\bar{B}_n\bar{A}_n$$


$$D_A = \bar{I}A_n + I\bar{J}\bar{B}_n\bar{A}_n$$

$$X = IB_n + IJA_n$$

$$Y = IJB_n$$

# Use of Decoder-OR

Present State		Input		Next State		Output		$D_B$	$D_A$
$B_n$	$A_n$	$I$	$J$	$B_{n+1}$	$A_{n+1}$	$X$	$Y$		
0	0	0	0	0	0	0	0	0	0
		0	1	0	0	0	0	0	0
		1	0	0	1	0	0	0	1
		1	1	1	0	0	0	1	0
0	1	0	0	0	1	0	0	0	1
		0	1	0	1	0	0	0	1
		1	0	1	0	0	0	1	0
		1	1	0	0	1	0	0	0
1	0	0	0	1	0	0	0	1	0
		0	1	1	0	0	0	1	0
		1	0	0	0	1	0	0	0
		1	1	0	0	1	1	0	0

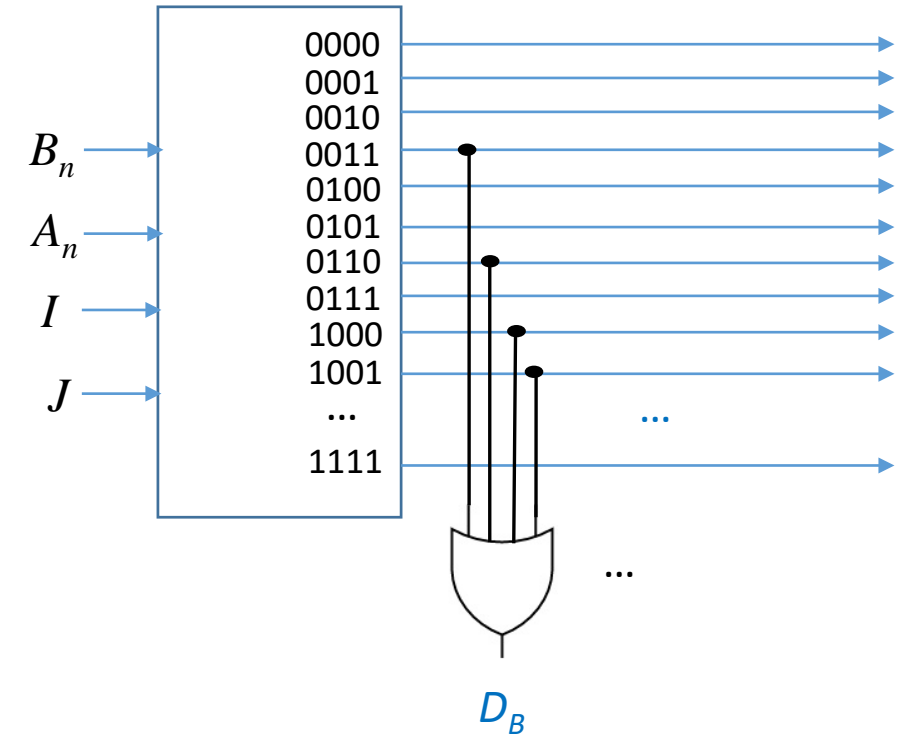

$$D_B = F(B_n, A_n, I, J) = \sum m(3, 6, 8, 9) \quad D_A = \sum m(2, 4, 5) \quad X = \sum m(7, 10, 11) \quad Y = \sum m(11)$$

## References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill