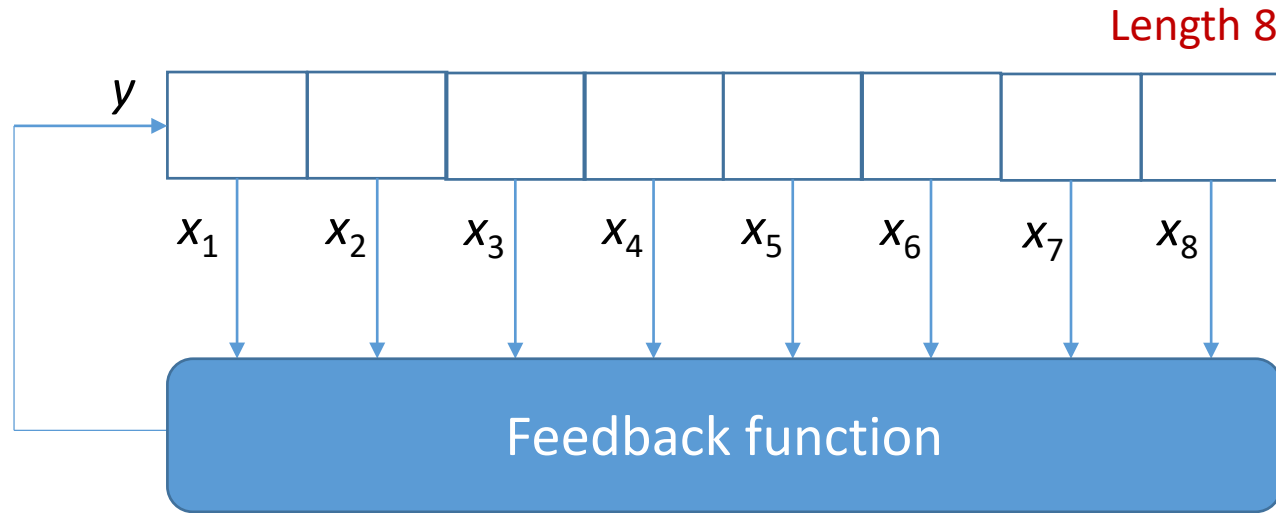


Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 24

Feedback Shift Register



Linear feedback example:

$$y = x_1 + x_2 + x_7$$

If shift register (SR) contains,

$$10011011 \rightarrow y = 1 + 0 + 1 = 0$$

With clock trigger, SR value

$$01001101 \rightarrow y = 0 + 1 + 0 = 1$$

...

Nonlinear feedback


example: $y = x_1x_2 + x_7$

$$\text{Linear feedback: } y = C_1x_1 + C_2x_2 + C_3x_3 + C_4x_4 + C_5x_5 + C_6x_6 + C_7x_7 + C_8x_8$$

$C_i = 0 \text{ or } 1 \Rightarrow$ when 1, the output bit is tapped

+ : Sum operation obtained by Ex-OR

Feedback Polynomial

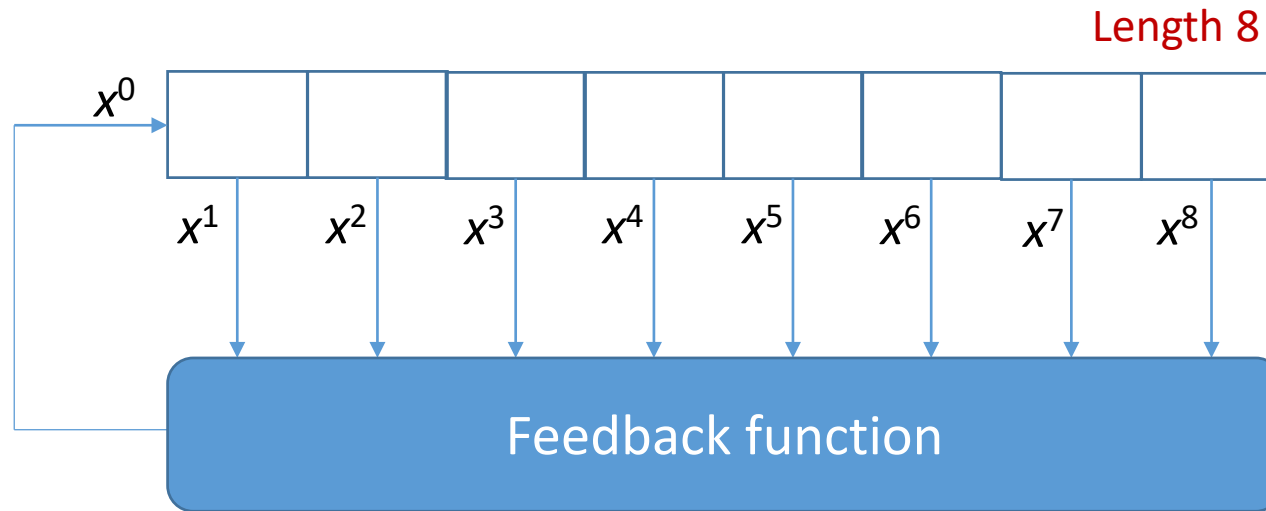

Example:

$$f(x) = x^8 + x^7 + x^4 + x^2 + x + 1$$

$$f(x) = x^8 + x^7 + x^2 + x + 1$$


$$f(x) = x^8 + x^7 + 1$$

Tap from bit 7 and 8
Ex-Ored and fed as
serial input to bit 1

$$f(x) = 1 + C_1x^1 + C_2x^2 + C_3x^3 + C_4x^4 + C_5x^5 + C_6x^6 + C_7x^7 + C_8x^8$$

For n -bit shift register, degree of the polynomial is n .

Pseudorandom Sequence

 

Q	R	S	T	Serial in = $S \oplus T$	Clock cycle
1	1	1	1	0	1
0	1	1	1	0	2
0	0	1	1	0	3
0	0	0	1	1	4
1	0	0	0	0	5
0	1	0	0	0	6
0	0	1	0	1	7
1	0	0	1	1	8
1	1	0	0	0	9
0	1	1	0	1	10
1	0	1	1	0	11
0	1	0	1	1	12
1	0	1	0	1	13
1	1	0	1	1	14
1	1	1	0	1	15
1	1	1	1	0	16 (repeats)

$$f(x) = x^4 + x^3 + 1$$

Cycle length = 15


Pseudorandom sequence:
000100110101111..

If QRST = 0000, it remains locked i.e. no change in state

Also possible with Ex-NOR feedback where 1111 excluded.

Non-Maximal Length

Q	R	S	T	$Serial\ in = R \oplus S$	$Clock\ cycle$
1	1	1	1	0	1
0	1	1	1	0	2
0	0	1	1	1	3
1	0	0	1	0	4
0	1	0	0	1	5
1	0	1	0	1	6
1	1	0	1	1	7
1	1	1	0	0	8
0	1	1	1	0	9

 

$$f(x) = x^3 + x^2 + 1$$

Cycle length = 7

Primitive Polynomials


- Polynomials that produce maximal length ($2^n - 1$) sequence are called primitive polynomials.
- Necessary (but, not sufficient condition) to be primitive polynomial
 - No. of taps even
 - Tap numbers are co-prime
- If tap sequence of n -bit LFSR generating primitive polynomial is $n, m, l, k, \dots, 0$ then the tap sequence $n - n, n - m, n - l, n - k, \dots, n - 0$ i.e. $0, n - m, n - l, n - k, \dots, n$ will also give primitive polynomial.

Degree	Polynomial [#]
2, 3, 4, 6, 7	$x^n + x + 1$
5	$x^5 + x^2 + 1$
8	$x^8 + x^6 + x^5 + x + 1$
9	$x^9 + x^4 + 1$
10	$x^{10} + x^3 + 1$

[#]Polynomial that requires minimum number of Ex-OR gates for given degree.

$x^{5-5} + x^{5-2} + x^{5-0}$
 i.e. $x^5 + x^3 + 1$
 is also primitive polynomial

Internal Feedback

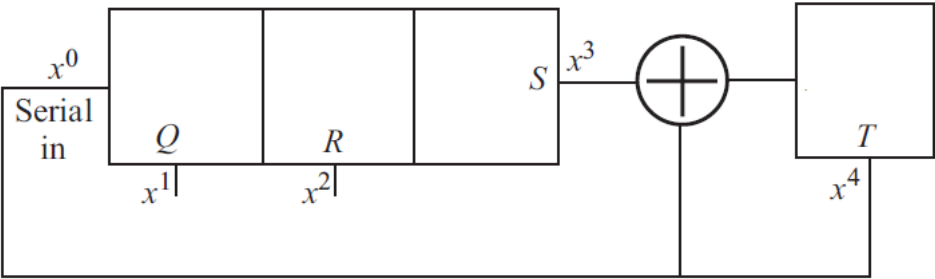

$$f(x) = x^4 + x^3 + 1$$

Cycle length = 15


Pseudorandom sequence with int. feedback:

101011001000111..

Pseudorandom sequence with ext. feedback:

000100110101111.. (earlier)

Q	R	S	T	Serial in = T	Input to T FF	Clock cycle
1	1	1	1	1	0	1
1	1	1	0	0	1	2
0	1	1	1	1	0	3
1	0	1	0	0	1	4
0	1	0	1	1	1	5
1	0	1	1	1	0	6
1	1	0	0	0	0	7
0	1	1	0	0	1	8
0	0	1	1	1	0	9
1	0	0	0	0	0	10
0	1	0	0	0	0	11
0	0	1	0	0	1	12
0	0	0	1	1	1	13
1	0	0	1	1	1	14
1	1	0	1	1	1	15
1	1	1	1	1	0	(repeats)

 


Ext. feedback

Primitive polynomial for external feedback also gives maximal length for internal feedback and generates pseudorandom sequence (different).

External Input

Example: Cycle Redundancy Check (CRC)

 

$$g(x) = x^3 + x + 1$$

Transmitter

Message: 1100101(000)

Remainder: 010

Coded
message: 1100101010
3 check bits

Receiver

Remainder: 000

No error

CRC is specially useful
for detecting burst error

Clock	S_{in}	Q_1	Q_2	Q_3
0	1	0	0	0
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1
4	1	1	1	1
5	0	0	0	1
6	1	1	1	0
7	0	1	1	1
8	0	1	0	1
9	0	1	0	0
10	-	0	1	0

$Q_1Q_2Q_3$: initialized with 000

Transmitter

Clock	S_{in}	Q_1	Q_2	Q_3
0	1	0	0	0
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1
4	1	1	1	1
5	0	0	0	1
6	1	1	1	0
7	0	1	1	1
8	1	1	0	1
9	0	0	0	0
10	end	0	0	0

Receiver

$$D_1 = S_{in} \oplus Q_3$$

$$D_2 = Q_1 \oplus Q_3$$

$$D_3 = Q_2$$


$$Q_{n+1} = D_n$$

Application

- Fast Counter: Simpler feedback for which higher clock rate is possible.
- Test pattern generator: Pseudorandom pattern is efficient in high fault-coverage of Application-Specific Integrated Circuit (ASIC).
- Scrambling: LFSR output is Ex-Ored with data to widen the bandwidth.
- Cryptography: Pseudorandom numbers are generated from an LFSR with a seed value which serves as cryptographic key and provides efficient encryption / decryption.
- Error Control Code: Used in Cycle Redundancy Check (CRC) for data transmission and storage. It is popular as it is easy to implement.


(CRC-16: $g(x) = x^{16} + x^{15} + x^2 + 1$ can detect up to 16 burst error)

Serial Addition

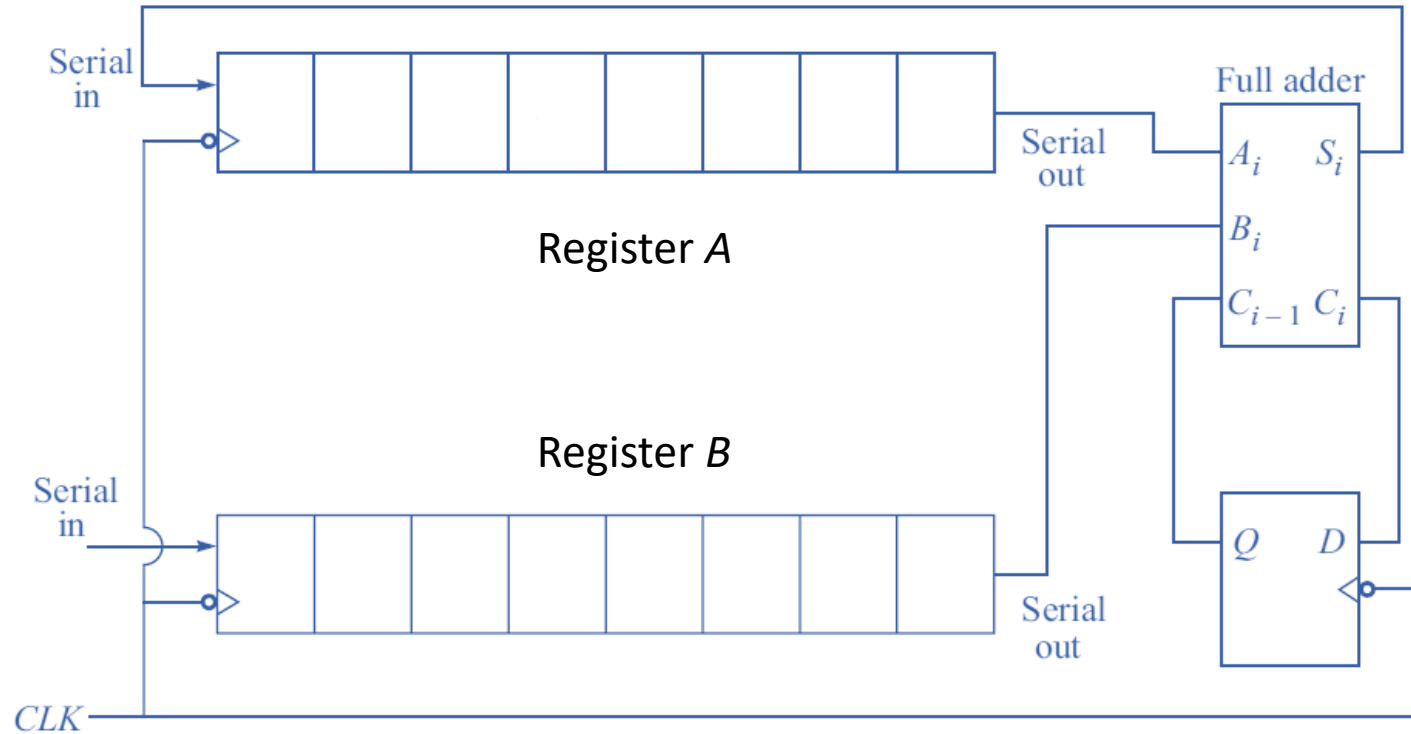

- Initially, register A and B store the addend and augend.
- Least significant bits are first out serially when addition starts.
- Initially, D flip-flop is reset. It stores the carry generated from i -th bit addition and feed that as input to $(i+1)$ -th bit addition.
- Sum bit is serially entered in A .
- If required, next number to be added with former two can be serially entered in B .

Serial Addition

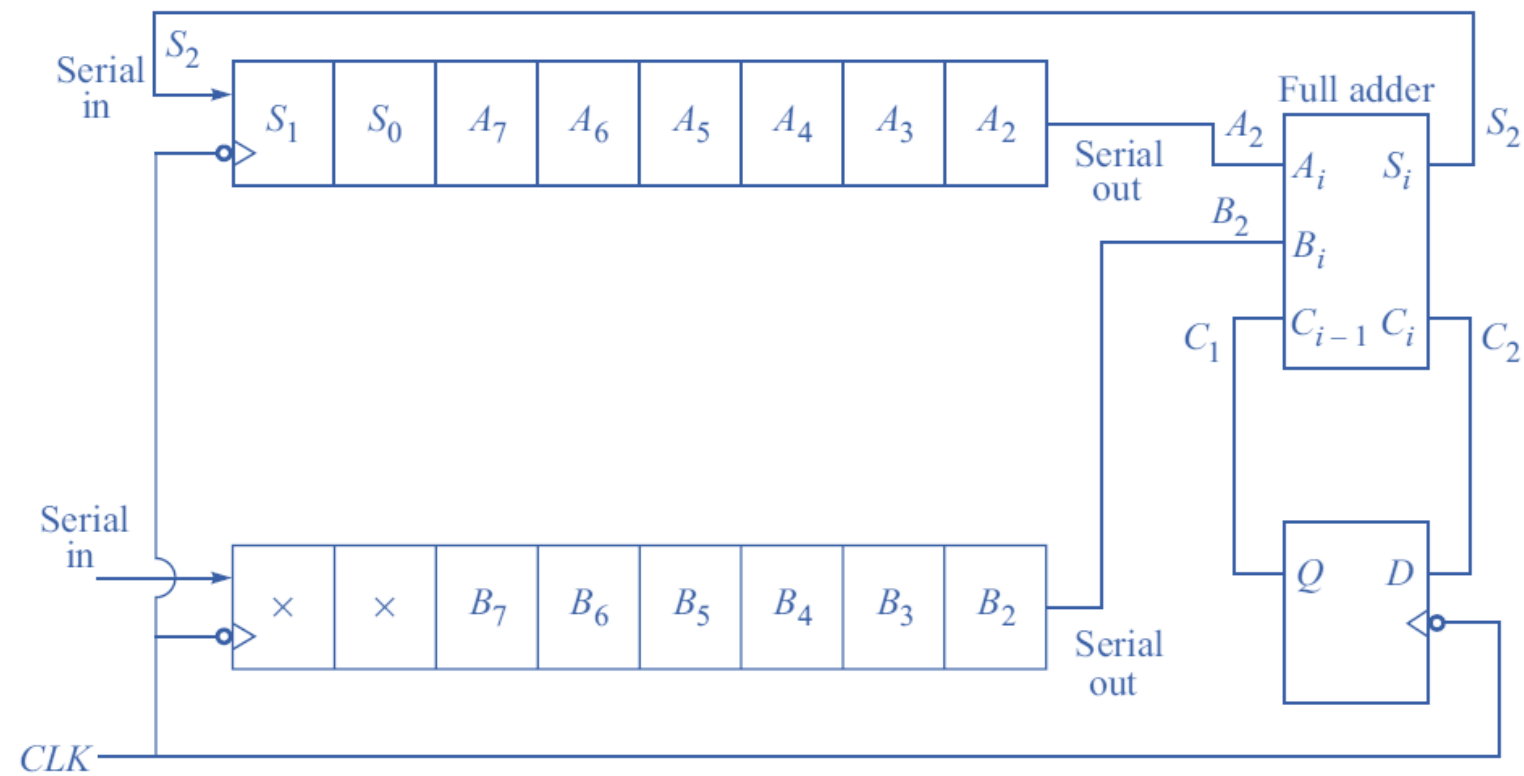

8 clock cycles to complete 8 bit addition

Clock 0: A: 00001010 Q: 0
 B: 00001011


Clock 1: A: 10000101 Q: 0
 B: x0000101

Clock 2: A: 01000010 Q: 1
 B: xx000010

...

x: 0 or 1 depending on next
no., if any, to be added

Serial Multiplication

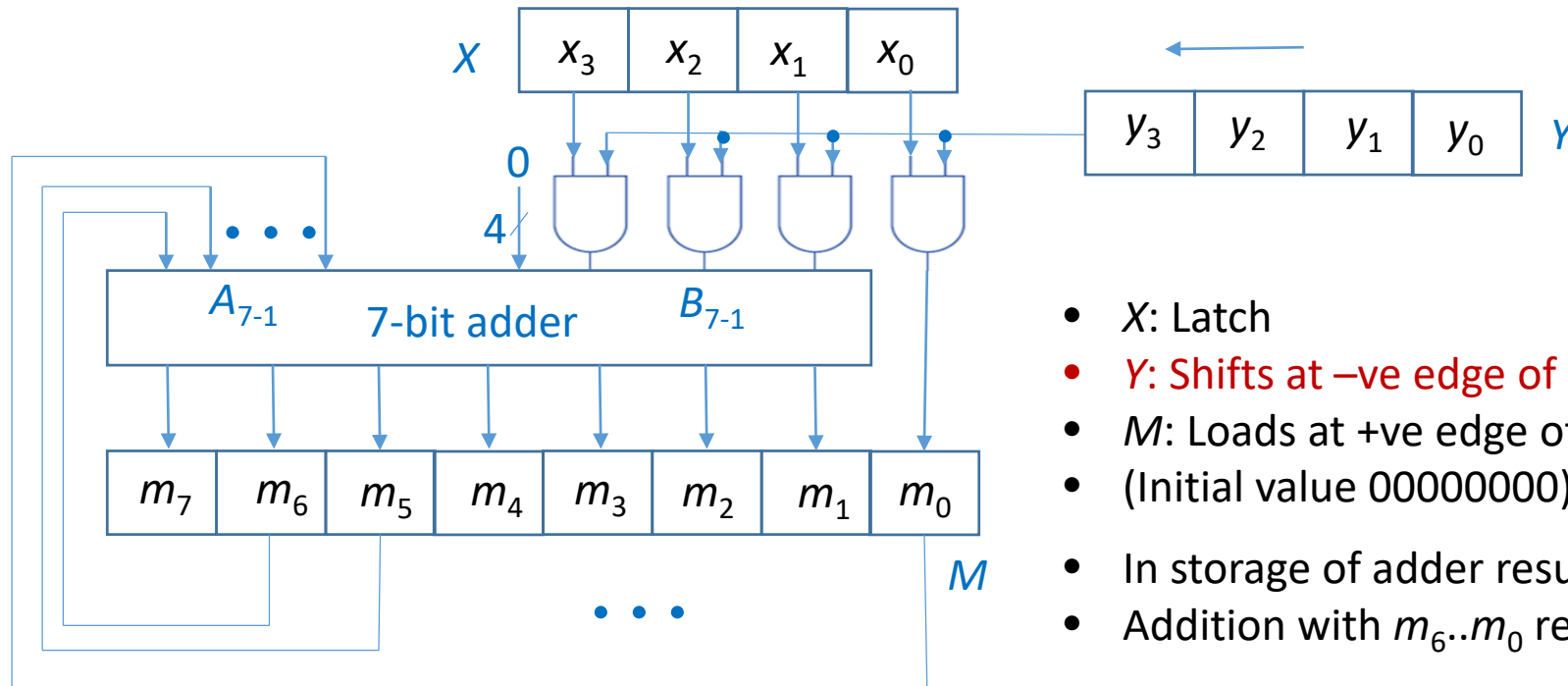

- X : Latch
- Y : Shifts at –ve edge of clock
- M : Loads at +ve edge of clock
- (Initial value 00000000)
- In storage of adder result, one left shift
- Addition with $m_6..m_0$ returns as $m_7..m_1$

$x_3x_2x_1x_0$: 1101


$y_3y_2y_1y_0$: 1011

1101	$(13)_{10}$
1011	$(11)_{10}$
-----	-----
10001111	$(143)_{10}$

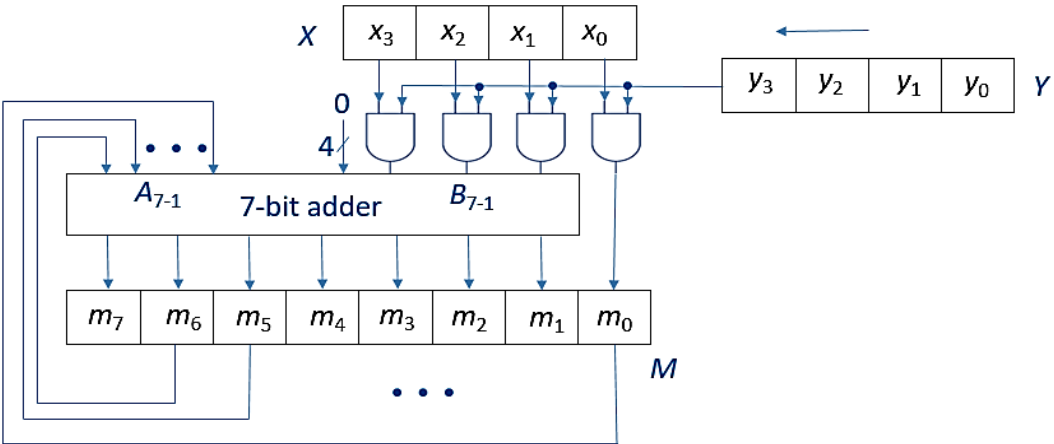Example

$x_3x_2x_1x_0$: 1101
 $y_3y_2y_1y_0$: 1011



$x_3x_2x_1x_0$: 1101
 y_3 : 1 y_2 : 0 ...



AND o/p:	1101	0000	1101	1101
M output:	00000000	00001101	00011010	01000001
M at adder i/p (in blue):	00000000	00011010	00110100	10000010
Other adder i/p (in blue):	00001101	00000000	00001101	00001101

Addition result (in blue):	00001101	00011010	01000001	10001111
M at clock trigger:	00001101	00011010	01000001	10001111
Clock	1	2	3	4

Review: Combinatorial Divider Circuit

 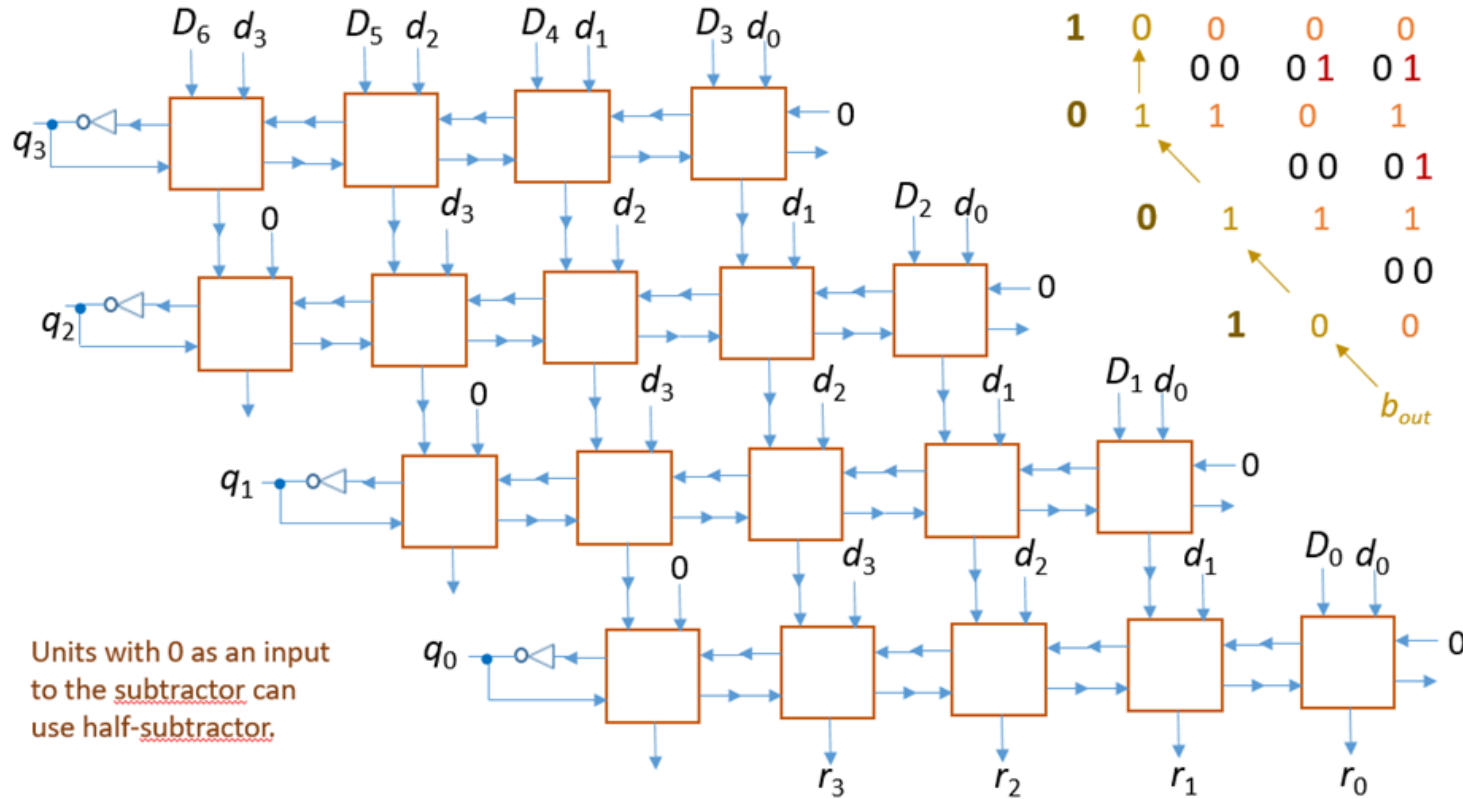


D: 1110101


d: 1101

q: 1001

r: 0000

 

Serial Division

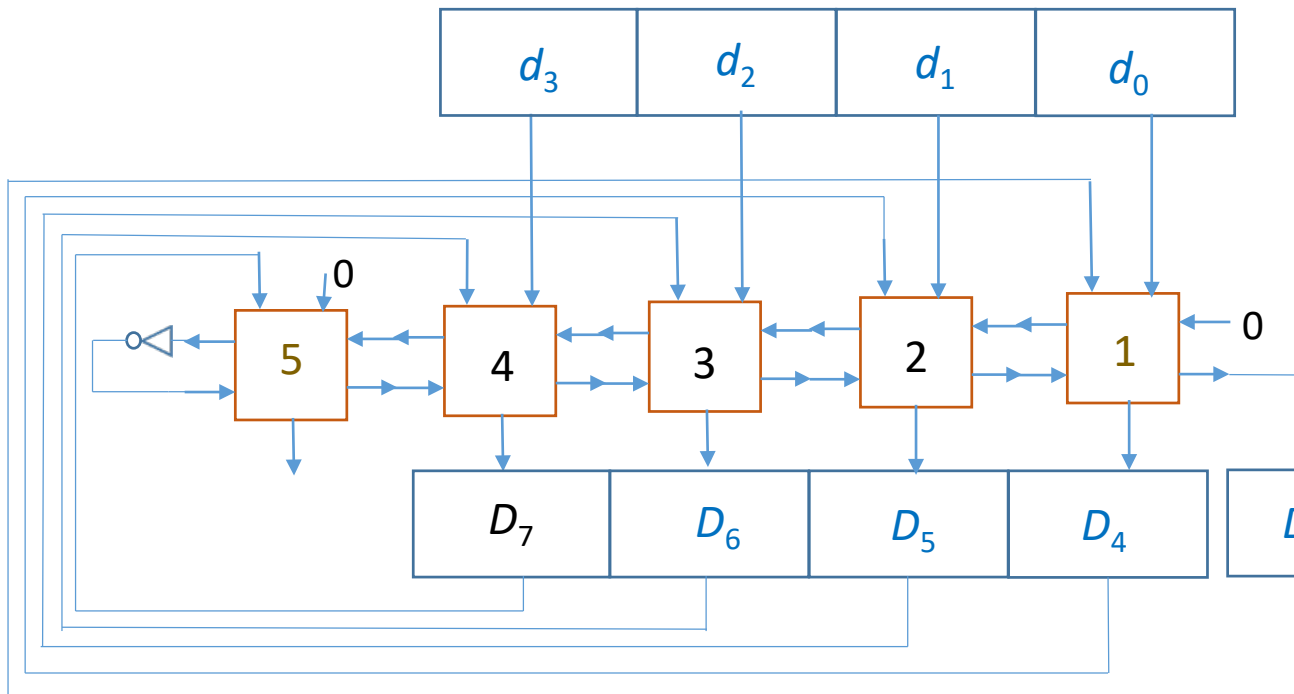


1 and 5 can use
Half-subtractor

$D_6 \dots D_0$: 7-bit dividend
 $d_3 \dots d_0$: 4-bit divisor

$D_7 \dots D_4$: 4-bit register
 $D_3 \dots D_0$: 4-bit shift register
 $d_3 \dots d_0$: 4-bit register

After 4 clock triggers:

 $D_7 \dots D_4$: 4-bit remainder
 $D_3 \dots D_0$: 4-bit quotient



References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ Lloris Ruiz A., Castillo Morales E., Parrilla Roure L., García Ríos A. Number Systems. In: Algebraic Circuits. Intelligent Systems Reference Library, vol 66. Springer, Berlin, Heidelberg