

# **Digital Electronic Circuits**

## **Section 1 (EE, IE)**

### **Lecture 9**


# Minimization and Propagation Delay

A \ BC				
	00	01	11	10
0	0	1	1	0
1	0	0	1	1

Diagram illustrating the Karnaugh map for the function  $Y = A'C + A.B$ . The map shows the prime implicants (P.I.) for the function:

- $A'C$  (Yellow box, covering cells (0,1) and (1,1))
- $A.B$  (Green box, covering cells (0,1) and (1,1))
- $B.C$  (Red box, covering cells (0,1) and (1,0))

 
Truth Table is realized by  
 $Y = A'C + A.B$





$B.C$  : Redundant P.I. Its inclusion increases cost 'unnecessarily'.

In this, effect of propagation delay in logic gates is not considered.

# Propagation Delay in Logic Gate

 

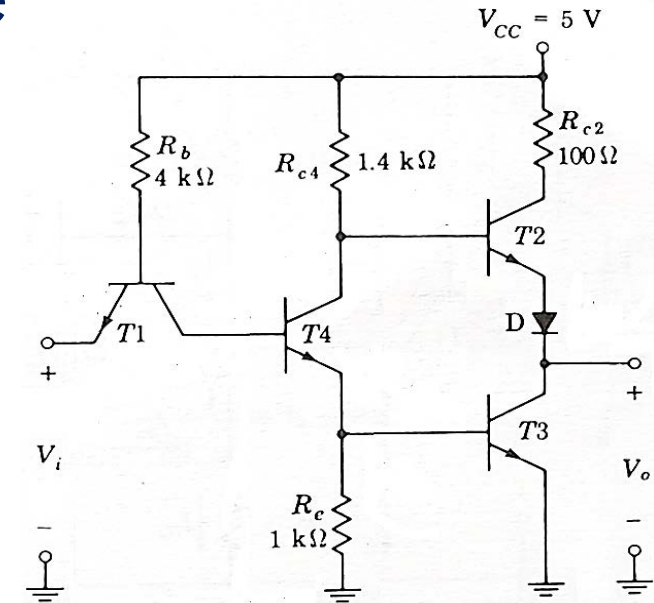 
Logic operations realized by logic gates have finite propagation delay.




Prop. Delay: TTL  $\approx 10 \text{ ns}$   
CMOS  $\approx 50 \text{ ns}$   
(depends on load; also,  
supply voltage for CMOS)
 
# Glitches and Hazards in Logic Circuit

- Glitches are undesired positive or negative going pulse in a digital logic circuit.
- Glitch occurs due to finite propagation delay of logic gates and occurs for specific combinations of input (not for other combinations)
- Glitch is transient in nature and has short duration ( $\approx$  ns).
- A logic circuit has Hazard if there is a potential for glitch.
- A circuit with hazard may generate glitch depending on input combination.



# Example of Glitch

 

$$Y = A'.C + A.B$$

Consider,  $B = 1, C = 1$

$$\begin{aligned}\text{Then, } Y &= A'.1 + 1.A \\ &= A' + A \\ &= 1\end{aligned}$$

i.e.  $Y = 1$ , always  
for  $B = 1, C = 1$   
as per Boolean Algebra

**$B = 1, C = 1, A : 1 \rightarrow 0$**


Glitch occurs: Due to propagation delay of NOT gate, both AND Gates have 0 in one of the inputs for a short duration.

**Glitch:**  $B = 1, C = 1, A : 1 \rightarrow 0$


**No Glitch:**  $B = 1, C = 1, A : 0 \rightarrow 1$

# Static 1 Hazard

$$A' + A = 1$$

 

 In Static 1 Hazard, output should remain static at 1 according to Boolean Logic but glitch occurs under certain conditions.



$\tau_1$  = NOT gate delay

$\tau_2$  = OR gate delay

# Detecting Static 1 Hazard

- Two logically adjacent cells with output 1 in K-Map not covered by a common product term.
- Boolean expression produces  $(A + A')$  for certain condition.

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	0	1	0	0
	1	0	1	1	1

$$Y = B'.C + A.B$$

$$AC = 11, Y = B + B'$$

Glitch,  $ABC : 111 \rightarrow 101$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	0	1	0	1
	1	0	1	0	1

$$Y = B'.C + B.C'$$

No Hazard for one variable changing

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	0	0	0	0
	01	0	0	1	1
	11	1	0	1	1
	10	1	0	0	0

$$Y = B.C + A.C'.D'$$

$$ABD = 110, Y = C + C'$$

Glitch: Static 1 Hazard


$ABCD : 1110 \rightarrow 1100$

# Covering Static 1 Hazard

$BC \backslash A$	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$Y = A'.C + A.B + B.C$$

 **Hazard-free by covering  
with common product term  
(redundant in SOP minimization)**



Hazard-free circuit

$CD \backslash AB$	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	1	0	1	1
10	1	0	0	0

$$Y = B.C + A.C'.D' + A.B.D'$$



## References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ Technical documents from <http://www.ti.com> accessed on Oct. 08, 2018