

# Digital Electronic Circuits

## Section 1 (EE, IE)

### Lecture 20

Class Test 2:


**29-10-2020 (THU):**

**8:00 – 8:55 AM**

**Syllabus:** Logic families (not covered in CT1) and primarily post CT1, shall include concept dealt in pre-CT1 part which forms the pre-requisite.
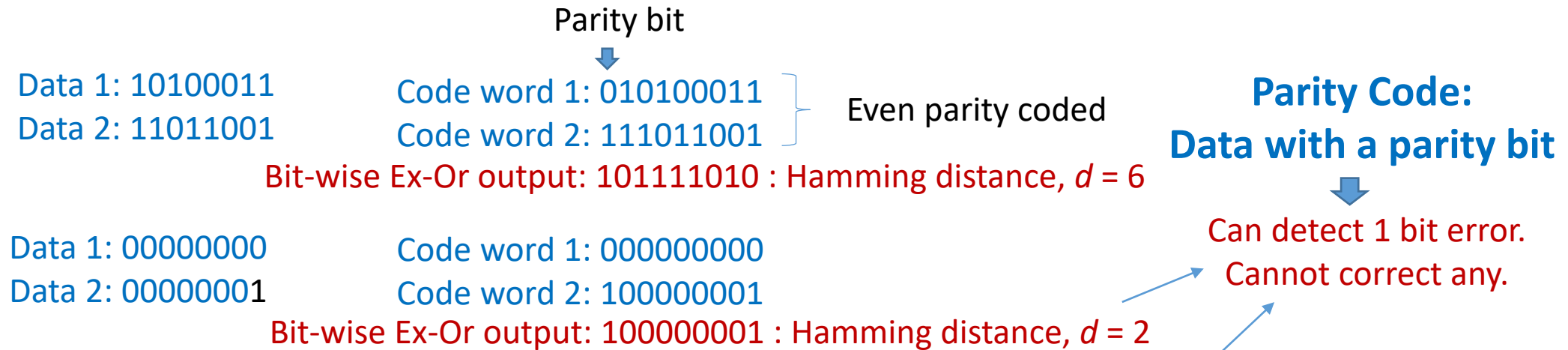
# Hamming Distance and Parity Code

- The number of bit positions by which code words differ is called Hamming distance.
- It can be found by counting number of 1s in bit-wise Ex-OR of two code words.



- To detect  $b$  bit errors, minimum hamming distance,  $d_{min} = b + 1$ .
- To correct  $b$  bit errors, minimum hamming distance,  $d_{min} = 2b + 1$ .

# Hamming Code

- Useful for correcting 1-bit error. It uses more than 1 parity bits.
- Parity bits in the code word are positioned at  $2^i$ -th positions.  
Rest of the positions are filled by data bits.

$2^0$	$2^1$		$2^2$				$2^3$							
P <sub>1</sub>	P <sub>2</sub>	D <sub>3</sub>	P <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	P <sub>8</sub>	D <sub>9</sub>	D <sub>10</sub>	D <sub>11</sub>	D <sub>12</sub>	D <sub>13</sub>	D <sub>14</sub>	D <sub>15</sub>

- If  $m$  parity bits ( $m \geq 2$ ) are used to code  $n$  data bits then,

$$2^m > m + n$$

Parity bits	Max. data bits	Max. total length
2	1	3
3	4	7
4	11	15

# Hamming Code Generation

<b>P<sub>1</sub></b>	<b>P<sub>2</sub></b>	D <sub>3</sub>	<b>P<sub>4</sub></b>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
----------------------	----------------------	----------------	----------------------	----------------	----------------	----------------

Binary coded position    0001   0010   0011   0100   0101   0110   0111

(7,4) Code: Rate = 4/7

$$P_1 = D_3 \oplus D_5 \oplus D_7 \quad : \text{All with 1 in 1's place of position}$$

$$P_2 = D_3 \oplus D_6 \oplus D_7 \quad : \text{All with 1 in 2's place of position}$$

$$P_4 = D_5 \oplus D_6 \oplus D_7 \quad : \text{All with 1 in 4's place of position}$$

Extending:

<b>P<sub>1</sub></b>	<b>P<sub>2</sub></b>	D <sub>3</sub>	<b>P<sub>4</sub></b>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	<b>P<sub>8</sub></b>	D <sub>9</sub>	D <sub>10</sub>	D <sub>11</sub>	D <sub>12</sub>
0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100

$$d_{min} = 3$$

Can detect all 2 bit error.

Can correct all 1 bit error.

$$P_1 = D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} \quad \dots$$

$$P_2 = D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} \quad \dots$$

$$P_4 = D_5 \oplus D_6 \oplus D_7 \oplus D_{12} \quad \dots$$

$$P_8 = D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} \quad : \text{All with 1 in 8's place of position}$$

# Example

Data: 10110101

$P_1$	$P_2$	1	$P_4$	0	1	1	$P_8$	0	1	0	1
0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100

$$P_1 = D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} = 1 \oplus 0 \oplus 1 \oplus 0 \oplus 0 = 0$$

$$P_2 = D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} = 1 \oplus 1 \oplus 1 \oplus 1 \oplus 0 = 0$$

$$P_4 = D_5 \oplus D_6 \oplus D_7 \oplus D_{12} = 0 \oplus 1 \oplus 1 \oplus 1 = 1$$

$$P_8 = D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} = 0 \oplus 1 \oplus 0 \oplus 1 = 0$$

Coded Data: 001101100101

# One bit Error Correction

$$\begin{aligned}
 C_1 &= D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} \oplus P_1 \\
 C_2 &= D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} \oplus P_2 \\
 C_4 &= D_5 \oplus D_6 \oplus D_7 \oplus D_{12} \oplus P_4 \\
 C_8 &= D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} \oplus P_8
 \end{aligned}$$

- If  $C_8C_4C_2C_1 = 0000$  : No error
- Else, it gives position of the error bit  
e.g.  $C_8C_4C_2C_1 = 0111$  means 7<sup>th</sup> bit is erroneously received
- Invert the erroneous bit to correct.

## Example:

**Coded Data:** 001101100101

**Data with** : 001101100111

1-bit error

In 11<sup>th</sup> pos.

$$C_1 = 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$C_2 = 1 \oplus 1 \oplus 1 \oplus 1 \oplus 1 \oplus 0 = 1$$

$$C_4 = 0 \oplus 1 \oplus 1 \oplus 1 \oplus 1 = 0$$

$$C_8 = 0 \oplus 1 \oplus 1 \oplus 1 \oplus 0 = 1$$

1011: 11<sup>th</sup> bit 1 is erroneous  
It is to be made 0 to correct

**Note:** If  $C_8C_4C_2C_1 = 1000$  then 8<sup>th</sup> position bit i.e.  $P_8$  is erroneous.

# Two bit Error Detection

$$C_1 = D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} \oplus P_1$$

$$C_2 = D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} \oplus P_2$$

$$C_4 = D_5 \oplus D_6 \oplus D_7 \oplus D_{12} \oplus P_4$$

$$C_8 = D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} \oplus P_8$$

$$C_8 C_4 C_2 C_1 = 0010$$

$$C_1 = D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} \oplus P_1$$

$$C_2 = D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} \oplus P_2$$

$$C_4 = D_5 \oplus D_6 \oplus D_7 \oplus D_{12} \oplus P_4$$

$$C_8 = D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} \oplus P_8$$

$$C_8 C_4 C_2 C_1 = 0110$$

← Two bits flip

$$C_1 = D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} \oplus P_1$$

$$C_2 = D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} \oplus P_2$$

$$C_4 = D_5 \oplus D_6 \oplus D_7 \oplus D_{12} \oplus P_4$$

$$C_8 = D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} \oplus P_8$$

$$C_8 C_4 C_2 C_1 = 0001$$

$$C_1 = D_3 \oplus D_5 \oplus D_7 \oplus D_9 \oplus D_{11} \oplus P_1$$

$$C_2 = D_3 \oplus D_6 \oplus D_7 \oplus D_{10} \oplus D_{11} \oplus P_2$$

$$C_4 = D_5 \oplus D_6 \oplus D_7 \oplus D_{12} \oplus P_4$$

$$C_8 = D_9 \oplus D_{10} \oplus D_{11} \oplus D_{12} \oplus P_8$$

$$C_8 C_4 C_2 C_1 = 0000$$





← Three bits flip

# **Sequential Logic Circuit**



    
# Bistable Circuit



- A bistable circuit has two stable states.
- Its value changes only by external trigger.
- It can store one bit of information



 Inconvenient  
to apply input  
/ trigger



# SR Latch

  

$S$	$R$	$Q_{last}$	$Q$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	N.A.
1	1	1	N.A.


N.A.: Not allowed

$S$	$R$	$V_2$	$V_3$
1	1	0	0


If  $SR = 00$  follows  $SR = 11$ , then there is a **race** between two gates and depending on who responds faster,  $V_2V_3$  settles at one of 01 or 10.

Latches to prior state

# SR Latch

 


<i>S</i>	<i>R</i>	<i>Q</i> <sup>+</sup>
0	0	<i>Q</i> <sup>-</sup>
0	1	0
1	0	1
1	1	N.A.

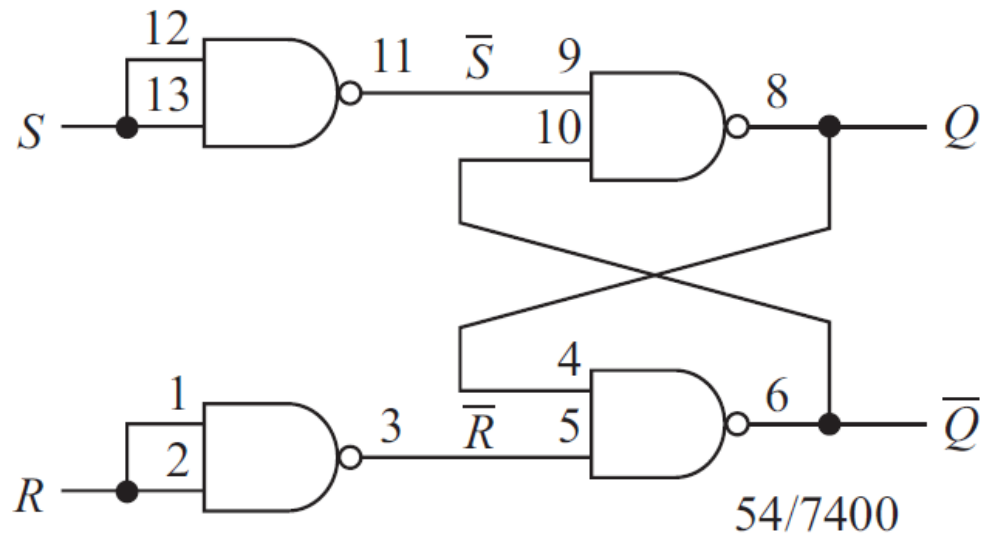

$\bar{S}$	$\bar{R}$	<i>Q</i>
0	0	Forbidden
0	1	1
1	0	0
1	1	Last state

Realizing SR Latch using only NAND gate

# IC 74279

 




$\overline{S}_1$	$\overline{S}_2$	$\overline{R}$	$Q$
0	0	0	Forbidden
0	X	1	1
X	0	1	1
1	1	0	0
1	1	1	Last state

Truth Table of 2 and 3


$\overline{S}_1$	$\overline{R}$	$Q$
0	0	Forbidden
0	1	1
1	0	0
1	1	Last state

Truth Table of 1 and 4

# Debounce Switch

 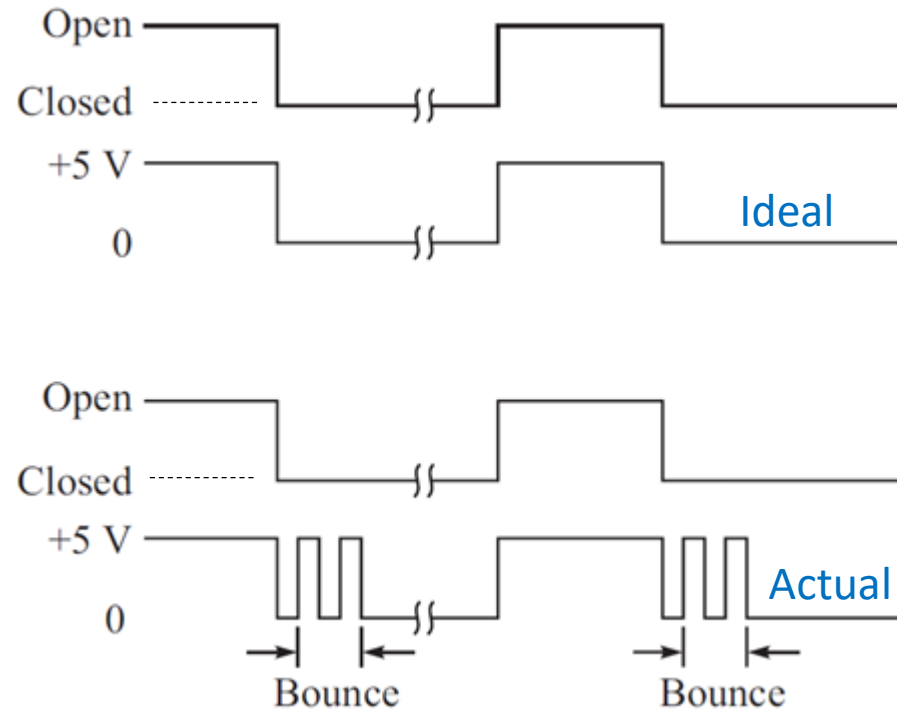
 


# Gated Latch


 


EN	$S$	$R$	$Q_{n+1}$
1	0	0	$Q_n$ (no change)
1	0	1	0
1	1	0	1
1	1	1	Forbidden
0	$X$	$X$	$Q_n$ (no change)

# Gated Latch

 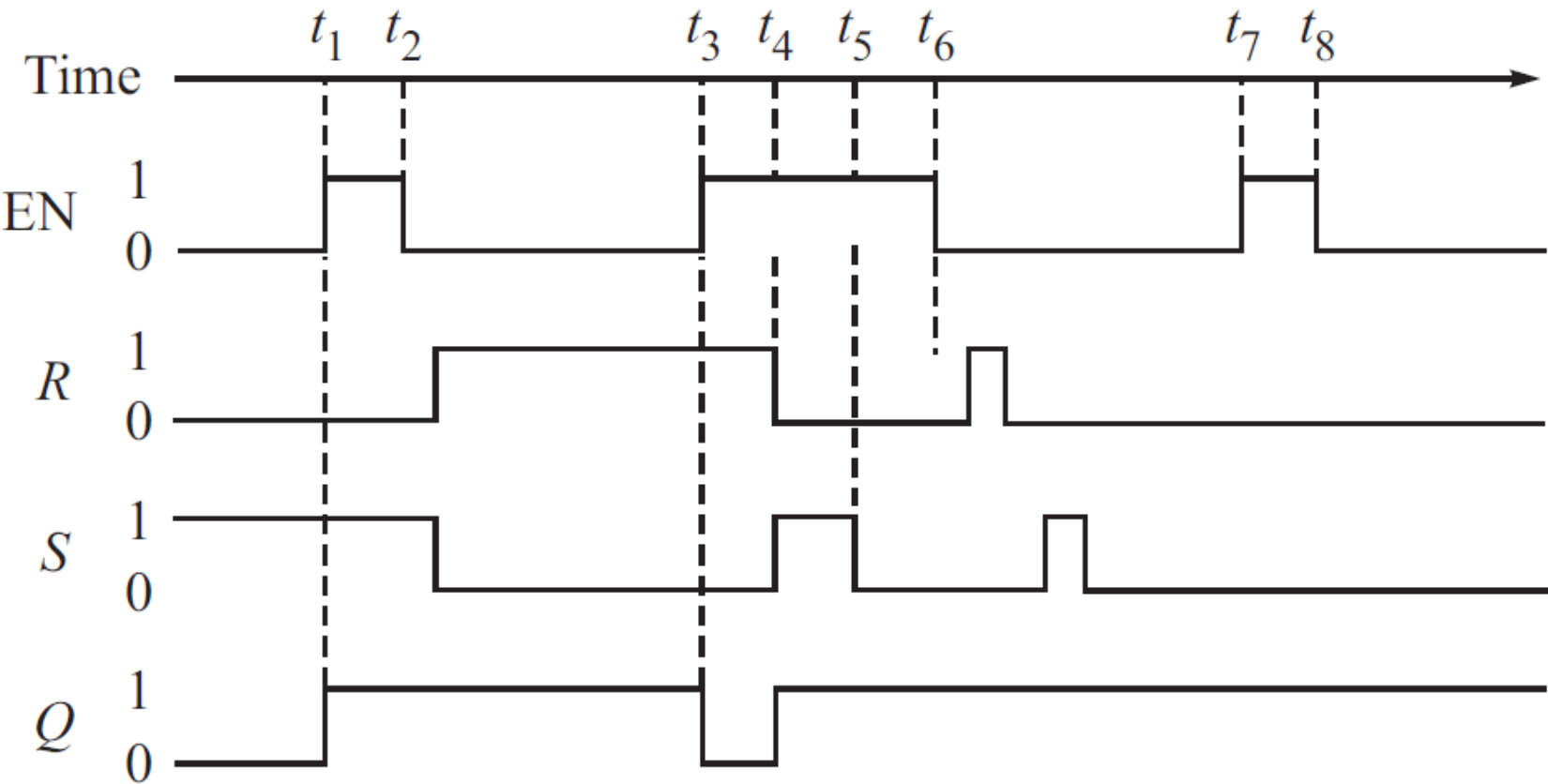


# Clocked *SR* Flip-Flop

  

Usually, Latch with clock / enable input is referred as Flip-Flop.



 When  $C$  is at HIGH level, state can change according to  $SR$  input.




Level-triggered  
*SR* Flip-Flop




 
# Triggering with Narrow Pulse


- Synchronous digital system requires one state change per clock cycle, synchronized with clock.
- More than one state change can occur in level-triggered flip-flop if there is feedback / input changes when clock remains enabled.



  
A very narrow pulse width positive trigger  
(effectively edge-triggered)




# Edge Triggered *SR* Flip-Flop

 

$C$	$S$	$R$	$Q_{n+1}$	Action
↑	0	0	$Q_n$	No change
↑	0	1	0	RESET
↑	1	0	1	SET
↑	1	1	Forbidden	


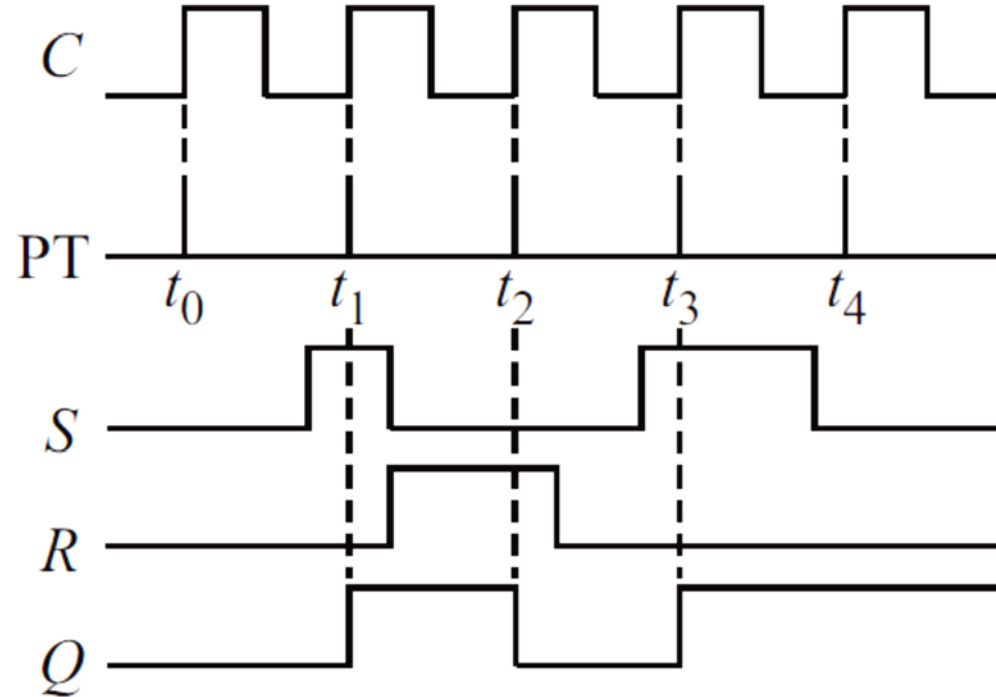


+ve edge triggered SR Flip-Flop

 


-ve edge triggered  
SR Flip-Flop

# *D* Flip-Flop

 
 


## D Flip-Flop with asynchronous preset and clear


$C$	$D$	$Q_{n+1}$
0	$X$	$Q_n$ (last state)
$\uparrow$	0	0
$\uparrow$	1	1

 

# JK Flip-Flop

  


$C$	$J$	$K$	$Q_{n+1}$	Action
↑	0	0	$Q_n$ (last state)	No change
↑	0	1	0	RESET
↑	1	0	1	SET
↑	1	1	$\overline{Q}_n$ (toggle)	Toggle

 

Dual -ve edge triggered JK Flip-Flop with active low PRESET and CLEAR


# Master-Slave Flip-Flop

 

**Master Flip-Flop:** According to type of Flip-Flop i.e. *JK, SR, D*.



**Slave Flip-Flop:** Always *SR* Flip-Flop.

Individually level-triggered, changes in different phases of clock, effectively edge-triggered.


 


**IC 7476**  
*JK* Master-Slave  
with asynch.  
preset and clear


# Edge-Triggering by Input Lockout

  

# Edge-Triggering by Input Lockout

  

# IC 7474

 

IC 7474: Dual +ve edge-triggered D Flip-Flop with asynch. active low preset and clear.

IC 7475 is a Quad D latch with two enables (one each for 2 latch).

IC 7476A: Dual -ve edge triggered JK Flip-Flop with active low PRESET and CLEAR



## References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ Texas Instrument's Digital Logic Pocket Data Book (2007)