

Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 5

Recap.: Shanon's Expansion Theorem

$$F(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot F(0, x_2, x_3, \dots, x_N) + x_1 \cdot F(1, x_2, x_3, \dots, x_N)$$

$$\begin{aligned} F(x_1, x_2, x_3, \dots, x_N) = & x_1' \cdot [x_2' \cdot F(0, 0, x_3, \dots, x_N) + x_2 \cdot F(0, 1, x_3, \dots, x_N)] \\ & + x_1 \cdot [x_2' \cdot F(1, 0, x_3, \dots, x_N) + x_2 \cdot F(1, 1, x_3, \dots, x_N)] \end{aligned}$$



Nesting

$$F(x, y) = x' \cdot F(0, y) + x \cdot F(1, y) = x' \cdot [y' \cdot F(0, 0) + y \cdot F(0, 1)] + x \cdot [y' \cdot F(1, 0) + y \cdot F(1, 1)]$$

$$F(x, y) = x' \cdot y' \cdot F(0, 0) + x' \cdot y \cdot F(0, 1) + x \cdot y' \cdot F(1, 0) + x \cdot y \cdot F(1, 1)$$

Truth Table to Boolean Function: Minterm

$$F(x,y) = x + x'.y$$

x	y	F(x,y)
0	0	0
0	1	1
1	0	1
1	1	1

$$x'.y'$$

$$\Rightarrow x'.y$$

$$\Rightarrow x.y'$$

$$\Rightarrow x.y$$

$$\begin{aligned} F(x,y) &= x'.y'.F(0,0) + x'.y.F(0,1) \\ &\quad + x.y'.F(1,0) + x.y.F(1,1) \\ &= x'.y + x.y' + x.y \end{aligned}$$

- Product term containing all variables of a function (primed, unprimed): *fundamental product* or *standard product* or **minterm**.
- Minterms of $F(x,y)$: $x'.y'$, $x'.y$, $x.y'$, $x.y$ (also designated as m_0 , m_1 , m_2 , m_3 , respectively)
- The minterm designation m_i corresponds to **decimal eqv. of x,y combination** of a row.

$$[\text{Decimal Eqv.} = B_3.2^3 + B_2.2^2 + B_1.2^1 + B_0.2^0]$$

- Boolean function: **Taking OR of minterms** associated with 1 in function output.

Minterm: More Example

x	y	z	minterm	Notation
0	0	0	$x'y'z'$	m_0
0	0	1	$x'y'z$	m_1
0	1	0	$x'yz'$	m_2
0	1	1	$x'yz$	m_3
1	0	0	$xy'z'$	m_4
1	0	1	$xy'z$	m_5
1	1	0	xyz'	m_6
1	1	1	xyz	m_7

$$F(x,y,z) = (x + y).(x + z)$$

x	y	z	$F(x,y,z)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Sum of Product (SOP): Canonical Form

$$F(x,y,z) = x'yz + xy'z' + xy'z + xyz' + xyz$$

$$F(x,y,z) = m_3 + m_4 + m_5 + m_6 + m_7$$

$$F(x,y,z) = \sum m(3,4,5,6,7)$$

Truth Table to Boolean Function: Maxterm

x	y	F(x,y)
0	0	0
0	1	1
1	0	1
1	1	1

⇒ $x + y$

$x + y'$

$x' + y$

$x' + y'$

$$\begin{aligned}
 F(x,y) &= [x' + y' + F(1,1)].[x' + y + F(1,0)] \\
 &\quad .[x + y' + F(0,1)].[x + y + F(0,0)] \\
 &= 1.1.1.(x + y) = x + y
 \end{aligned}$$

- Sum term containing all variables of a function (primed, unprimed): *fundamental sum* or *standard sum* or **Maxterm**.
- Maxterms of $F(x,y)$: $x+y$, $x+y'$, $x'+y$, $x'+y'$ (also designated as M_0 , M_1 , M_2 , M_3 , respectively)
- The Maxterm designation M_i corresponds to **decimal eqv. of x,y combination** of a row.
- Boolean function: **Taking AND of Maxterms** associated with **0** in function output.

$$F(x_1, x_2, x_3, \dots, x_N) = [x_1' + F(1, x_2, x_3, \dots, x_N)].[x_1 + F(0, x_2, x_3, \dots, x_N)]$$

Maxterm: More Example

x	y	z	Maxterm	Notation
0	0	0	$x+y+z$	M_0
0	0	1	$x+y+z'$	M_1
0	1	0	$x+y'+z$	M_2
0	1	1	$x+y'+z'$	M_3
1	0	0	$x'+y+z$	M_4
1	0	1	$x'+y+z'$	M_5
1	1	0	$x'+y'+z$	M_6
1	1	1	$x'+y'+z'$	M_7

$$F(x,y,z) = (x + y).(x + z)$$



x	y	z	$F(x,y,z)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Product of Sum(POS): Canonical Form

$$F(x,y,z) = (x+y+z).(x+y+z') \\ .(x+y'+z)$$

$$F(x,y,z) = M_0.M_1.M_2$$

$$F(x,y,z) = \prod M(0,1,2)$$

More on Canonical Forms

We have seen, (i) $F(x,y) = x + x'.y = \sum m(1,2,3) = \prod M(0)$
and (ii) $F(x,y,z) = (x + y).(x + z) = \sum m(3,4,5,6,7) = \prod M(0,1,2)$

From **example(ii) Truth Table** (T.T.):

$$F'(x,y,z) = \sum m(0,1,2) = m_0 + m_1 + m_2$$

$$F(x,y,z) = (F'(x,y,z))' = (m_0 + m_1 + m_2)' = m_0'.m_1'.m_2' \text{ (De Morgan's Th.)}$$

We already noted, $F(x,y,z) = \prod M(0,1,2) = M_0.M_1.M_2$

Extending to any T.T., $m_i' = M_i$

$$F(x,y) = x + x'.y = x.(y + y') + x'.y = x'.y + x.y' + x.y$$

$$\begin{aligned} F(x,y,z) &= (x + y).(x + z) = (x + y + z.z').(x + z + y.y') \\ &= (x + y + z).(x + y + z').(x + z + y).(x + z + y') \\ &= (x + y + z).(x + y + z').(x + y' + z) \end{aligned}$$


Getting minterms
and Maxterms
algebraically

Conversion between Canonical Forms


Ex. (ii) Truth Table

x	y	z	F(x,y,z)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Two Level Implementation

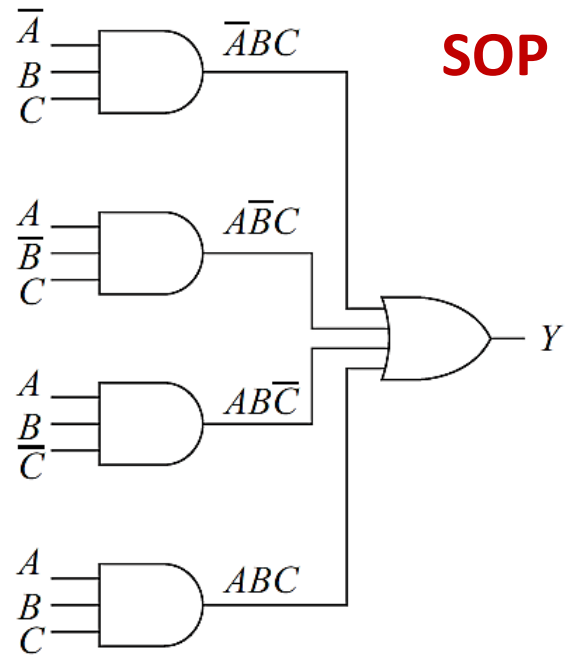


$$Y = F(A,B,C) = \sum m(3,5,6,7)$$

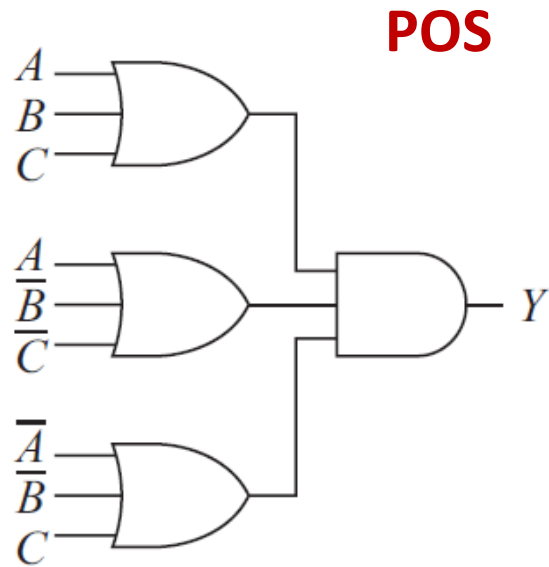

$$Y = F(A,B,C) = \prod M(0,3,6)$$


SOP: 3-level implementation

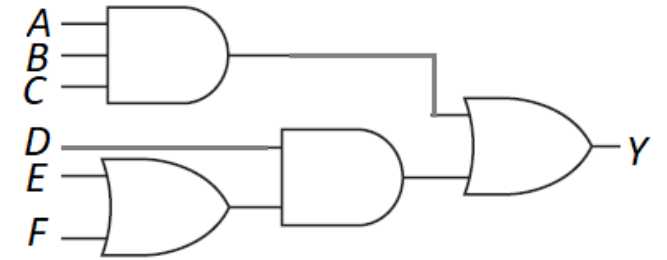

NAND - NAND, NOR - NOR Implementation


$$A.B + C.D + E.F = ((A.B + C.D + E.F)')' \\ = ((A.B)'.(C.D)'.(E.F)')'$$

AND - OR \leftrightarrow NAND - NAND

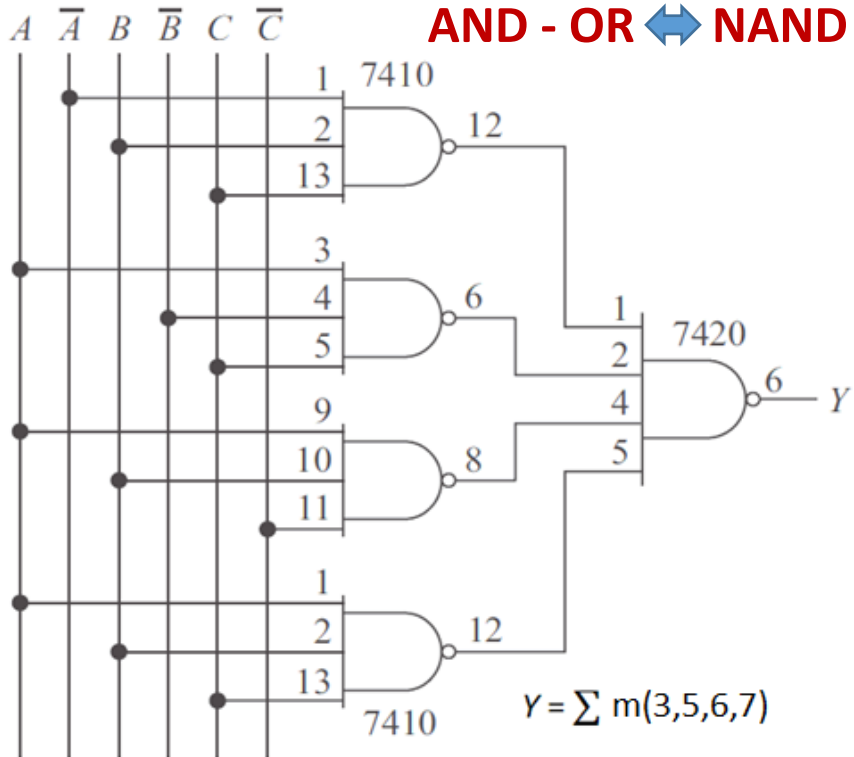


$$(A + B).(C + D).(E + F) = (((A + B).(C + D).(E + F))')' \\ = ((A + B)' + (C + D)' + (E + F)')$$

OR - AND \leftrightarrow NOR - NOR

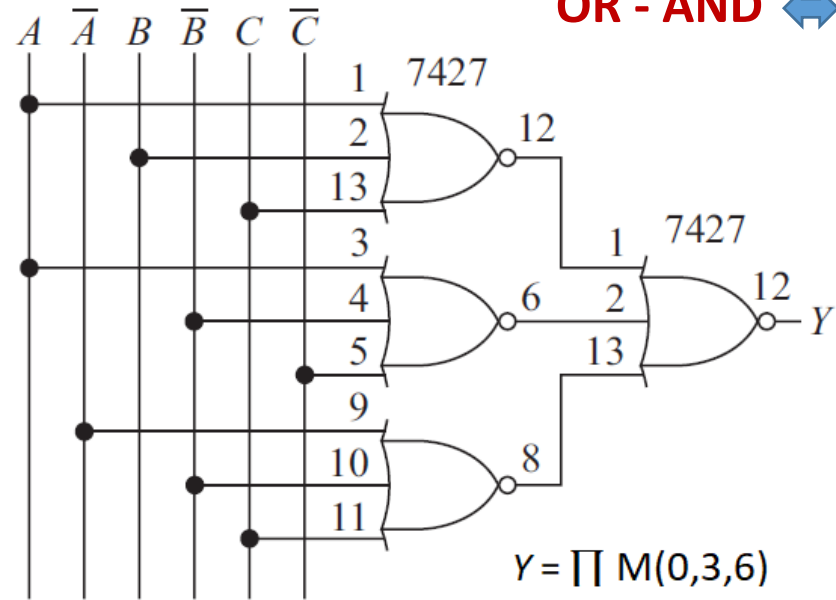

Positive and Negative Logic

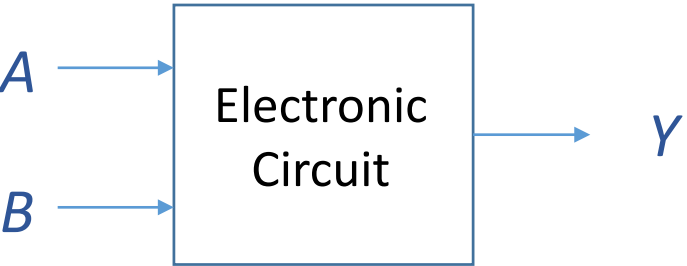

A	B	Y
Low	Low	Low
Low	High	High
High	Low	High
High	High	High

In terms of voltage levels

Positive
Logic
H = 1
L = 0

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

OR

Negative
Logic
H = 0
L = 1

A	B	Y
1	1	1
1	0	0
0	1	0
0	0	0

AND

Positive Logic	Negative Logic
OR	AND
AND	OR
NAND	NOR
NOR	NAND

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ M. Morris Mano, and Michael D. Ciletti, Digital Design 5e, Pearson