

Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 8

Simplest SOP and POS: An Example

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$Y = F(A,B,C)$
 $= \sum m(2,4,5,6,7)$


<i>AB</i> \ <i>C</i>	0	1
00	0	0
01	1	0
11	1	1
10	1	1

$Y = A + B.C'$



<i>AB</i> \ <i>C</i>	0	1
00	0	0
01	1	0
11	1	1
10	1	1

$Y = (A + B).(A + C')$

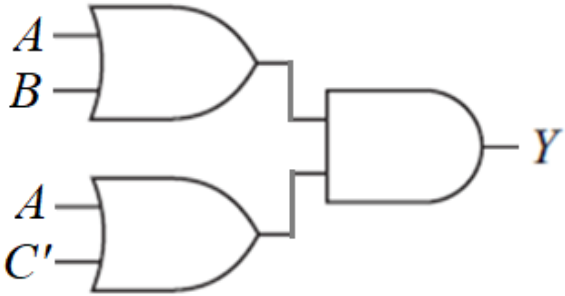

Here, realization of POS is costlier.

Cost Criteria


- **Literal Cost:** The number of times a literal appears in complemented or uncomplemented form (L).
- **Gate Input Cost:** The number of inputs to the gates in the implementation. It may not count NOT gates (G) or it may include NOT gate count (GN).

If the number of terms excluding single variable term is T , and the number of distinct inversions is N , then


$$G = L + T$$

$$GN = L + T + N$$

SOP: 4 Gate inputs: $G = 4$

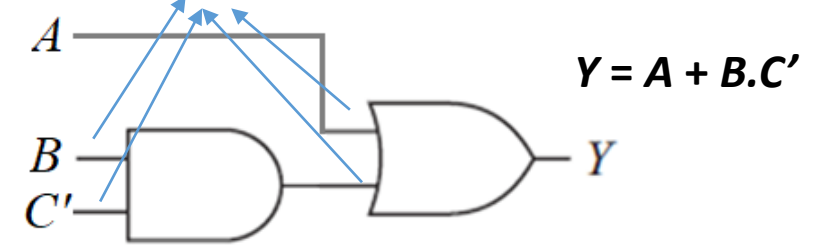

POS: 6 Gate inputs: $G = 6$

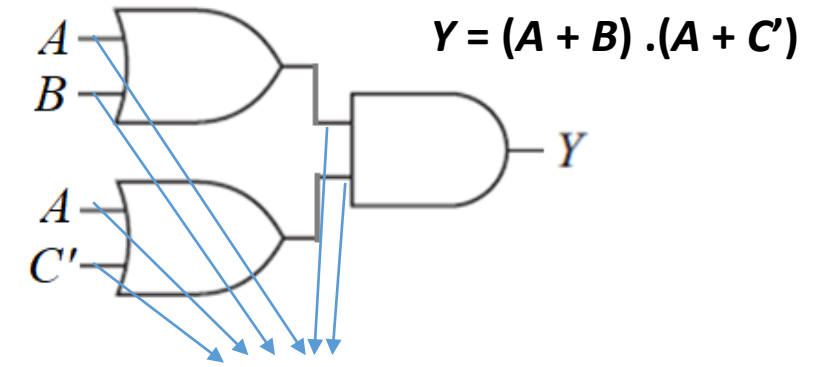

Implementation	L	T	N	G	GN
$Y = A + B.C'$	3	1	1	4	5
$Y = (A + B).(A + C')$	4	2	1	6	7

Cost Criteria: Examples

Implementation	L	T	N	G	GN
$Y = A.B + B.C + C.A$	6	3	0	9	9
$Y = (A+B).(B+C).(C+A)$	6	3	0	9	9
$Y = A.B.C + A'.B'.C'$	6	2	3	8	11
$Y = (A'+B).(B'+C).(C'+A)$	6	3	3	9	12
$Y = A.B + B'.C.D + A'.B'.D + B.C'.D$	11	4	3	15	18
$Y = (A+C').(A+D).(B'+C'+D).(B+C+D')$	10	4	3	14	17



Considered: 2-Level implementation, no restriction in fan-in or kind of logic gates to be used (as in K-Map, QM simplification)

Implementation using only 2-input NAND gate: An Example

$$Y = A.B + C.D.E = ((A.B)'.(C.D.E)')' = ((A.B)'.'(C.D)'.E)')'$$



Cost: 5 Units
(10 Gate inputs)

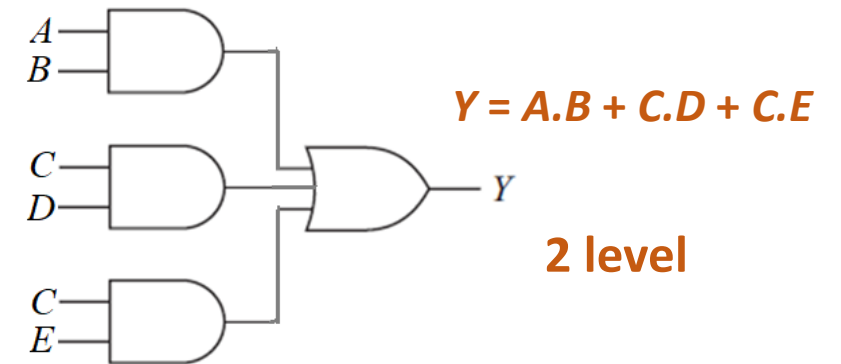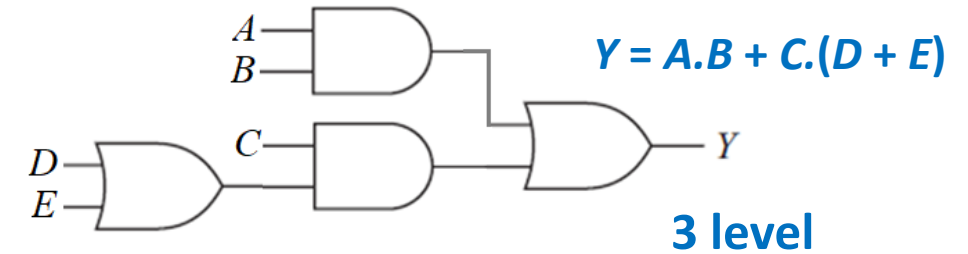

Total Cost (TC)
= No. of gate i/p
+ No. of gates

Multiple Output Minimization

Common P.I.

A \ BC				
	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$$F_1 = B'.C + A.B$$

Individual
implementation

$$G = 6 \times 2 = 12$$

$$TC = 12 + 3 \times 2 = 18$$




A \ BC				
	00	01	11	10
0	0	1	1	1
1	0	1	0	0

Using common P.I.

$$G = 6 + 4 = 10$$

$$TC = 10 + 3 + 2 = 15$$

$$F_2 = B'.C + A'.B$$

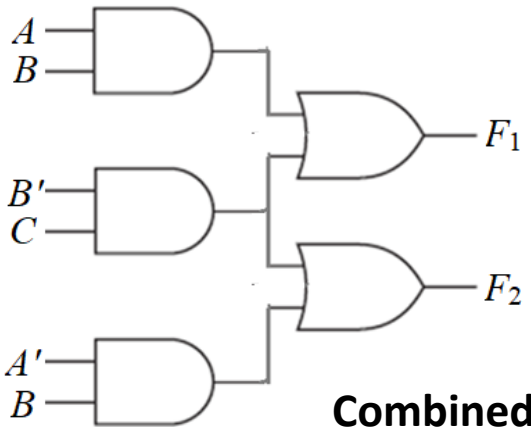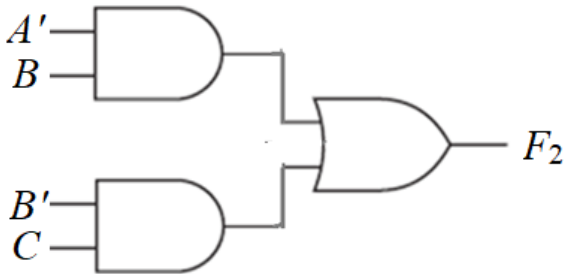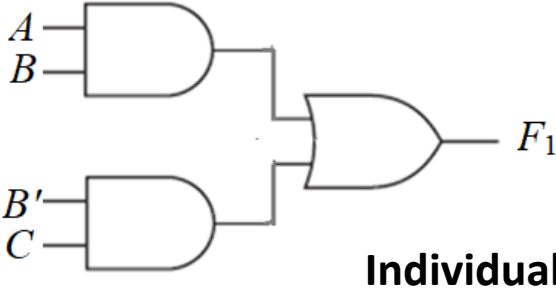

Multiple Output Minimization

Common term need
to be generated

BC	00	01	11	10
A				
0	1	1	1	0
1	0	0	0	0

$$F_1 = \sum m(0,1,3) \\ = A'.B' + A'.C$$

Individual
implementation

$$G = 6 + 8 = 14$$

$$TC = 14 + 3 + 3 = 20$$

$$F_2 = \sum m(3,6) \\ = A'.B.C + A.B.C'$$

BC	00	01	11	10
A				
0	0	0	1	0
1	0	0	0	1

BC	00	01	11	10
A				
0	1	1	1	0
1	0	0	0	0

$$F_1 = A'.B' + A'.B.C$$

$$F_2 = A'.B.C + A.B.C'$$

Combined

$$G = 7 + 5 = 12$$

$$TC = 12 + 3 + 2 = 17$$

Multiple Output Minimization

BC	00	01	11	10
A				
0	1	1	1	0
1	0	0	0	0

$$F_1 = \sum m(0,1,3) \\ = A'.B' + A'.C$$

Individual
implementation
 $G = 6 + 2 = 8$
 $TC = 8 + 3 + 1 = 12$

BC	00	01	11	10
A				
0	0	0	1	0
1	0	0	1	0

$$F_2 = \sum m(3,7) \\ = B.C$$

Individual: Less cost

BC	00	01	11	10
A				
0	1	1	1	0
1	0	0	0	0

BC	00	01	11	10
A				
0	0	0	1	0
1	0	0	1	0

Common term part of
individual bigger group

$$F_1 = A'.B' + A'.B.C$$

$$F_2 = A'.B.C + A.B.C$$

$$G = 7 + 5 = 12 \\ TC = 12 + 3 + 2 \\ = 17$$

Multiple Output Minimization

Common term part of
bigger group in which other
members already covered

AB \ CD	CD			
	00	01	11	10
00	0	0	1	1
01	1	1	1	0
11	1	1	1	0
10	0	0	0	0

 Individual Minimization

$$F_1 = B.C' + B.D + A'.B'.C$$

$$F_2 = B.D' + B.C + A.B'.D$$

AB \ CD	CD			
	00	01	11	10
00	0	0	0	0
01	1	0	1	1
11	1	0	1	1
10	0	1	1	0

 Combined Minimization

$$F_1 = B.C' + B.C.D + A'.B'.C$$

$$F_2 = B.D' + B.C.D + A.B'.D$$

Individual

$$G = 10 + 10 = 20$$

$$TC = 20 + 4 + 4 = 28$$

Combined

$$G = 11 + 8 = 19$$

$$TC = 19 + 4 + 3 = 26$$

Any 3rd option?

Multiple Output Minimization

Use of Don't Care

AB \ CD				
	00	01	11	10
00	0	0	1	1
01	X	1	1	0
11	X	1	1	0
10	0	0	0	0

$$F_1 = B.D + A'.B'.C$$

$$F_2 = B.C + A.B'.D$$

AB \ CD				
	00	01	11	10
00	0	0	0	0
01	X	0	1	1
11	X	0	1	1
10	0	1	1	0

$$G = 7 + 7 = 14$$

$$TC = 14 + 3 + 3 = 20$$

AB \ CD				
	00	01	11	10
00	0	0	1	1
01	X	X	1	0
11	1	X	1	0
10	0	0	0	0

$$F_1 = B.C'.D' + B.C.D + A'.B'.C$$

$$F_2 = B.C'.D' + B.C.D + A.B'.D$$

$$G = 12 + 6 = 18$$

$$TC = 18 + 4 + 2 = 24$$

AB \ CD				
	00	01	11	10
00	0	0	0	0
01	1	0	1	X
11	X	0	1	X
10	0	1	1	0

Individual

$$G = 20, TC = 28$$

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill