

# Digital Electronic Circuits

## Section 1 (EE, IE)

### Lecture 17


**Class Test 2:**

27-10-2020 (TUE): Starting 10:15 AM  
(as was suggested by students, this is additional holiday after Dusserah as per institute holiday list)


**Syllabus:** Logic families (not covered in CT1) and primarily post CT1, shall include concept dealt in pre-CT1 part which forms the pre-requisite.

# Binary Coded Decimal (BCD)

 - 0: 0000
- 1: 0001
- 2: 0010
- 3: 0011
- 4: 0100
- 5: 0101
- 6: 0110
- 7: 0111
- 8: 1000
- 9: 1001



Decimal	BCD
10	0001 0000
11	0001 0001
99	1001 1001
100	0001 0000 0000
101	0001 0000 0001
487	0100 1000 0111
...	...

 

# Addition of BCD

- Result is valid BCD when 4-bit sum is less than or equal to 9.

```

0101
0010
-----
0111
  ↓
  7

```

```

0011
0110
-----
1001
  ↓
  9

```

Binary addition

```

      A3A2A1A0
      B3B2B1B0
      -----
C3 S3S2S1S0

```

- Result is not valid when 4-bit sum is more than 9. Addition of 6 gives valid BCD.

```

0100      1011
0111      0110
-----
1011
  ↓
Not valid BCD

(000)1 0001
  ↓    ↓
  1    1

```

```

1001      (000)1 0001
1000      0110
-----
(000)1 0001
  ↓    ↓
  1    1

(000)1 0111
  ↓    ↓
  1    7

```

# Logic for Addition of 6

Decimal result	$C_3$	$S_3$	$S_2$	$S_1$	$S_0$	$Y$ (Add 6)
0 - 9	--	--	--	--	--	0
10	0	1	0	1	0	1
11	0	1	0	1	1	1
12	0	1	1	0	0	1
13	0	1	1	0	1	1
14	0	1	1	1	0	1
15	0	1	1	1	1	1
16	1	0	0	0	0	1
17	1	0	0	0	1	1
18	1	0	0	1	0	1

BCD Addition result is between 0 and 18.

$Y = 1$  when Addition of 6 is needed

$Y = 1$  when addition result is between 10 and 18.

i.e.  $C_3S_3S_2S_1S_0$  : 01010 to 10010

$Y = 0$  when  $C_3S_3S_2S_1S_0$  : 00000 to 01001


$Y = X$  (don't care) when  $C_3S_3S_2S_1S_0 > 10010$

This Truth Table on simplification gives

$$Y = C_3 + S_3S_2 + S_3S_1$$

# BCD Adder Unit

49	0100	1001
+ 58	0101	1000
	-----	
	1 0001	
	0110	
	-----	
	1010	0111
	0110	
	-----	
(000)1	0000	0111
↓	↓	↓
1	0	7

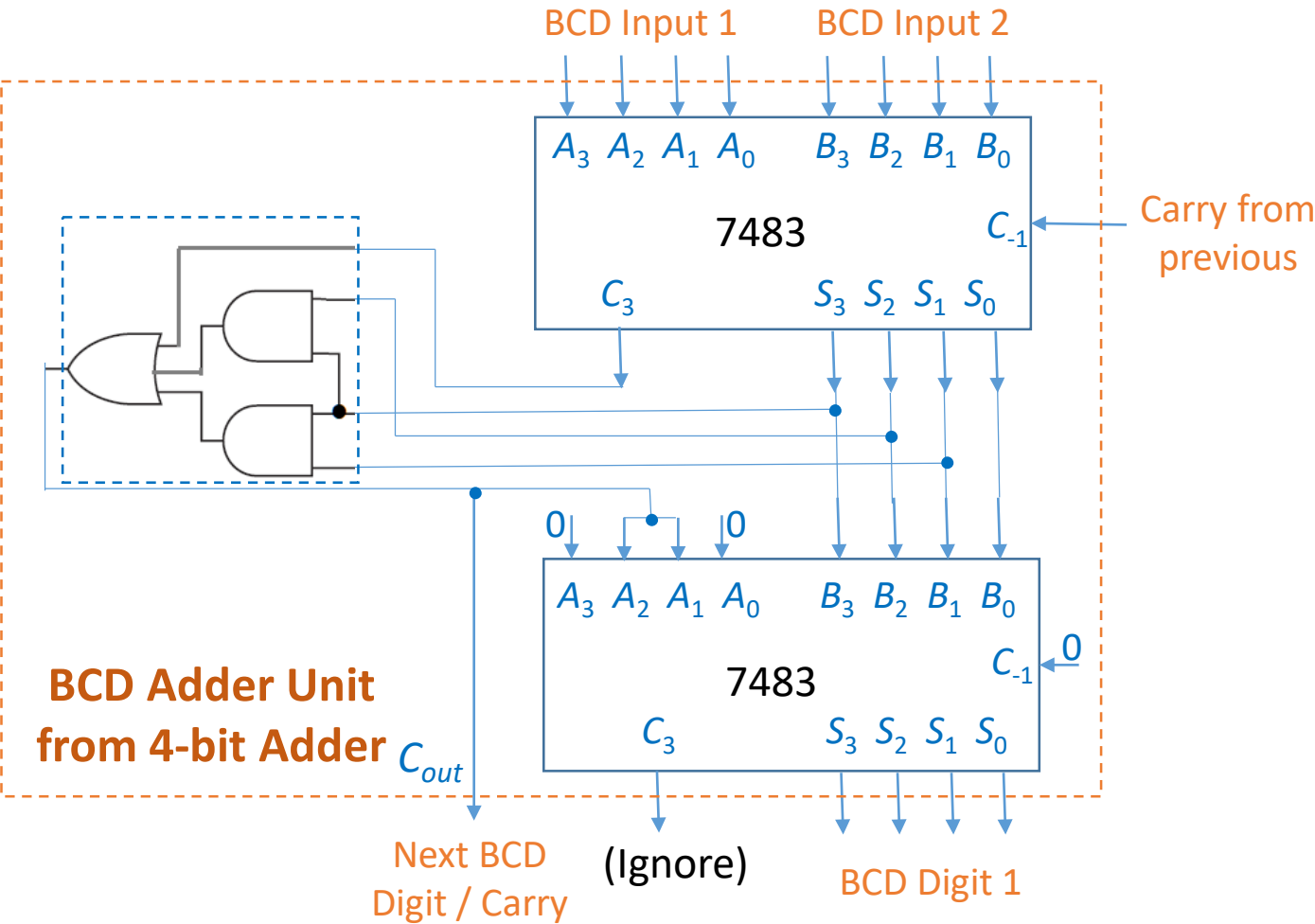

# BCD Subtraction

## Subtraction using 10's C: Decimal

(Similar to 2's C subtraction in binary)

**Smaller from larger:**  $7 - 4$

10's C of 4 =  $10 - 4 = 6$

$7 + 6 = 13$

Carry present: Result +ve

Ignore carry

Difference = 3 (+ve)

**Larger from smaller:**  $4 - 7$


10's C of 7 =  $10 - 7 = 3$

$4 + 3 = 7$

Carry absent: Result -ve

Difference = 10's C of 7 (-ve)

=  $10 - 7 = 3$  (-ve)

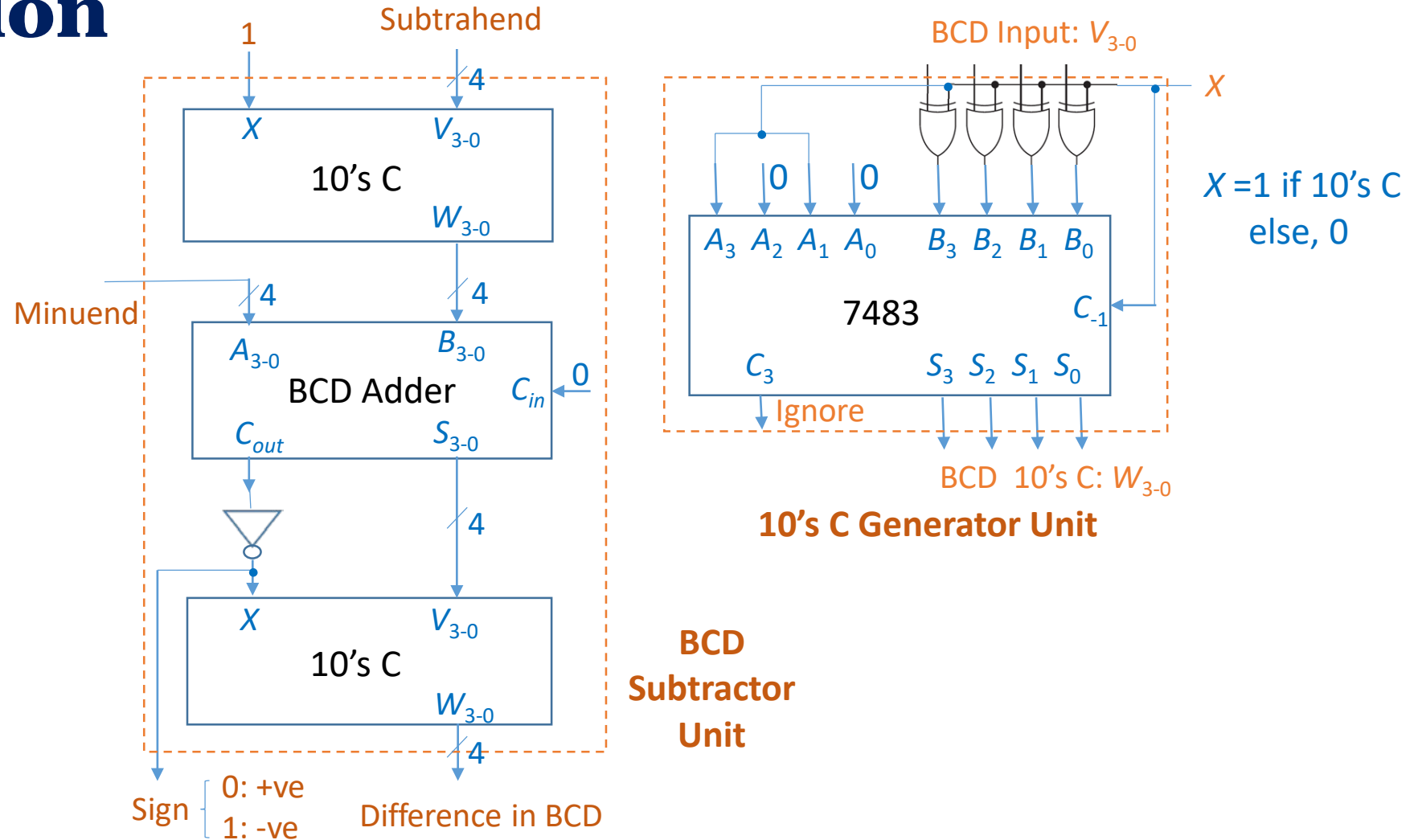

# 9's Complement and 1's Complement

## Decimal Subtraction using 9's C:

**Smaller from larger:**  $7 - 4$

9's C of 4 =  $9 - 4 = 5$

$7 + 5 = 12$

Carry present: Result +ve

Add carry to get result

Difference =  $2 + 1 = 3$  (+ve)

**Larger from smaller:**  $4 - 7$

9's C of 7 =  $9 - 7 = 2$

$4 + 2 = 6$

Carry absent: Result -ve

Difference = 9's C of 6 (-ve)  
=  $9 - 6 = 3$  (-ve)

## Binary Subtraction using 1's C:

**Smaller from larger:**  $0111 - 0100$

1's C of 0100 = 1011

$0111 + 1011 = 10010$

Carry present: Result +ve

Add carry to get result

Difference =  $0010 + 1 = 0011$  (+ve)

**Larger from smaller:**  $0100 - 0111$

1's C of 0111 = 1000

$0100 + 1000 = 1100$

Carry absent: Result -ve

Difference = 1's C of 1100 (-ve)  
= 0011 (-ve)

# Subtraction Revisited

0000 :	0	1000 :	-8
0001 :	1	1001 :	-7
0010 :	2	1010 :	-6
0011 :	3	1011 :	-5
0100 :	4	1100 :	-4
0101 :	5	1101 :	-3
0110 :	6	1110 :	-2
0111 :	7	1111 :	-1

Range: -8 to +7

0111 (7)  
1110 (-2)  
-----  
 $\pm$  0101 (5)

0011 (3)  
1101 (-3)  
-----  
 $\pm$  0000 (0)


0010 (2)  
1001 (-7)  
-----  
1011 (-5)

$$\begin{array}{r} A_3A_2A_1A_0 \\ B_3B_2B_1B_0 \\ \hline [C_3] \ S_3S_2S_1S_0 \end{array}$$


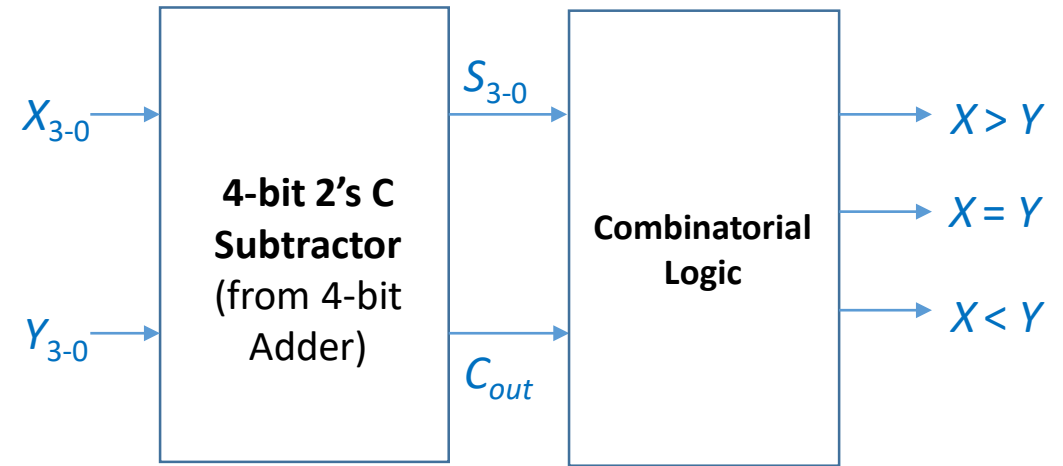
# Magnitude Comparison by Subtraction

- Magnitude comparison finds if (i) one number is same as the other number (identity / equality) or (ii) greater / smaller than the other number.
- An adder circuit performing 2's C subtraction ( $X - Y$ ) can be used for this.
  - If  $X = Y$  and  $X > Y$  then  $C_{out} = 1$ .  
If  $C_{out} = 0$ , then  $X < Y$ .
  - if  $C_{out}$  is 1 and any of  $S_i = 1$  then  $X > Y$ , else  $X = Y$ .



$$(X < Y) = C_{out}'$$


$$(X = Y) = C_{out} \cdot S_3' \cdot S_2' \cdot S_1' \cdot S_0'$$

$$(X > Y) = C_{out} \cdot (S_3 + S_2 + S_1 + S_0)$$

# 1-bit Magnitude Comparison

- Magnitude comparison can be done without generating addition / subtraction result.

Input		Output		
X	Y	$X > Y$	$X = Y$	$X < Y$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

 

$$(X > Y): G = X.Y'$$

$$(X = Y): E = X'.Y' + X.Y$$

$$(X < Y): L = X'.Y$$

(If NAND gate is not used, two NOT gates will be required to get  $X'$  and  $Y'$ )

$$\begin{aligned} X'.Y' + X.Y &= (X' + Y).(X + Y') \\ &= (X.Y')'.(X'.Y)' \\ &= [(X.Y') + (X'.Y)]' \end{aligned}$$

# 2-bit Magnitude Comparison

Numbers to be compared:  $X$ :  $X_1X_0$  and  $Y$ :  $Y_1Y_0$

Define:

$$G_0 = X_0.Y_0'$$

$$E_0 = X_0'.Y_0' + X_0.Y_0$$

$$L_0 = X_0'.Y_0$$

$$G_1 = X_1.Y_1'$$

$$E_1 = X_1'.Y_1' + X_1.Y_1$$

$$L_1 = X_1'.Y_1$$

$X > Y$ :

- If  $X_1 > Y_1$
- If  $X_1 = Y_1$  and  $X_0 > Y_0$

$$(X > Y) = G_1 + E_1G_0$$

$X = Y$ :


- If  $X_1 = Y_1$  and  $X_0 = Y_0$

$$(X = Y) = E_1.E_0$$

$X < Y$ :

- If  $X_1 < Y_1$
- If  $X_1 = Y_1$  and  $X_0 < Y_0$

$$(X < Y) = L_1 + E_1L_0$$

 

Other than two 1-bit comparators, a logic circuit to generate final outputs.

# ***n*-bit Magnitude Comparison**

Numbers to be compared: ***X*** :  $X_{n-1}X_{n-2} \dots X_1X_0$  and ***Y*** :  $Y_{n-1}Y_{n-2} \dots Y_1Y_0$

$$(X > Y) = G_{n-1} + E_{n-1}G_{n-2} + E_{n-1}E_{n-2}G_{n-3} + \dots + E_{n-1}E_{n-2} \dots E_1G_0$$

$$(X = Y) = E_{n-1}E_{n-2} \dots E_1E_0$$

$$(X < Y) = L_{n-1} + E_{n-1}L_{n-2} + E_{n-1}E_{n-2}L_{n-3} + \dots + E_{n-1}E_{n-2} \dots E_1L_0$$



With cascading inputs coming from another block with lower significant bits:

$$(X > Y)_{\text{out}} = G_{n-1} + E_{n-1}G_{n-2} + \dots + E_{n-1}E_{n-2} \dots E_1G_0 + E_{n-1}E_{n-2} \dots E_0 \cdot (X > Y)_{\text{in}}$$

$$(X = Y)_{\text{out}} = E_{n-1}E_{n-2} \dots E_1E_0 \cdot (X = Y)_{\text{in}}$$


$$(X < Y)_{\text{out}} = L_{n-1} + E_{n-1}L_{n-2} + \dots + E_{n-1}E_{n-2} \dots E_1L_0 + E_{n-1}E_{n-2} \dots E_0 \cdot (X < Y)_{\text{in}}$$

# 4-bit Comparator IC

 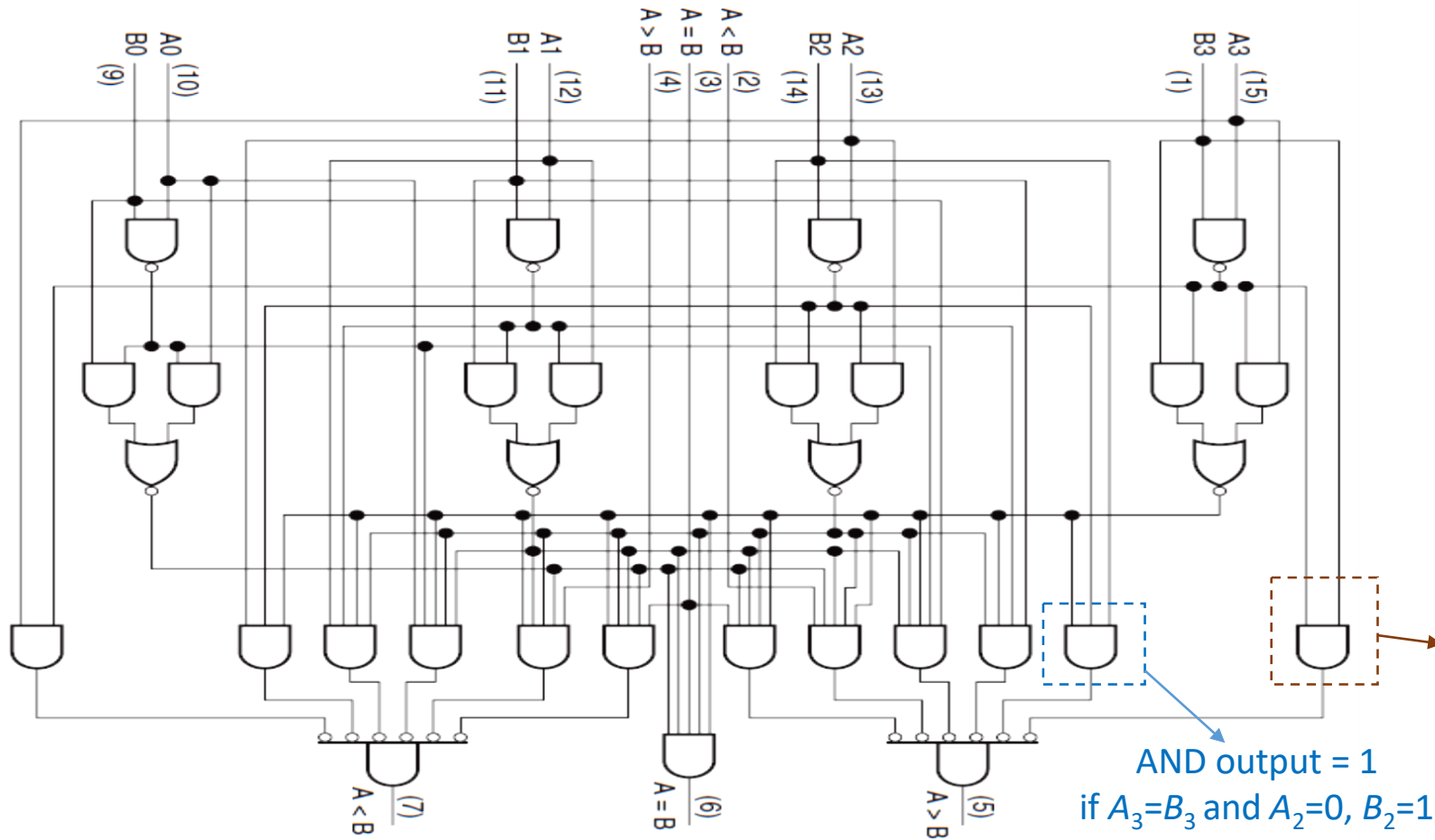


# IC 7485 Function Table

COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A3, B3	A2, B2	A1, B1	A0, B0	A>B	A<B	A=B	A>B	A<B	A=B
A3>B3	X	X	X	X	X	X	H	L	L
A3<B3	X	X	X	X	X	X	L	H	L
A3=B3	A2>B2	X	X	X	X	X	H	L	L
A3=B3	A2<B2	X	X	X	X	X	L	H	L
A3=B3	A2=B2	A1>B1	X	X	X	X	H	L	L
A3=B3	A2=B2	A1<B1	X	X	X	X	L	H	L
A3=B3	A2=B2	A1=B1	A0>B0	X	X	X	H	L	L
A3=B3	A2=B2	A1=B1	A0<B0	X	X	X	L	H	L
A3=B3	A2=B2	A1=B1	A0=B0	H	L	L	H	L	L
A3=B3	A2=B2	A1=B1	A0=B0	L	H	L	L	H	L
A3=B3	A2=B2	A1=B1	A0=B0	H	H	L	L	L	L
A3=B3	A2=B2	A1=B1	A0=B0	L	L	L	H	H	L
A3=B3	A2=B2	A1=B1	A0=B0	X	X	H	L	L	H

 


# Cascaded Comparison

## 8-bit comparison

 


Here, generation of comparator output of one stage delays the output generation of next stage to which it is fed.

## 24-bit comparison

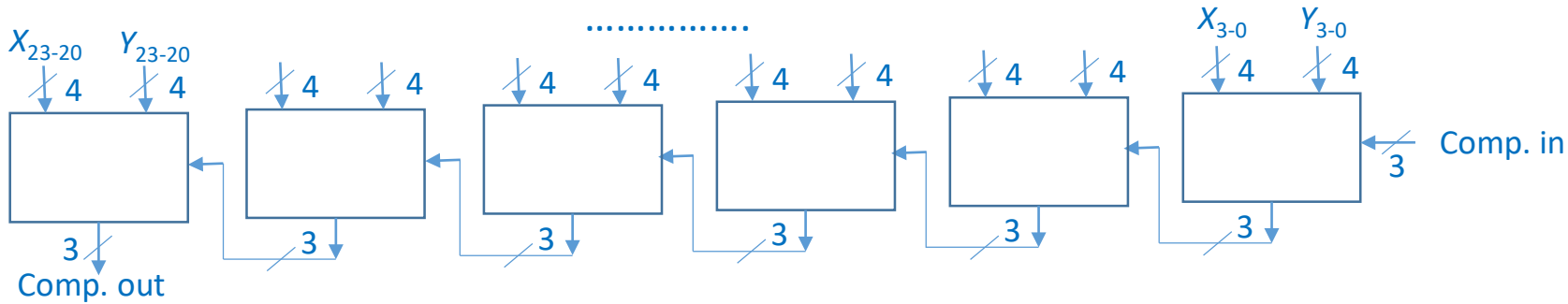

# Multi-level Comparison

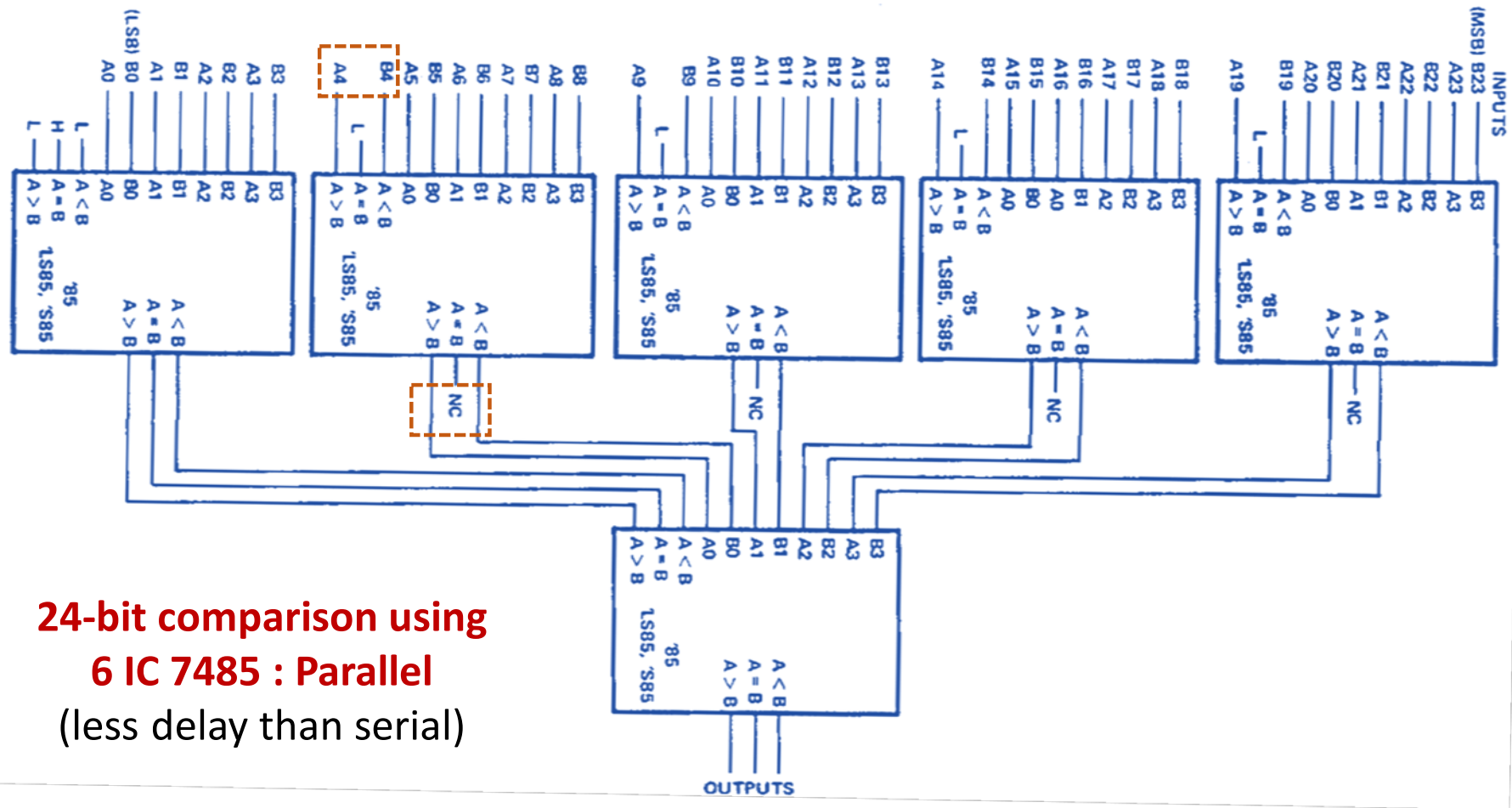

24-bit comparison using  
6 IC 7485 : Parallel  
(less delay than serial)

CASCAADING INPUTS			OUTPUTS		
A>B	A<B	A=B	A>B	A<B	A=B
H	H	L	L	L	L
L	L	L	H	H	L


A3=B3 | A2=B2 | A1=B1 | A0=B0

Treated equal in next level


 
# Arithmetic Logic Unit

Arithmetic Logic Unit (ALU) is a versatile unit that can perform arithmetic or logic operation on operands as per control input.



If  $S = 0$ ,  
 $Y_0 = (A.B)'$   
 $Y_1 = (A + B)'$

If  $S = 1$ ,  
 $Y_0 = A'.B + A.B'$   
(sum bit of H.A.)  
 $Y_1 = A.B$   
(carry bit of H.A.)

$$Y_0 = S'.(A.B)' + S.(A'.B + A.B')$$


... simplification ...

$$= S'.A' + A'.B + A.B'$$

$$Y_1 = S'.(A + B)' + S.A.B$$

$$= S'.A'.B' + S.A.B$$

# Arithmetic Logic Unit

 

Function Table


$S_1$	$S_0$	$C_{in}$	Output
0	0	X	$Y = (A.B)'$
0	1	X	$Y = (A + B)'$
1	0	0	$Y = A$
1	0	1	$Y = A \text{ PLUS } 1$
1	1	0	$Y = A \text{ PLUS } B$
1	1	1	$Y = A \text{ PLUS } B \text{ PLUS } 1$

Logic operation: Bitwise  
 Arithmetic operation: 2-bit number

	$\overline{A_0}\overline{B_0}$	$\overline{A_0}B_0$	$A_0B_0$	$A_0\overline{B_0}$
$\overline{S_1}\overline{S_0}$	1	1	0	1
$\overline{S_1}S_0$	1	0	0	0
$S_1S_0$	0	1	0	1
$S_1\overline{S_0}$	0	0	1	1

$Y_0$   
 for  $C_{in} = 0$

# IC 74181

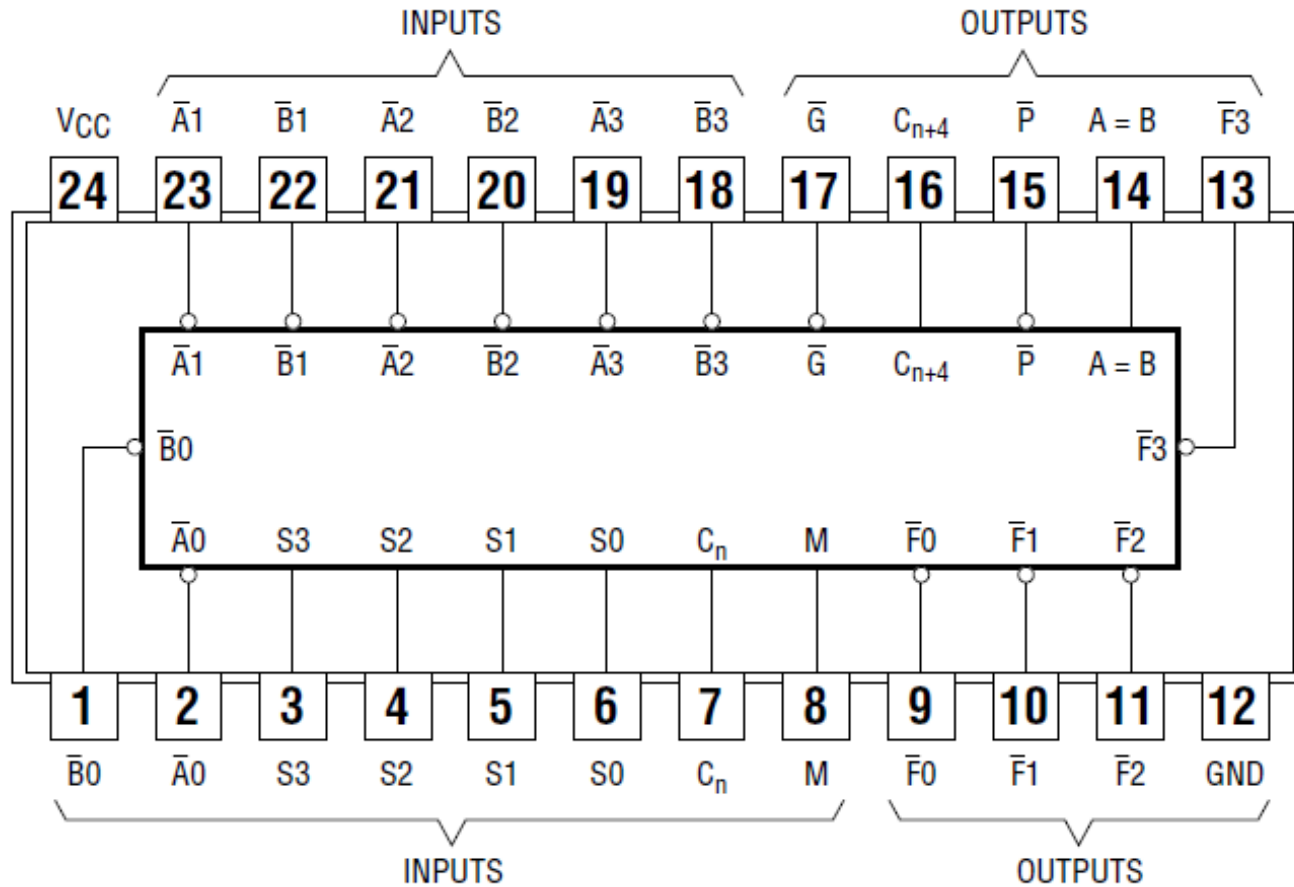

**M: Mode** L: Arithmetic operation  
H: Logic operation

## Arithmetic operation:

Addition  
Subtraction  
Shift operand A by one position  
Magnitude comparison  
....

## Logic operation:

NOT, AND, NAND, OR, NOR  
Ex-OR, Ex-NOR  
....

## Other outputs:

Group carry Generation  
and Propagation,  
Ripple carry, Equality

**Function  
outputs:  
(F3...F0)**

# Function Table

SELECTION				ACTIVE-LOW DATA		
				M = H LOGIC FUNCTION	M = L; ARITHMETIC OPERATIONS	
S3	S2	S1	S0		Cn = L (no carry)	Cn = H (with carry)
L	L	L	L	$F = \overline{A}$	$F = A \text{ MINUS } 1$	$F = A$
L	L	L	H	$F = \overline{AB}$	$F = AB \text{ MINUS } 1$	$F = AB$
L	L	H	L	$F = \overline{A} + B$	$F = \overline{AB} \text{ MINUS } 1$	$F = \overline{AB}$
L	L	H	H	$F = 1$	$F = \text{MINUS } 1(2\text{'s COMP})$	$F = 0$
L	H	L	L	$F = \overline{A + B}$	$F = A \text{ PLUS } (A + \overline{B})$	$F = A \text{ PLUS } (A + \overline{B}) \text{ PLUS } 1$
L	H	L	H	$F = \overline{B}$	$F = AB \text{ PLUS } (A + \overline{B})$	$F = AB \text{ PLUS } (A + \overline{B}) \text{ PLUS } 1$
L	H	H	L	$F = \overline{A \oplus B}$	$F = A \text{ MINUS } B \text{ MINUS } 1$	$F = A \text{ MINUS } B$
L	H	H	H	$F = A + \overline{B}$	$F = A + \overline{B}$	$F = (A + \overline{B}) \text{ PLUS } 1$
H	L	L	L	$F = \overline{AB}$	$F = A \text{ PLUS } (A + B)$	$F = A \text{ PLUS } (A + B) \text{ PLUS } 1$
H	L	L	H	$F = A \oplus B$	$F = A \text{ PLUS } B$	$F = A \text{ PLUS } B \text{ PLUS } 1$
H	L	H	L	$F = B$	$F = \overline{AB} \text{ PLUS } (A + B)$	$F = \overline{AB} \text{ PLUS } (A + B) \text{ PLUS } 1$
H	L	H	H	$F = A + B$	$F = (A + B)$	$F = (A + B) \text{ PLUS } 1$
H	H	L	L	$F = 0$	$F = A \text{ PLUS } A$	$F = A \text{ PLUS } A \text{ PLUS } 1$
H	H	L	H	$F = \overline{AB}$	$F = AB \text{ PLUS } A$	$F = AB \text{ PLUS } A \text{ PLUS } 1$
H	H	H	L	$F = AB$	$F = \overline{AB} \text{ PLUS } A$	$F = \overline{AB} \text{ PLUS } A \text{ PLUS } 1$
H	H	H	H	$F = A$	$F = A$	$F = A \text{ PLUS } 1$

- $(A = B)$  output is open collector providing wired-AND option (to compare > 4 bits)
- $A \text{ PLUS } A = 2 \times A$  which makes one left shift of A.

**Note:**  
74181 uses 1's C subtraction.

$C_n$	$C_{n+4}$	Result
L	L	$A \leq B$
L	H	$A > B$
H	L	$A < B$
H	H	$A \geq B$

**Magnitude Comparison**

Data: Active Low  
Mode, M: L

$S_3 S_2 S_1 S_0$ : LHLH  
(Subtraction)

# Function Table

SELECTION S3 S2 S1 S0				M = H LOGIC FUNCTION
L	L	L	L	$F = \overline{A}$
L	L	L	H	$F = \overline{AB}$
L	L	H	L	$F = \overline{A} + B$
L	L	H	H	$F = 1$
L	H	L	L	$F = \overline{A + B}$
L	H	L	H	$F = \overline{B}$
L	H	H	L	$F = \overline{A} \oplus \overline{B}$
L	H	H	H	$F = A + \overline{B}$
H	L	L	L	$F = \overline{AB}$
H	L	L	H	$F = A \oplus B$
H	L	H	L	$F = B$
H	L	H	H	$F = A + B$
H	H	L	L	$F = 0$
H	H	L	H	$F = A\overline{B}$
H	H	H	L	$F = A\overline{B}$
H	H	H	H	$F = A$


$A$	$B$	$f_0$	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$	$f_8$	$f_9$	$f_{10}$	$f_{11}$	$f_{12}$	$f_{13}$	$f_{14}$	$f_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
		13	5	9	1	14	6	10	2	15	7	11	3	16	8	12	4

**S3 S2 S1 S0: Function No.**

L	L	L	L	1
L	L	L	H	2
L	L	H	L	3
.....				
H	H	H	H	16

All possible logic functions of 2 variables are generated. Note that  $A$  and  $B$  are of 4-bits and bit-wise logic operation is done.

# Logic Circuit

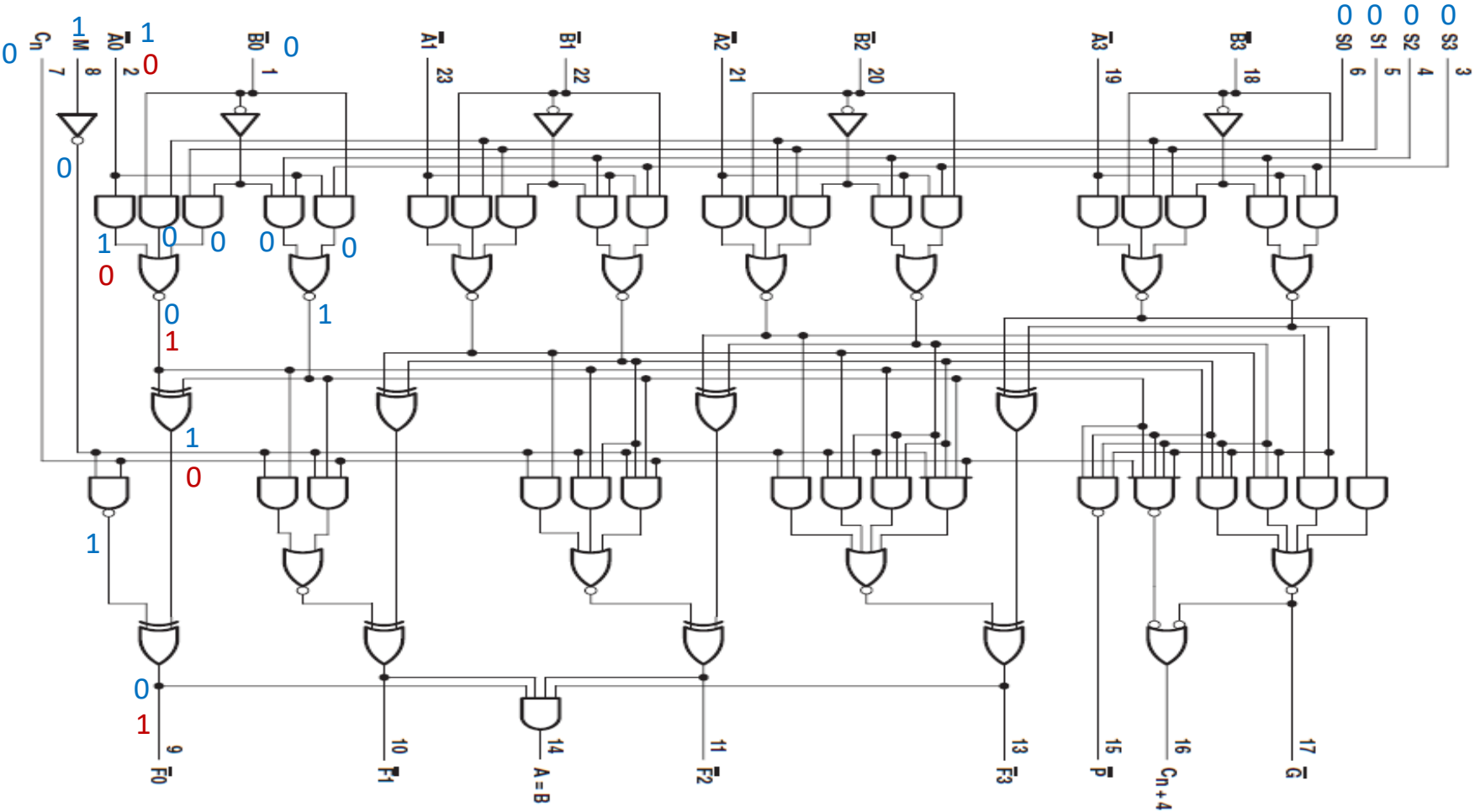

SELECTION				M = H LOGIC FUNCTION
S3	S2	S1	S0	
L	L	L	L	$F = \overline{A}$
L	L	L	H	$F = \overline{AB}$
L	L	H	L	$F = \overline{A} + B$

S3 S2 S1 S0: 0000  
M: 1, B: 0000, C<sub>n</sub>: 0

A0: 1 → F0: 0  
A0: 0 → F0: 1  
F0 = A0'

## References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill