

# Tutorial 1


EC31003 – Digital Electronics Circuits

12/09/2020

# Questions


1. (a) Find the minimum number of 2-input NOR gates required to realize the following expression:  
 $A'.B' + X.Y$ 

 (b) Find the minimum number of 2-input NAND gates required to realize the following expression:  
 $(W' + X')(Y + Z)$
2. The following is an internal schematic of a TTL logic gate. Based on your analysis of the transistor circuit determine the truth table for output Y and obtain the minimized expression for Y using DeMorgan's Theorem.




# Questions

 3. For a given logic family, consider  $V_{OL} = 0.9 \text{ V}$  and  $V_{OH} = 4.5 \text{ V}$ . For a given circuit,  $V_{IL} = 1.2 \text{ V}$  and  $V_{IH} = 3.2 \text{ V}$ . Find the noise margins ( $NM_L$ ,  $NM_H$ ), transition width and logic swing. Is it functionally better than a circuit with  $V_{IL} = 1.5 \text{ V}$  and  $V_{IH} = 3 \text{ V}$ ?
4. (a) Reduce the Boolean expression:  $Y = A'B(D' + C'D) + B(A + A'CD)$   
(b) In the circuit shown in the following figure, if  $C=0$ , find the expression for  $Y$ ?



# Questions

 Q.5. For the 2-input TTL NAND gate,  $V_{cc} = 5\text{ V}$  and a  $100\ \Omega$  load is connected to its output. Consider  $V_{CE(sat)} = 0.3\text{ V}$  and the current gain  $h_{FE} = 50$  for any of the transistors. Consider the diode drop in forward bias  $V_D = 0.7\text{ V}$ . The output voltage when both inputs are  $0\text{ V}$  is (i) \_\_\_\_\_ and when both inputs are  $5\text{ V}$  is (ii) \_\_\_\_\_ respectively.



# Solution 1(a)

- ▶ Find the minimum number of 2-input NOR gates required to realize the following expression:  $A'B' + XY$

- ▶  $A'B' + XY$

$$= (A'B' + X)(A'B' + Y)$$

(Distributive Property)

$$= ((A'B' + X)' + (A'B' + Y)')'$$

(De Morgan's law)

$$= (((A+B)' + X)' + ((A+B)' + Y)')'$$

⇒ 4 NOR gates required

# Solution 1(b)

- ▶ Find the minimum number of 2-input NAND gates required to realize the following expression:  $(W'+X')(Y+Z)$

- ▶  $(W'+X')(Y+Z)$

$$= (W'+X')Y + (W'+X')Z \quad \text{(Distributive law)}$$

$$= [((W'+X')Y + (W'+X')Z)']'$$

$$= [((W'+X')Y)' \cdot ((W'+X')Z)']' \quad \text{(De Morgan's theorem)}$$

$$= [((WX)'Y)' \cdot ((WX)'Z)']'$$

⇒ 4 NAND gates required

# Solution 2

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$\begin{aligned}
 Y &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} \\
 &\quad + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C} + A\bar{B}C\bar{D} \\
 &= \bar{A}\bar{B}(\bar{C} + C\bar{D}) + \bar{A}\bar{B}(\bar{C} + C\bar{D}) + A\bar{B}(\bar{C} + C\bar{D}) \\
 &= (\bar{C} + C\bar{D})(\bar{A}\bar{B} + \bar{A}\bar{B} + A\bar{B}) \\
 &= (\bar{C} + \bar{D})(\bar{A} + A\bar{B}) \\
 &= (\bar{C} + \bar{D})(\bar{A} + \bar{B}) \\
 &= \bar{C}\bar{D} \quad \bar{A}\bar{B}
 \end{aligned}$$

# Solution 3

Given,  $V_{OL} = 0.9 \text{ V}$  and  $V_{OH} = 4.5 \text{ V}$

For 1<sup>st</sup> circuit,  $V_{IL} = 1.2 \text{ V}$  and  $V_{IH} = 3.2 \text{ V}$

$$NM_L = V_{IL} - V_{OL} = 1.2 - 0.9 = \mathbf{0.3 \text{ V}}$$

$$NM_H = V_{OH} - V_{IH} = 4.5 - 3.2 = \mathbf{1.3 \text{ V}}$$

$$\text{Transition width} = V_{IH} - V_{IL} = 3.2 - 1.2 = \mathbf{2 \text{ V}}$$

$$\text{Logic swing} = V_{OH} - V_{OL} = 4.5 - 0.9 = \mathbf{3.6 \text{ V}}$$

For 2<sup>nd</sup> circuit,  $V_{IL} = 1.5 \text{ V}$  and  $V_{IH} = 3 \text{ V}$

$$NM_L = V_{IL} - V_{OL} = 1.5 - 0.9 = \mathbf{0.6 \text{ V}}$$

$$NM_H = V_{OH} - V_{IH} = 4.5 - 3 = \mathbf{1.5 \text{ V}}$$

No, the 2<sup>nd</sup> circuit is functionally better than the 1<sup>st</sup> circuit due to its higher noise margins.



## Solution 4 (a)

$$\begin{aligned} Y &= A'B(D'+C'D)+B(A+A'CD) \\ &= A'B(D'+C')+B(A+CD) \\ &= B[A'(D'+C')+(A+CD)] \\ &= B[A'D'+(A'C'+A)+CD] \\ &= B[A'D'+(A+C')+CD] \\ &= B[(A'D'+A)+(C'+CD)] \\ &= B[(A+D')+(C'+D)] \\ &= B[A+(D'+D)+C'] \\ &= B[A+1+C'] \\ &= B \end{aligned}$$

## Solution 4 (b)

$$Y = (1.((A+B)' + AB))'$$

APPLY DE MORGANS LAW

$$Y = (A'B' + AB)'$$

$$Y = (A \text{ XNOR } B)'$$

$$Y = (A \text{ XOR } B)$$

$$Y = AB' + A'B$$

# Solution 5

When both inputs are LOW, the output is HIGH (Q3 is ON but Q2 and Q4 are OFF).

Applying KVL,

$$V_{CC} = I_L R_4 + V_{CE(sat)} + V_D + I_L R_L$$

$$I_L = \frac{V_{CC} - V_{CE(sat)} - V_D}{R_L + R_4}$$

Substituting the values, we get  $I_L = 17.39 \text{ mA}$

$$\text{Hence, } V_0 = I_L R_L = 1.739 \text{ V}$$

When both inputs are HIGH, i.e. 5V:

For open load,

Q3 is OFF. Q2 and Q4 in saturation. For open load,  $I_{C4} \approx 0$ . That makes Q4 go deep in saturation i.e.  $V_O = V_{CE} \approx 0$ .

For resistive load,  $R_L$

If a voltage drop exists across  $R_L$  (i.e.  $V_O > 0$ ), then a current has to flow through it. This current has to be sourced by the Q4 transistor, i.e. the current has to flow out of the collector terminal through  $R_L$ . However, this is not possible since Q4 is an npn transistor and its collector can only sink current. Hence, the output voltage  $V_O$  is maintained at 0, i.e.  $V_O = 0$ .

