


Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 22

An Example

 
- To analyse the circuit and find how states change with the input clock and how output is generated.



Note that,

- for the basic logic gate part of the circuit, output will be considered as immediately available when input is presented and
- for the flip-flop / memory element part of the circuit, its output change as per **Truth Table / Characteristic Eqn.** waits till the clock trigger.
- Basic gate delay is negligible compared to clock time period. Effect of those delay will be considered later.

Defining Flip-Flop Inputs and Output

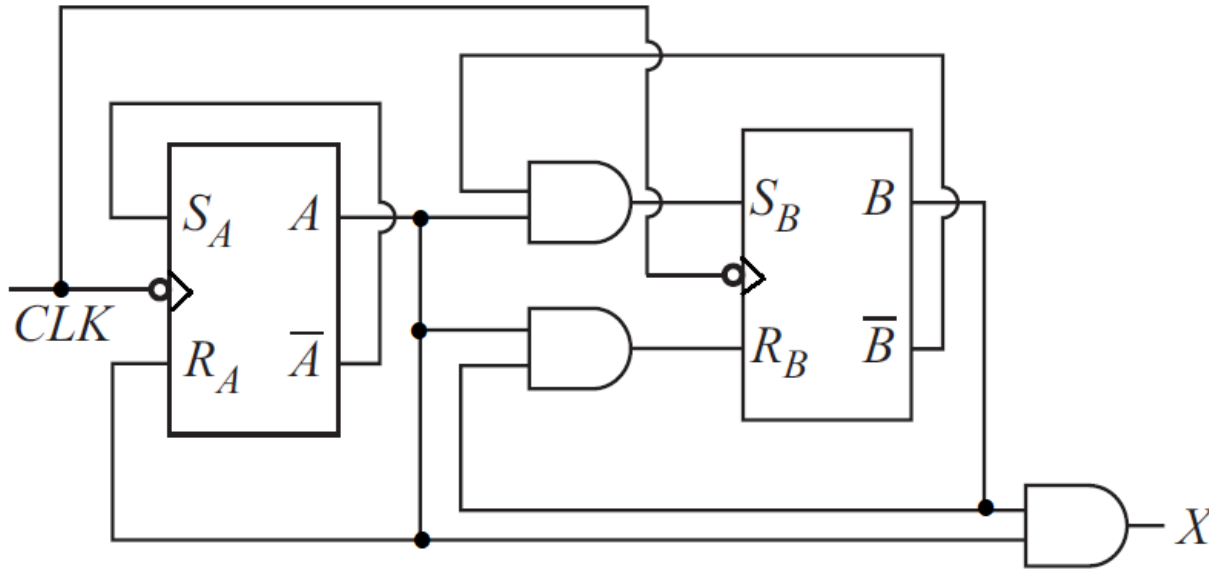

For Flip-Flop A,

$$S_A = A_n'$$
$$R_A = A_n$$

For Output,

$$X = A_n \cdot B_n$$

For Flip-Flop B,

$$S_B = A_n \cdot B_n'$$
$$R_B = A_n \cdot B_n$$

State Analysis Table

Current State		Current Flip-Flop Input					Next State		Output
CLK	B_n	A_n	S_B	R_B	S_A	R_A	B_{n+1}	A_{n+1}	X
0	0	0	0	0	1	0	0	1	0
1	0	1	1	0	0	1	1	0	0
2	1	0	0	0	1	0	1	1	0
3	1	1	0	1	0	1	0	0	1
4	0	0	0	0	1	0	0	1	0
5	0	1			...				

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	N.A.

$$S_A = A_n'$$

$$R_A = A_n$$


$$X = A_n \cdot B_n$$

$$S_B = A_n \cdot B_n'$$

$$R_B = A_n \cdot B_n$$


- Clock 0: The initial state is assumed to be 0 for each flip-flop.
- Clock n : Next state of clock $(n - 1)$ is the present state at clock n and the circuit evolves.
- State transition as per Flip-Flop Truth Table for the input present.

Analysis Result

 


The circuit generates an **output = 1** at **every 4th clock** trigger when it reaches the state **$BA = 11$** and repeats the state transition **$00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$**



Using Timing Diagram

 

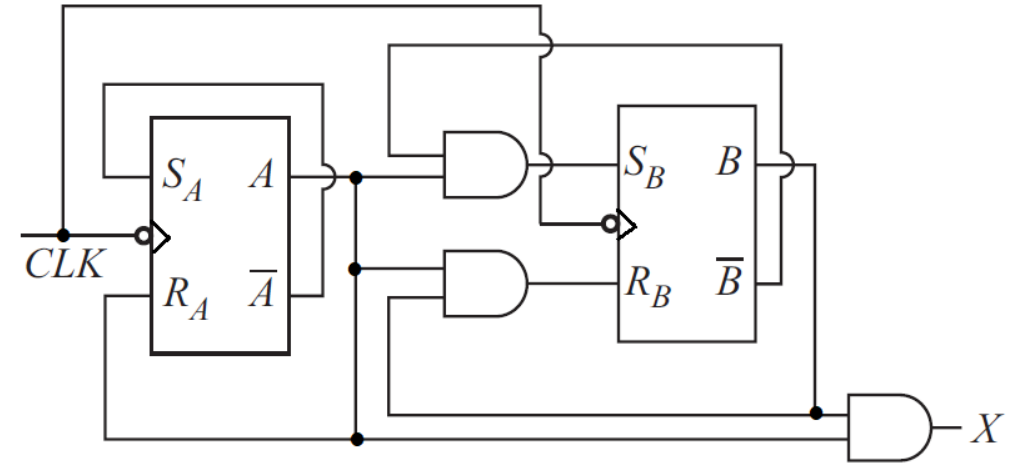- Starting with initial 00 state, progress with time where Flip-Flop can change state only at –ve edge of the clock.
- Timing diagram can show the effect of delay in various elements and any deviation in performance due to propagation delay.



Using Timing Diagram

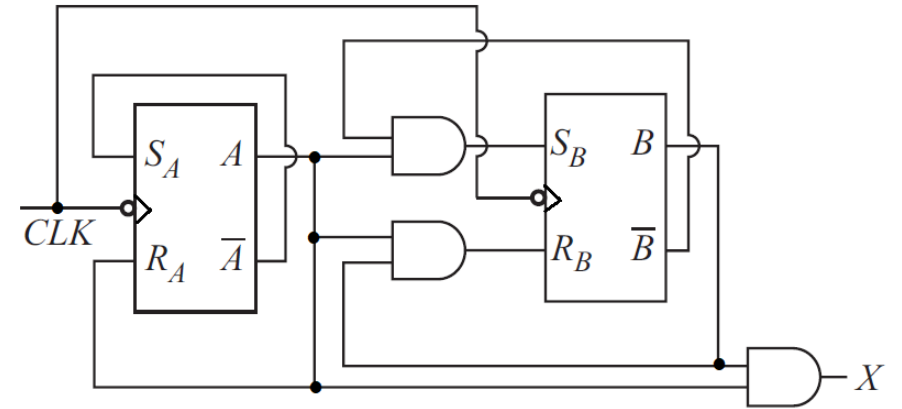 

Using Characteristic Equation

SR Flip-Flop Characteristic Eqn.: $Q_{n+1} = S + R'.Q_n$

$$S_A = A_n'$$

$$R_A = A_n$$

$$A_{n+1} = S_A + R_A'.A_n$$

Substituting,

$$\begin{aligned} A_{n+1} &= A_n' + A_n'.A_n \\ &= A_n' \end{aligned}$$

$$S_B = A_n.B_n'$$

$$R_B = A_n.B_n$$

$$B_{n+1} = S_B + R_B'.B_n$$


Substituting,

$$\begin{aligned} B_{n+1} &= A_n.B_n' + (A_n.B_n)'.B_n \\ &= A_n.B_n' + (A_n' + B_n)'.B_n \\ &= A_n.B_n' + A_n'.B_n + B_n'.B_n \\ &= A_n.B_n' + A_n'.B_n \\ &= A_n \oplus B_n \end{aligned}$$

CLK	B_n	A_n	B_{n+1}	A_{n+1}	X
0	0	0	0	1	0
1	0	1	1	0	0
2	1	0	1	1	0
3	1	1	0	0	1
4	0	0	0	1	0
5	0	1		...	

$$X = A_n.B_n$$


Another Example

 

$$D = X \oplus Q_n$$

$$Y = X \cdot Q_n'$$


Q_n	X	D	Q_{n+1}	Y
0	0	0	0	0
0	1	1	1	1
1	0	1	1	0
1	1	0	0	0

 

T Flip-Flop

State toggles when input is 1, else maintains previous state. Output is 1 when input received at State 0 is 1, else output is 0.

***D* to other Flip-Flops**

 

$$Q_{n+1} = T.Q_n' + T'.Q_n$$




$$D = T.Q_n' + T'.Q_n$$

$$Q_{n+1} = D$$

$$Q_{n+1} = J.Q_n' + K'.Q_n$$



$$D = J.Q_n' + K'.Q_n$$

 

$$Q_{n+1} = S + R'.Q_n$$



$$D = S + R'.Q_n$$

SR, JK Flip-Flops to D Flip-Flop

$$Q_{n+1} = S + R'.Q_n$$

Consider,

$$S = D$$

$$R = D'$$

Then,

$$\begin{aligned} Q_{n+1} &= D + (D')'.Q_n \\ &= D + D.Q_n \\ &= D.(1 + Q_n) \\ &= D.1 = D \end{aligned}$$

$$Q_{n+1} = J.Q_n' + K'.Q_n$$


Consider,

$$J = D$$

$$K = D'$$

Then,
 
$$\begin{aligned} Q_{n+1} &= D.Q_n' + (D')'.Q_n \\ &= D.Q_n' + D.Q_n \\ &= D.(Q_n' + Q_n) \\ &= D.1 = D \end{aligned}$$



$$Q_{n+1} = T.Q_n' + T'.Q_n$$


?

D Flip-Flop from ***T*** Flip-Flop

<i>D</i>	<i>Q_n</i> → <i>Q_{n+1}</i>	<i>T</i>
0	0	0
0	1	1
1	0	1
1	1	0

<i>D</i> \ <i>Q_n</i>	0	1
0	0	1
1	1	0

$$T = D.Q_n' + D'.Q_n$$

 

 Truth Table

 Excitation Table

$$\begin{aligned}
 Q_{n+1} &= T.Q_n' + T'.Q_n \\
 &= (D.Q_n' + D'.Q_n).Q_n' + (D.Q_n' + D'.Q_n)'.Q_n \\
 &= D.Q_n' + (D'.Q_n' + D.Q_n).Q_n \\
 &= D.Q_n' + D.Q_n = D
 \end{aligned}$$

Conversion: *SR* and *JK*

- JK* Flip-Flop can directly replace *SR* Flip-Flop as the Truth Table differs only for 11 input which is avoided in a circuit that uses *SR* Flip-Flop.

J_n	K_n	Q_n	Q_{n+1}	S_n	R_n
0	0	0	0	0	×
0	0	1	1	×	0
0	1	0	0	0	×
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	×	0
1	1	0	1	1	0
1	1	1	0	0	1

$Q_n \rightarrow Q_{n+1}$		S	R
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0

To obtain *JK* Flip-Flop
from *SR* Flip-Flop


Conversion: *SR* and *JK*

Q_n	$J_n K_n$			
	0 0	0 1	1 1	1 0
0	0	0	1	1
1	×	0	0	×

$$S_n = J_n \bar{Q}_n$$

Q_n	$J_n K_n$			
	0 0	0 1	1 1	1 0
0	×	×	0	0
1	0	1	1	0

$$R_n = K_n Q_n$$

 

J_n	K_n	Q_n	Q_{n+1}	S_n	R_n
0	0	0	0	0	×
0	0	1	1	×	0
0	1	0	0	0	×
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	×	0
1	1	0	1	1	0
1	1	1	0	0	1


Flip-Flop Timing Parameters

Setup time: Minimum amount of time data must be present before clock trigger arrives.

Hold time: Minimum amount of time data must be held after clock trigger.

Propagation delay: Time taken for the output to change after clock trigger in response to the input.

Parameter	74LS74A ($V_{CC}=5V$)	74HC74 ($V_{CC}=4.5V$)
t_{setup} (Data) [^]	20	25
t_{hold} [^]	5	≈ 0
t_p (CLK to Q) [#]	25/40 [*]	44
f_{max} ^{\$}	33	50
	TTL	CMOS

 

[^]:minimum time in ns

[#]:maximum time in ns

^{*}:L to H / H to L

^{\$}:typical in MHz

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill