


Digital Electronic Circuits

Section 1 (EE, IE)


Lecture 4

Inverter (NOT Gate)


$$Y = \text{not } A$$

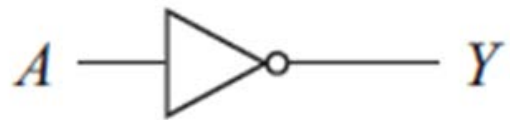


$$Y = \overline{A} \quad Y = A'$$

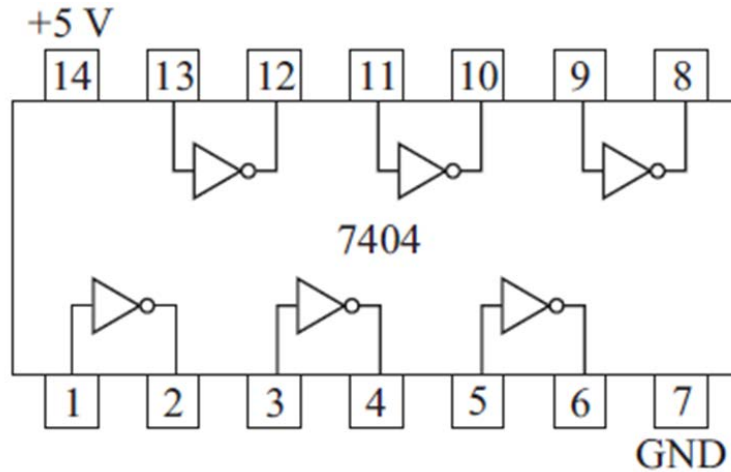

A	Y	A	Y
L	H	0	1
H	L	1	0

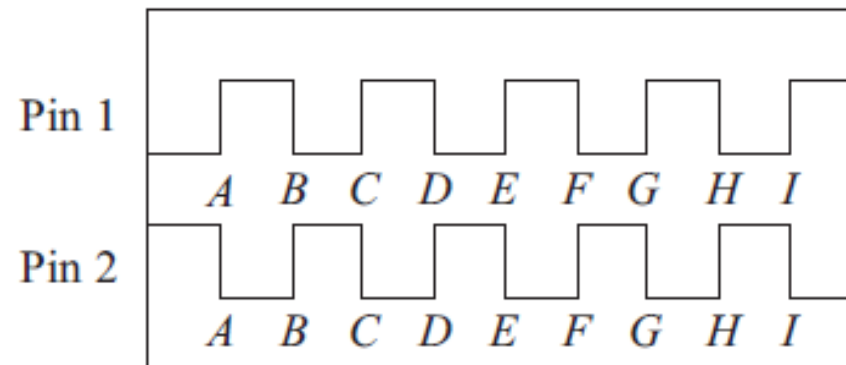


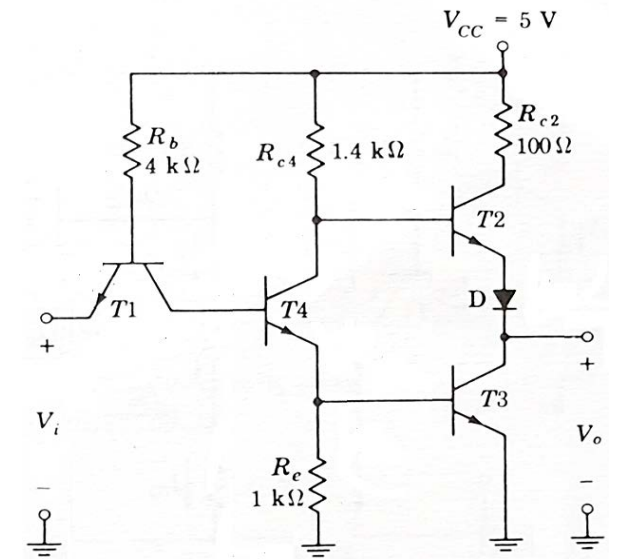Delay in actual circuit i.e. not instantaneous.





AND Gate

$Y = A \text{ AND } B$

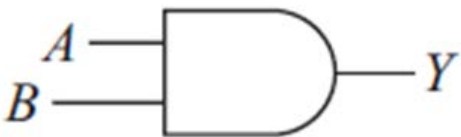

$Y = A.B = A.B$
 $= B.A$



(Commutative)

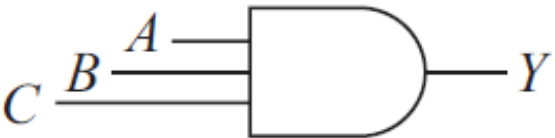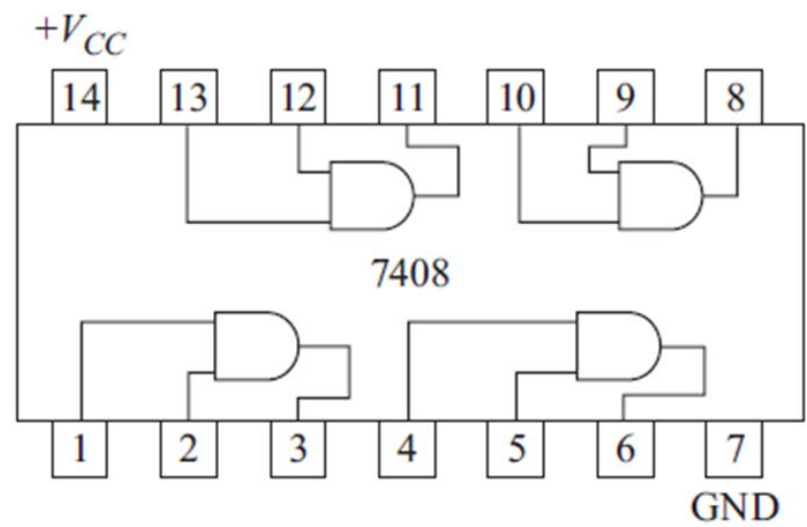

$Y = A.B.C$
 $= A.(B.C)$
 $= (A.B).C$

(Associative)

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

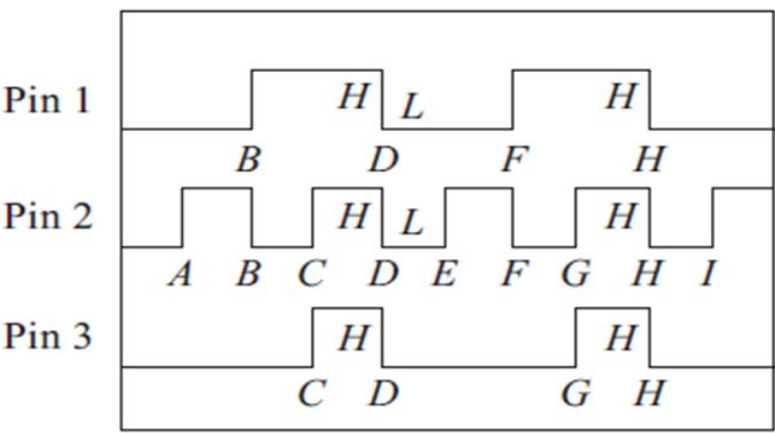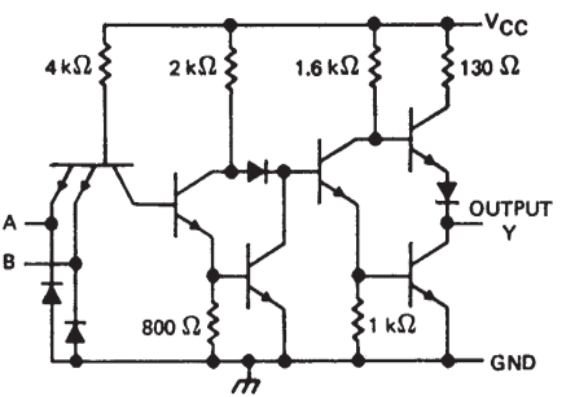

OR Gate



$Y = A \text{ OR } B$



$$Y = A + B$$

$$= B + A$$

(Commutative)

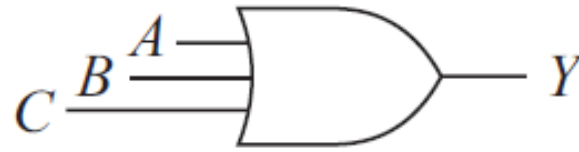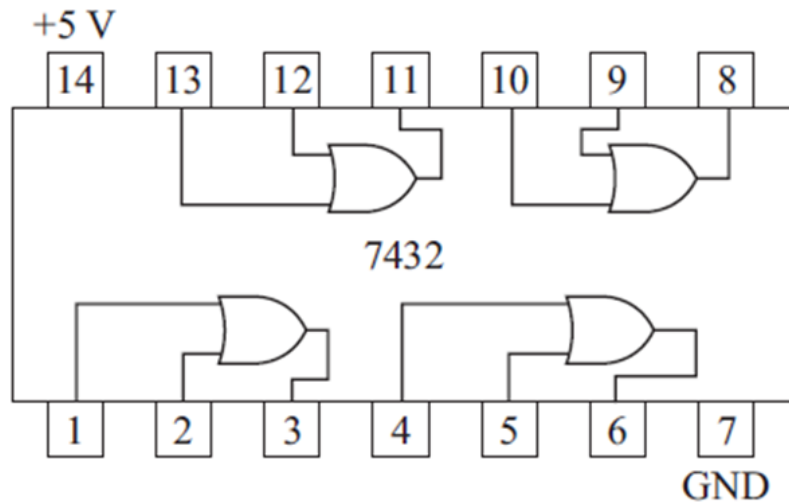



$$Y = A + B + C$$

$$= A + (B + C)$$



$$= (A + B) + C$$

(Associative)


A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

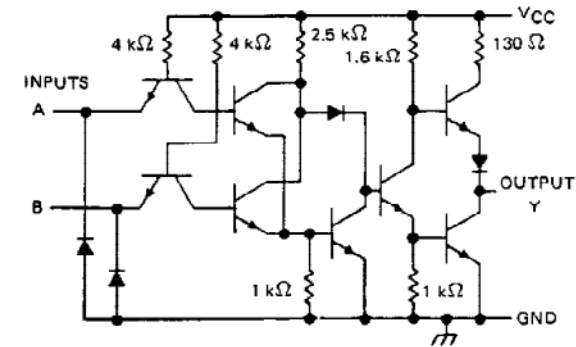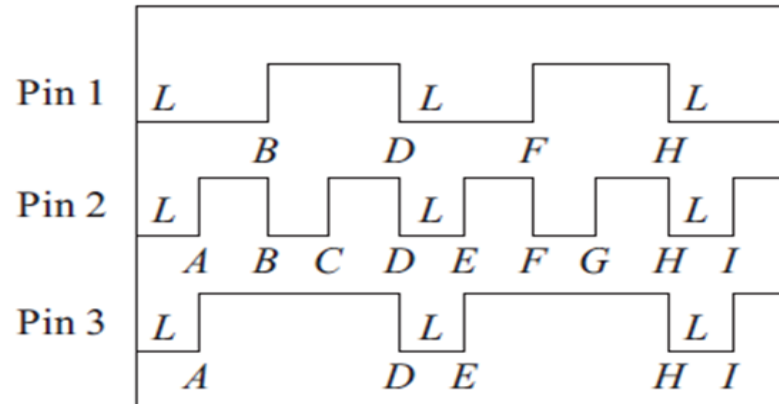

NOR Gate

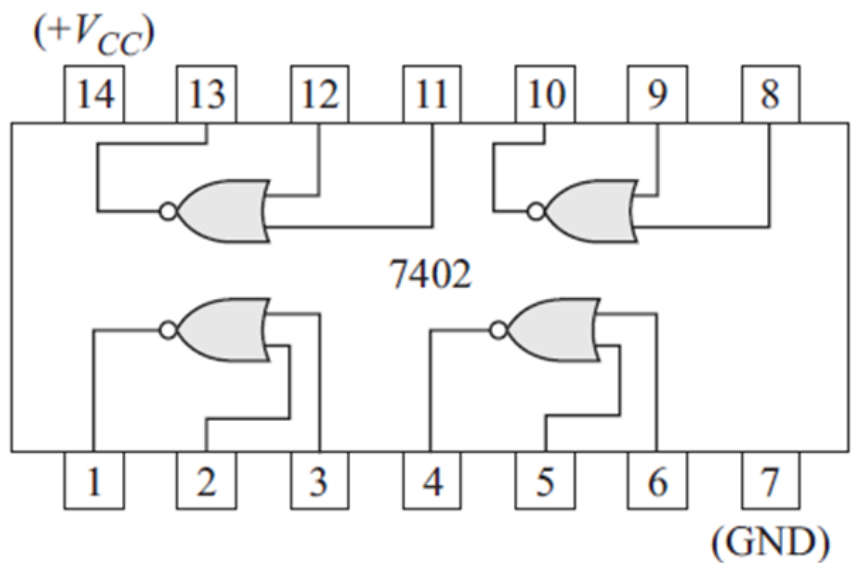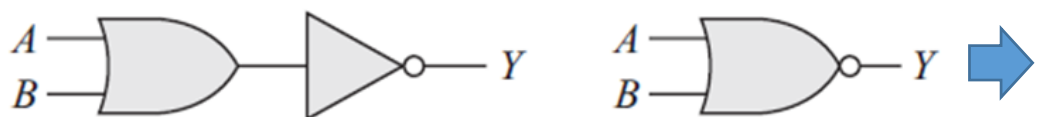

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

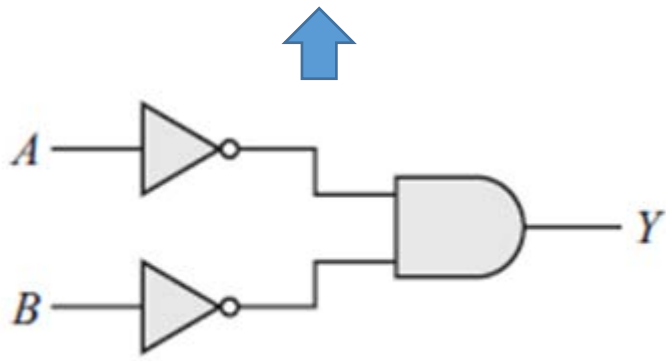



$$Y = \overline{A + B} = \overline{A} \overline{B}$$

(Commutative)


De Morgan's
1st Theorem:

$$Y = \overline{(A + B + C + \dots)} \\ = \overline{A} . \overline{B} . \overline{C} \dots$$

NAND Gate

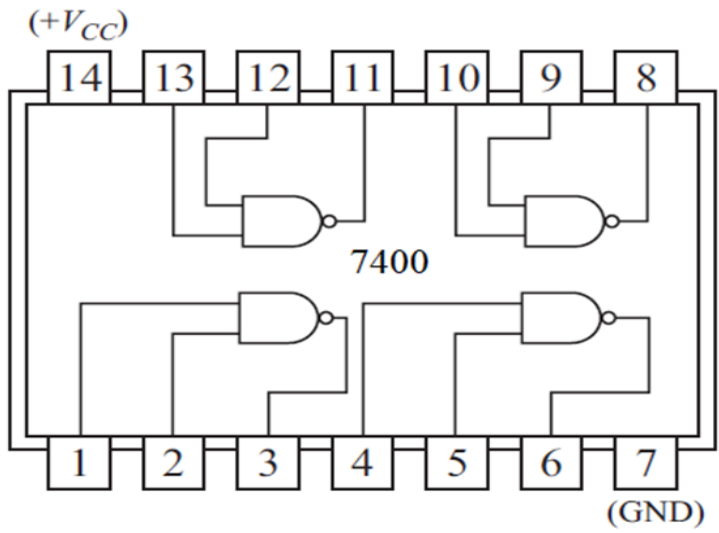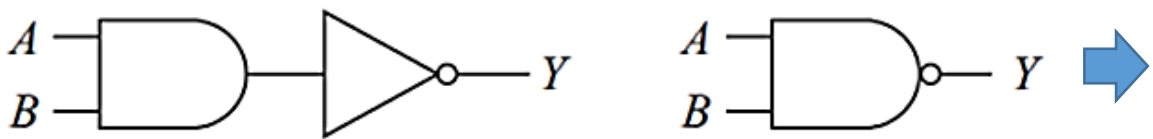

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

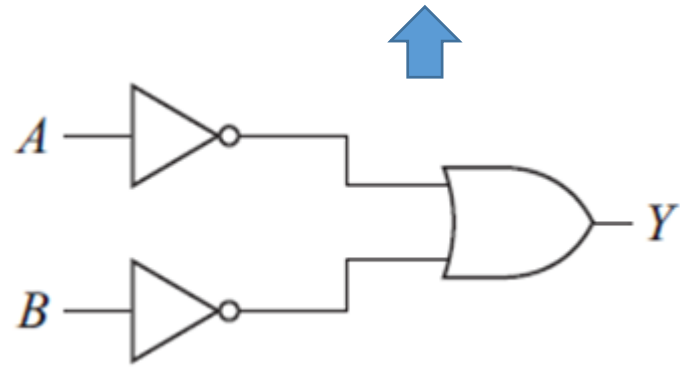

$$Y = \overline{A} \overline{B} = \overline{A} + \overline{B}$$






(Commutative)

De Morgan's
2nd Theorem:

$$Y = \overline{ABC}.. \\ = \overline{A} + \overline{B} + \overline{C} + ...$$

Universality of NOR, NAND gate

Realization of AND, OR, NOT

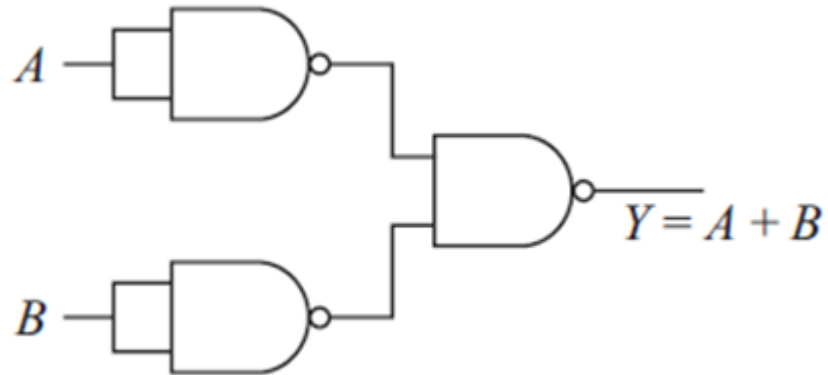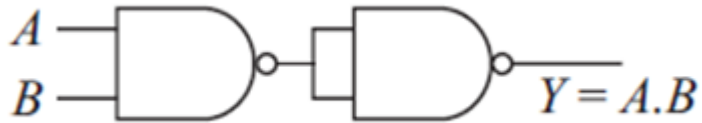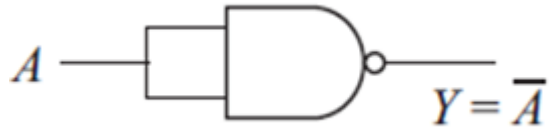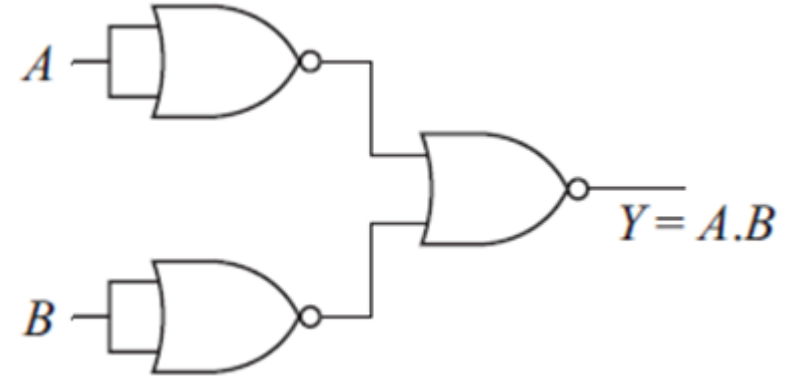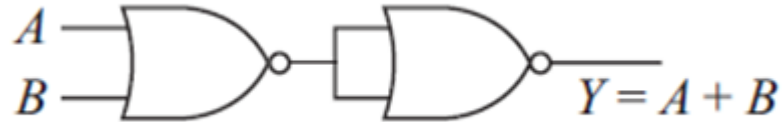

Possible Logic Operations

All Possible Logic Operations																		
x	y	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}	
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	
			NOR		NOT x		NOT y		NAND	AND								OR

- 2^{2^n} possible functions with n variables
- Formalization of representation and manipulation: Boolean Algebra


Boolean Algebra: Huntington Postulates

No.	Postulate	Description
1	Closed with operators + and .	Result of each is 1, $0 \in B$
2	Identity element: 0 with +, 1 with .	$x + 0 = x$; $x.1 = x$
3	Commutative w.r.t. +, .	$x + y = y + x$; $x.y = y.x$
4	. is distributive over +, + is distributive over .	$x.(y + z) = x.y + x.z$; $x + (y.z) = (x + y).(x + z)$
5	For $x \in B$, there is $x' \in B$ s.t. $x + x' = 1$ and $x.x' = 0$	$0 + 0' = 0 + 1 = 1$, $1 + 1' = 1$; $0.0' = 0.1 = 0$, $1.1' = 1.0 = 0$
6	At least 2 elements $x, y \in B$ s.t. $x \neq y$	$B = \{0,1\}$, $0 \neq 1$

1854: Boolean Algebra,
George Boole

1904: Postulates, E. V.
Huntington

1938: Switching Algebra
(2-valued), Claude. E.
Shanon

Associative Law: $(x + y) + z = x + (y + z)$; $(x.y).z = x.(y.z)$  From postulates

Postulates and Basic Theorems

Name	(a)	(b)
Identity	$x + 0 = x$	$x.1 = x$
Null	$x + 1 = 1$	$x.0 = 0$
Complementarity	$x + x' = 1$	$x.x' = 0$
Idempotency	$x + x = x$	$x.x = x$
Involution	$(x')' = x$	
Commutative	$x + y = y + x$	$x.y = y.x$
Associative	$(x + y) + z = x + (y + z)$	$(x.y).z = x.(y.z)$
Distributive	$x.(y + z) = x.y + x.z$	$x + (y.z) = (x + y).(x + z)$

Proof: Null (a)

$$\begin{aligned}x + 1 &= (x + 1).1 \\&= (x + 1).(x + x') \\&= x + x'.1 \\&= x + x' \\&= 1\end{aligned}$$

Duality and Boolean Expressions

Name	(a)	(b)
Absorption	$x + x.y = x$	$x.(x + y) = x$
Adsorption	$x + x'.y = x + y$	$x.(x' + y) = x.y$
Uniting	$x.y + x.y' = x$	$(x + y).(x + y') = x$
Consensus	$x.y + x'.z + y.z = x.y + x'.z$	$(x + y).(x' + z).(y + z) = (x + y).(x' + z)$
De Morgan's	$(x_1 + x_2 + x_3 + \dots x_N)' = x_1'.x_2'.x_3'. \dots x_N'$	$(x_1.x_2.x_3. \dots x_N)' = x_1' + x_2' + x_3' + \dots + x_N'$

Duality: Boolean Algebraic expression remains valid if the operators and identity elements are interchanged.

Proof: Null (b)
 $x + 1 = 1$ (proven)
By Duality, $x.0 = 0$

Operator precedence: Parentheses, NOT, AND, OR

More Proof

Proof: Idempotency (a)

$$\begin{aligned}x + x &= (x + x).1 && \text{:Identity}\\&= (x + x).(x + x') && \text{:Complem.}\\&= x + x.x' && \text{:Distribut.}\\&= x + 0 && \text{:Complem.}\\&= x && \text{:Identity}\end{aligned}$$

Proof: Idempotency (b)

$$\begin{aligned}x.x &= x.x + 0\\&= x.x + x.x'\\&= x.(x + x')\\&= x.1\\&= x\end{aligned}$$

[Also, by duality of (a),
 $x + x = x$]

Proof: Involution

$$\begin{aligned}(x')' &= (x')' + 0\\&= (x')' + x.x'\\&= [(x')' + x].[(x')' + x']\\&= [x + (x')'].[x' + (x')']\\&= [x + (x')'].1\\&= [x + (x')'].[x + x']\\&= x + (x')'.x'\\&= x + x'.(x')'\\&= x + 0\\&= x\end{aligned}$$

More Proof

Proof: Consensus (a)

$$\begin{aligned}x.y + x'.z + y.z &= x.y + x'.z + y.z.1 \\&= x.y + x'.z + y.z.(x + x') \\&= x.y + x'.z + x.y.z + x'.y.z \\&= (x.y + x.y.z) + (x'.z + x'.y.z) \\&= (x.y + x.y.z) + (x'.z + x'.y.z) \\&= x.y.(1 + z) + x'.z.(1 + y) \\&= x.y.1 + x'.z.1 \\&= x.y + x'.z\end{aligned}$$

Proof: De Morgan's Th. (a) 2 var.: $(x + y)' = x'.y'$

We know, $(x + y) + (x + y)' = 1$

To show, $(x + y) + x'.y' = 1$

$$\begin{aligned}(x + y) + x'.y' &= [(x + y) + x'].[(x + y) + y'] \\&= [(y + x) + x'].[(x + y) + y'] \\&= [y + (x + x')].[x + (y + y')] \\&= [y + 1].[x + 1] \\&= 1.1 \\&= 1\end{aligned}$$

More Characteristics

- Distributive Law, $x + (y.z) = (x + y).(x + z)$, is not valid for ordinary algebra.
- **Complement** is not available in ordinary algebra.
- Boolean algebra does not have **subtraction, division**.
- Boolean algebra (2-valued) has **finite set of elements** (0 and 1).

**Difference
with ordinary
algebra**

Use of NAND (\uparrow), NOR (\downarrow) instead of AND (\cdot), OR ($+$):

- $(x \uparrow y) \uparrow z \neq x \uparrow (y \uparrow z)$; $(x \uparrow y)' \uparrow z = x \uparrow (y \uparrow z)'$
- $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$; $(x \downarrow y)' \uparrow z = x \downarrow (y \downarrow z)'$
- $x \uparrow (y \downarrow z) \neq (x \downarrow y) \uparrow (x \downarrow z)$; $x \uparrow (y \downarrow z) = (x' \downarrow y) \uparrow (x' \downarrow z)$
- $x \downarrow (y \uparrow z) \neq (x \uparrow y) \downarrow (x \uparrow z)$; $x \downarrow (y \uparrow z) = (x' \uparrow y) \downarrow (x' \uparrow z)$

Pseudoassociative

Pseudodistributive

Boolean Function to Truth Table

$$F(x,y) = x + x'.y$$

$$F(0,0) = 0 + 0'.0 = 0 + 1.0 = 0 + 0 = 0$$

$$F(0,1) = 0 + 0'.1 = 0 + 1.1 = 0 + 1 = 1$$

$$F(1,0) = 1 + 1'.0 = 1 + 0.0 = 1 + 0 = 1$$

$$F(1,1) = 1 + 1'.1 = 1 + 0.1 = 1 + 0 = 1$$

x	y	$F(x,y)$
0	0	0
0	1	1
1	0	1
1	1	1

x	y	z	$F(x,y,z)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F(x,y,z) = (x + y).(x + z)$$


$$F(0,0,0) = (0 + 0).(0 + 0) \\ = 0.0 = 0$$

$$F(0,0,1) = (0 + 0).(0 + 1) \\ = 0.1 = 0$$


...

...

Implementation of Boolean Function

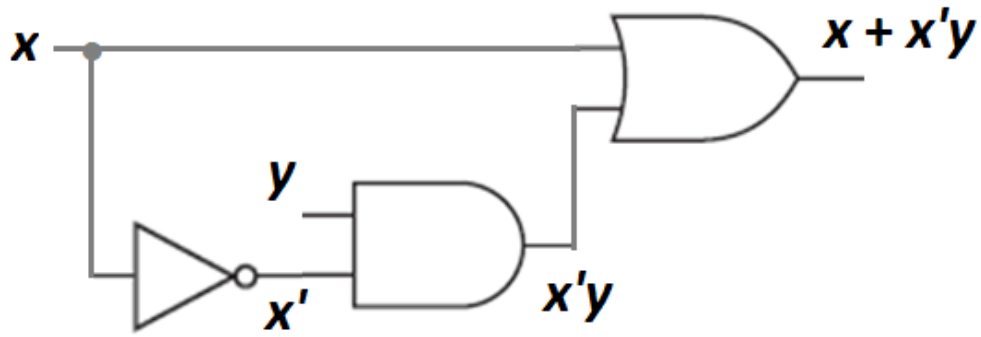

$$F(x,y) = x + x'y$$

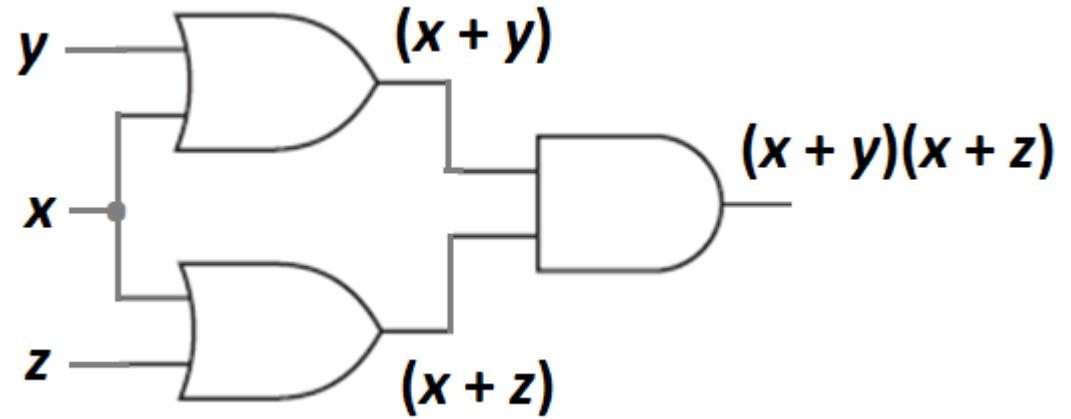

$$F(x,y,z) = (x + y).(x + z)$$

Efficient Implementation

Use of Boolean Algebra

Equivalence can be verified from Truth Table.

From Adsorption Theorem:

$$F(x,y) = x + x'.y = x + y$$




Earlier: One NOT, One 2 i/p AND,
One 2 i/p OR

Now: One 2 i/p OR

From Postulate (Distributive Law):

$$(x + y).(x + z) = x + y.z$$

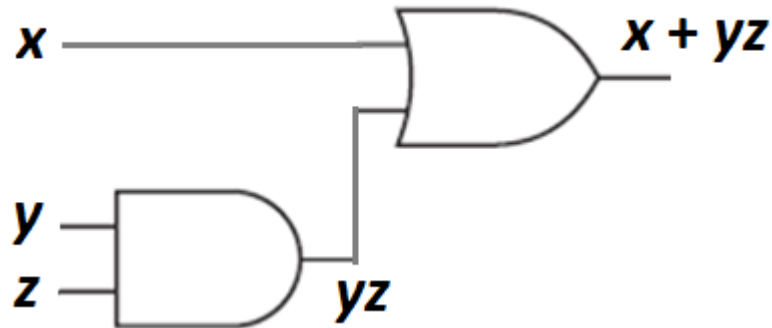

Earlier: One 2 i/p AND, Two 2 i/p OR

Now: One 2 i/p AND, One 2 i/p OR

Algebraic Simplification

Simplify,

$$Y = F(A,B,C) = A(A' + C)(A'B + C)(A'BC + C')$$

$$\begin{aligned} Y &= (AA' + AC) (A'B + C) (A'BC + C') : \text{distribut.} \\ &= AC(A'B + C) (A'BC + C') : XX' = 0 \\ &= (AC \cdot A'B + AC \cdot C) (A'BC + C') : \text{distribut.} \\ &= AC(A'BC + C') : XX' = 0 \\ &= AC \cdot A'BC + AC \cdot C' : \text{distribut.} \\ &= 0 + 0 = 0 : XX' = 0 \end{aligned}$$

Note that, output Y is always L here and can be connected to LOW voltage directly.

Simplify, $Y = (A + B)(A'(B' + C'))' + A'(B + C)$

$$\begin{aligned} Y &= (A + B) ((A + (B' + C'))') + A'(B + C) : \text{De Morgan's} \\ &= (A + B) (A + BC) + A'(B + C) : \text{De Morgan's} \\ &= (AA + ABC + AB + BBC) + A'(B + C) \\ &= (A + AB + ABC + BC) + A'(B + C) \\ &= A(1 + B + BC) + BC + A'(B + C) \\ &= A + BC + A'(B + C) \\ &= (A + A'(B + C)) + BC \\ &= A + B + C + BC \\ &= A + B + C(1 + B) \\ &= A + B + C \end{aligned}$$

Shanon's Expansion Theorem

$$F(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot F(0, x_2, x_3, \dots, x_N) + x_1 \cdot F(1, x_2, x_3, \dots, x_N)$$

Proof: x_1 can take only 2 values, 0 and 1

$$\begin{aligned}\text{For } x_1 = 0, \text{ LHS} &= F(0, x_2, x_3, \dots, x_N) = 0' \cdot F(0, x_2, x_3, \dots, x_N) + 0 \cdot F(1, x_2, x_3, \dots, x_N) \\ &= 1 \cdot F(0, x_2, x_3, \dots, x_N) + 0 \\ &= F(0, x_2, x_3, \dots, x_N) = \text{RHS}\end{aligned}$$

$$\begin{aligned}\text{For } x_1 = 1, \text{ LHS} &= F(1, x_2, x_3, \dots, x_N) = 1' \cdot F(0, x_2, x_3, \dots, x_N) + 1 \cdot F(1, x_2, x_3, \dots, x_N) \\ &= 0 \cdot F(0, x_2, x_3, \dots, x_N) + F(1, x_2, x_3, \dots, x_N) \\ &= 0 + F(1, x_2, x_3, \dots, x_N) \\ &= F(1, x_2, x_3, \dots, x_N) = \text{RHS}\end{aligned}$$

Dual Form:

$$F(x_1, x_2, x_3, \dots, x_N) = [x_1' + F(1, x_2, x_3, \dots, x_N)] \cdot [x_1 + F(0, x_2, x_3, \dots, x_N)]$$

Example:

$$F(x, y) = x + x' \cdot y$$

$$F(0, y) = 0 + 0' \cdot y = 1 \cdot y = y$$

$$F(1, y) = 1 + 1' \cdot y = 1$$

$$\begin{aligned}F(x, y) &= x' \cdot F(0, y) + x \cdot F(1, y) \\ &= x' \cdot y + x \cdot 1 \\ &= x' \cdot y + x \\ &= x + x' \cdot y\end{aligned}$$

Example on Simplification

Simplify,

$$F(A, B, C, D, E) = A + \bar{A}.B + A.D.(B + E).(B.C + D.E)$$

Choice of A as expansion variable as it is associated with more number of terms

$$F(0, B, C, D, E) = 0 + \bar{0}.B + 0.D.(B + E).(B.C + D.E) = B$$

$$F(1, B, C, D, E) = 1 + \bar{1}.B + 1.D.(B + E).(B.C + D.E) = 1$$

$$\begin{aligned} F(A, B, C, D, E) &= \bar{A}.F(0, B, C, D, E) + A.F(1, B, C, D, E) \\ &= \bar{A}.B + A.1 = A + \bar{A}.B = A + B \end{aligned}$$

More on Shanon's Expansion Theorem

$$F(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot F(0, x_2, x_3, \dots, x_N) + x_1 \cdot F(1, x_2, x_3, \dots, x_N)$$

$$F(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot [x_2' \cdot F(0, 0, x_3, \dots, x_N) + x_2 \cdot F(0, 1, x_3, \dots, x_N)] + x_1 \cdot [x_2' \cdot F(1, 0, x_3, \dots, x_N) + x_2 \cdot F(1, 1, x_3, \dots, x_N)] \quad \leftarrow \text{Nesting}$$

$$F(x, y) = x' \cdot F(0, y) + x \cdot F(1, y) = x' \cdot [y' \cdot F(0, 0) + y \cdot F(0, 1)] + x \cdot [y' \cdot F(1, 0) + y \cdot F(1, 1)] \quad \leftarrow \text{For 2 variables}$$

$$= x' \cdot y' \cdot F(0, 0) + x' \cdot y \cdot F(0, 1) + x \cdot y' \cdot F(1, 0) + x \cdot y \cdot F(1, 1)$$

Example:

$$F(x, y) = x + x' \cdot y \quad \Rightarrow \quad F(0, 0) = 0 + 0' \cdot 0 = 0; \quad F(0, 1) = 0 + 0' \cdot 1 = 1;$$

$$F(1, 0) = 1 + 1' \cdot 0 = 1; \quad F(1, 1) = 1 + 1' \cdot 1 = 1;$$

x	y	F(x,y)
0	0	0
0	1	1
1	0	1
1	1	1

$$F(x, y) = x' \cdot y' \cdot 0 + x' \cdot y \cdot 1 + x \cdot y' \cdot 1 + x \cdot y \cdot 1 = x' \cdot y + x \cdot y' + x \cdot y \quad \leftarrow \text{In Truth Table, o/p is 1 in 3 rows}$$

$$= x' \cdot y + x \cdot (y + y') = x' \cdot y + x \cdot 1 = x + x' \cdot y$$

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ M. Morris Mano, and Michael D. Ciletti, Digital Design 5e, Pearson
- ❑ Technical documents from <http://www.ti.com> accessed on Oct. 08, 2018