

Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 21


Class Test 2:

29-10-2020 (THU): 8:00 – 8:55 AM

Syllabus: Logic families (not covered in CT1) and primarily post CT1, shall include concept dealt in pre-CT1 part which forms the pre-requisite.

Characteristic Equation: *SR*

<i>S</i>	<i>R</i>	<i>Q_n</i>	<i>Q_{n+1}</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	N.A.
1	1	1	N.A.

 

$$Q_{n+1} = S + \overline{R} Q_n$$

<i>S</i>	<i>R</i>	<i>Q_{n+1}</i>
0	0	<i>Q_n</i>
0	1	0
1	0	1
1	1	N.A.

Characteristic Equation: *JK*

<i>J</i>	<i>K</i>	<i>Q_n</i>	<i>Q_{n+1}</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

<i>JK</i>					
<i>Q_n</i>		0 0	0 1	1 1	1 0
	0	0	0	1	1
	1	1	0	0	1

$$Q_{n+1} = J \overline{Q}_n + \overline{K} Q_n$$


<i>J</i>	<i>K</i>	<i>Q_{n+1}</i>
0	0	<i>Q_n</i>
0	1	0
1	0	1
1	1	<i>Q_n'</i>

Characteristic Equation: D and T

D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

D	Q_n	
	0	1
0	0	1
1	0	1

$$Q_{n+1} = D$$

 

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

T	Q_n	
	0	1
0	0	1
1	1	0

$$Q_{n+1} = T\overline{Q}_n + \overline{T}Q_n$$

Excitation Table: *SR*

- It presents what input should be placed to cause a specific transition of the Flip-Flop when clock triggers.
- It can be obtained from Flip-Flop Truth Table.

<i>S</i>	<i>R</i>	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	N.A.

Consider *SR* Flip-Flop with $Q_n = 0$

If $SR = 00$, $Q_{n+1} = 0$

If $SR = 01$, $Q_{n+1} = 0$

i.e. if $SR = 0X$, $Q_{n+1} = 0$

Therefore for *SR* FF,

If $Q_n \rightarrow Q_{n+1} = 0 \rightarrow 0$

then its input *SR* before clock trigger

$SR = 00$ or 01 i.e. $0X$

$Q_n \rightarrow Q_{n+1}$		<i>S</i>	<i>R</i>
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0

Excitation Table of *SR* Flip-Flop

Excitation Table: *JK*, *D* and *T*

$Q_n \rightarrow Q_{n+1}$		J	K
0	0	0	×
0	1	1	×
1	0	×	1
1	1	×	0

$Q_n \rightarrow Q_{n+1}$		D
0	0	0
0	1	1
1	0	0
1	1	1





$Q_n \rightarrow Q_{n+1}$		T
0	0	0
0	1	1
1	0	1
1	1	0

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	Q_n'

D	Q_{n+1}
0	0
1	1

T	Q_{n+1}
0	Q_n
1	Q_n'

State Transition Diagram

    


$Q_n \rightarrow Q_{n+1}$	S	R
0 0	0	×
0 1	1	0
1 0	0	1
1 1	×	0

It can be directly
obtained from
excitation table.

An Example

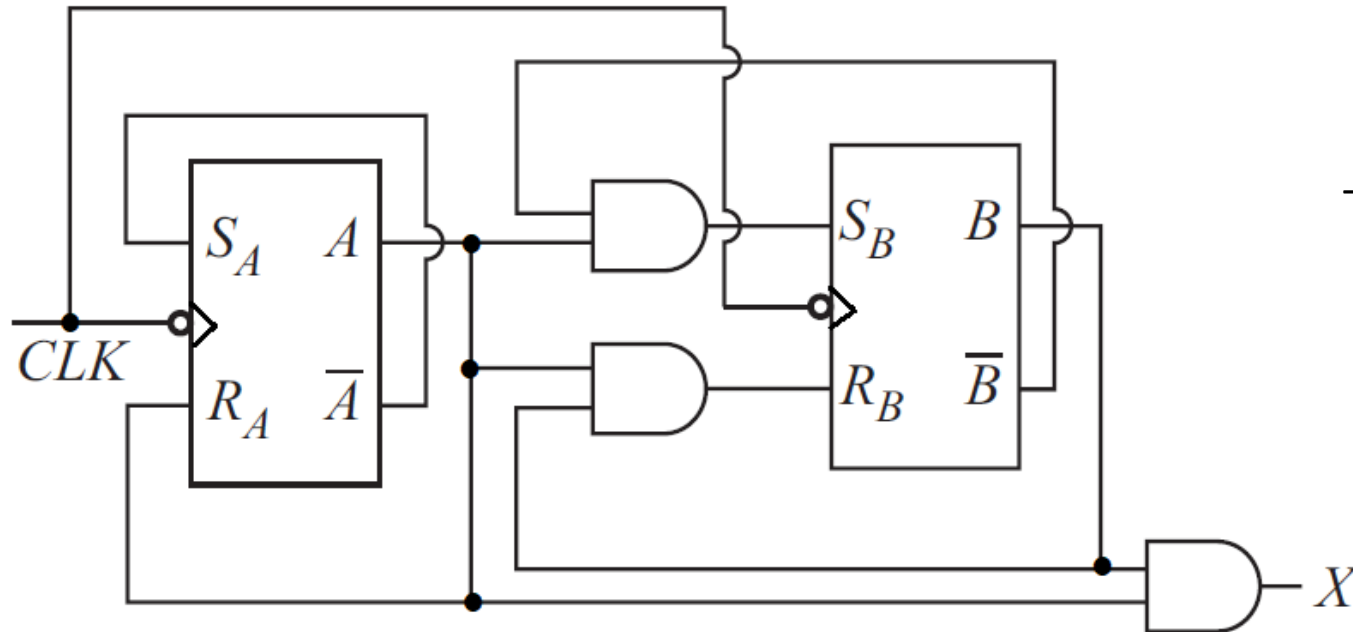
- To analyse the circuit and find how states change with the input clock and how output is generated.



Note that,

- for the basic logic gate part of the circuit, output will be considered as immediately available when input is presented and
- for the flip-flop / memory element part of the circuit, its output change as per **Truth Table / Characteristic Eqn.** waits till the clock trigger.
- Basic gate delay is negligible compared to clock time period. Effect of those delay will be considered later.

Defining Flip-Flop Inputs and Output

 

For Flip-Flop A,

$$S_A = A_n'$$
$$R_A = A_n$$

For Output,

$$X = A_n \cdot B_n$$

For Flip-Flop B,

$$S_B = A_n \cdot B_n'$$
$$R_B = A_n \cdot B_n$$

State Analysis Table

Current State		Current Flip-Flop Input					Next State		Output
CLK	B_n	A_n	S_B	R_B	S_A	R_A	B_{n+1}	A_{n+1}	X
0	0	0	0	0	1	0	0	1	0
1	0	1	1	0	0	1	1	0	0
2	1	0	0	0	1	0	1	1	0
3	1	1	0	1	0	1	0	0	1
4	0	0	0	0	1	0	0	1	0
5	0	1			...				

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	N.A.

$$S_A = A_n'$$

$$R_A = A_n$$


$$X = A_n \cdot B_n$$

$$S_B = A_n \cdot B_n'$$

$$R_B = A_n \cdot B_n$$

- Clock 0: The initial state is assumed to be 0 for each flip-flop.
- Clock n : Next state of clock $(n - 1)$ is the present state at clock n and the circuit evolves.
- State transition as per Flip-Flop Truth Table for the input present.

Analysis Result

 

The circuit generates an **output = 1** at **every 4th clock** trigger when it reaches the state **$BA = 11$** and repeats the state transition **$00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$**

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill