

Digital Electronic Circuits


Section 1 (EE, IE)

Lecture 11

MUX: non-inverted output

IC 74153

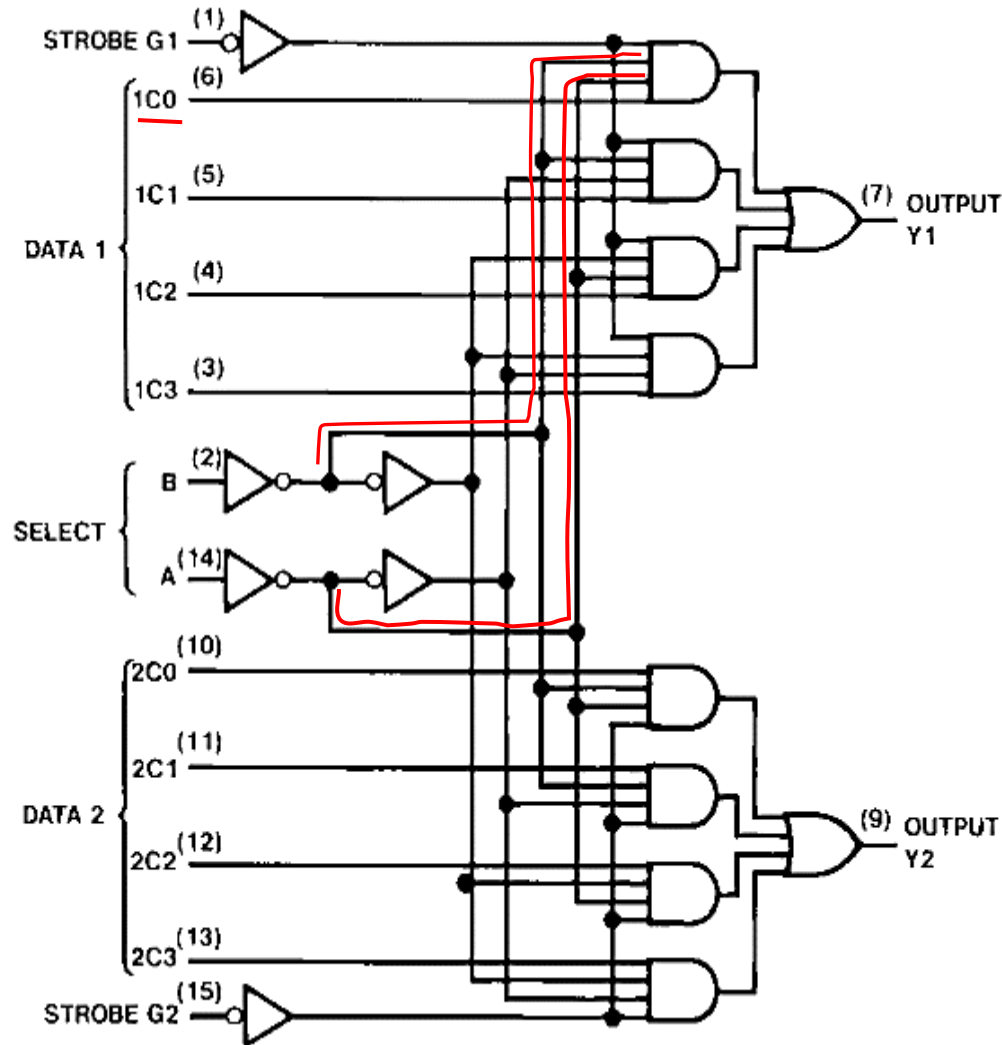
$$Y = E'.[(B'.A').C0 + (B'.A).C1 + (B.A').C2 + (B.A).C3]$$




STROBE (G)	B	A	Y
H	X	X	L
L	L	L	C0
L	L	H	C1
L	H	L	C2
L	H	H	C3

MUX: inverted output (IC 74150)

INPUTS					OUTPUT W
SELECT				STROBE \overline{G}	
A	B	C	D		
X	X	X	X	H	H
L	L	L	L	L	$\overline{E0}$
L	L	L	H	L	$\overline{E1}$
L	L	H	L	L	$\overline{E2}$
L	L	H	H	L	$\overline{E3}$
L	H	L	L	L	$\overline{E4}$
L	H	L	H	L	$\overline{E5}$
L	H	H	L	L	$\overline{E6}$
L	H	H	H	L	$\overline{E7}$
H	L	L	L	L	$\overline{E8}$
H	L	L	H	L	$\overline{E9}$
H	L	H	L	L	$\overline{E10}$
H	L	H	H	L	$\overline{E11}$
H	H	L	L	L	$\overline{E12}$
H	H	L	H	L	$\overline{E13}$
H	H	H	L	L	$\overline{E14}$
H	H	H	H	L	$\overline{E15}$

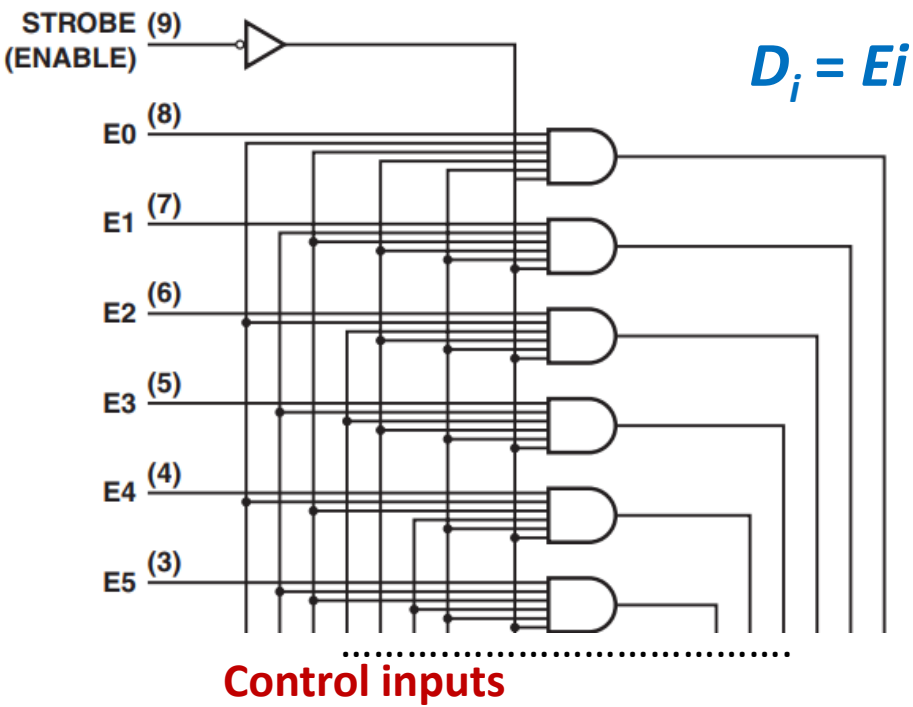

$$Y = (E'.A'B'C'D'.D_0 + E'.A'B'C'D.D_1 + \dots + E'.ABCD'.D_{14} + E'.ABCD.D_{15})'$$

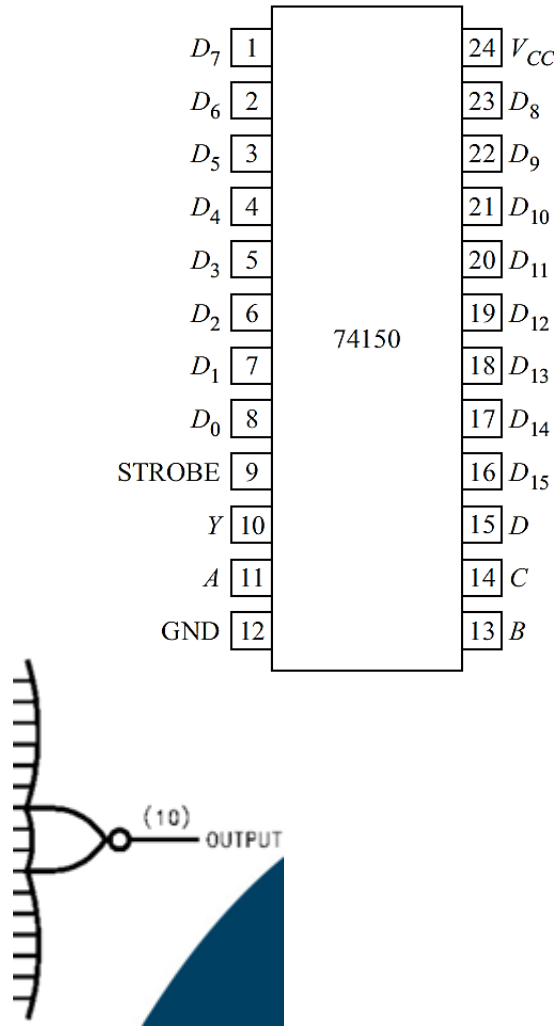


IC 74153

$$Y = E'.[(B'.A').C0 + (B'.A).C1 + (B.A').C2 + (B.A).C3]$$


	B	A	Y
F(0,0)	L	L	0
F(0,1)	L	H	1
F(1,0)	H	L	1
F(1,1)	H	H	0

$$Y = B'.A + B.A'$$
 
$$Y = (B'.A').0 + (B'.A).1 + (B.A').1 + (B.A).0$$




$$Y = F(A,B,C) \\ = \sum m(0,2,3,6,7)$$

 

IC 74151
8-to-1 MUX
with STROBE (EN'),
**both non-inverted
and inverted
output**

Multiplexer as Universal Logic Circuit

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

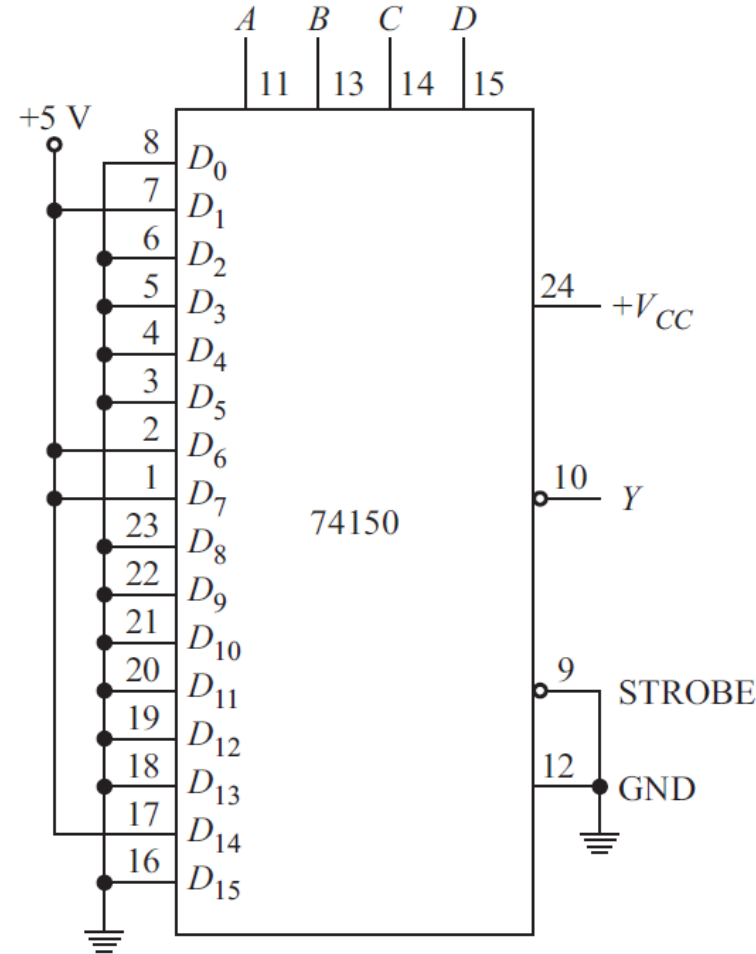

$$Y = (E'.A'B'C'D'.D_0 + E'.A'B'C'D.D_1 + \dots + E'.ABCD'.D_{14} + E'.ABCD.D_{15})'$$


$$E = 0,$$

$$Y' = A'B'C'D'.D_0 + A'B'C'D.D_1 + \dots + ABCD'.D_{14} + ABCD.D_{15}$$

$$Y = F(A,B,C,D) \\ = \sum m(0,2,3,4,5,8,9, \\ 10,11,12,13,15)$$

$$Y' = \sum m(1,6,7, 14)$$

Entered Variable and Multiplexer

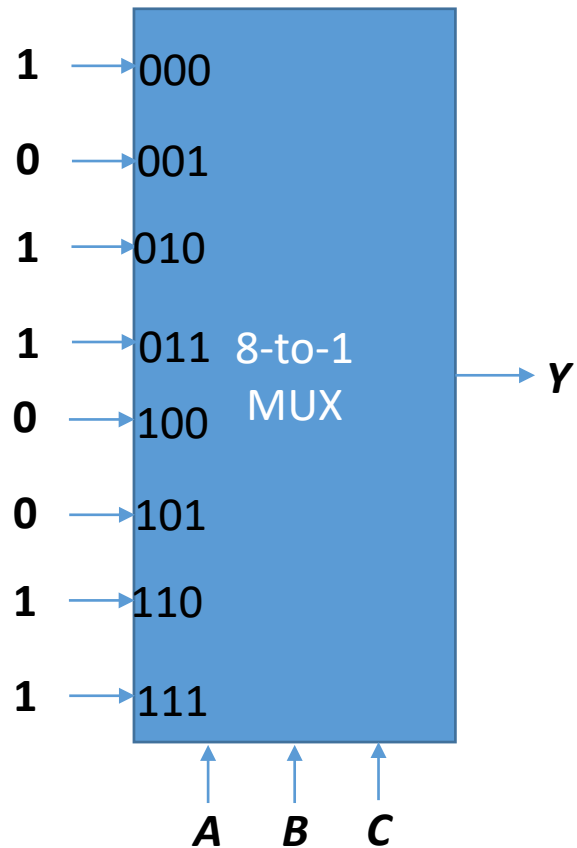


	A	B	C	Y
$Y=C'$	0	0	0	1
	0	0	1	0
$Y=1$	0	1	0	1
	0	1	1	1
$Y=0$	1	0	0	0
	1	0	1	0
$Y=1$	1	1	0	1
	1	1	1	1

A	B	Y
0	0	C'
0	1	1
1	0	0
1	1	1

$$Y = F(A, B, C)$$


$$= \sum m(0, 2, 3, 6, 7)$$

 

8-to-1 MUX and 4-variable function

$Y = F(A,B,C,D)$
 $= \sum m(0,2,3,4,5,8,9,10,11,12,13,15)$



<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1

 


IC 74151
EN = 0

<i>ABC</i>	000	001	010	011	100	101	110	111
<i>D</i> = 0	1	1	1	0	1	1	1	0
<i>D</i> = 1	0	1	1	0	1	1	1	1
<i>Y</i>	<i>D'</i>	1	1	0	1	1	1	<i>D</i>
8-to-1 MUX data input	$D_0 = D'$	$D_1 = 1$	$D_2 = 1$	$D_3 = 0$	$D_4 = 1$	$D_5 = 1$	$D_6 = 1$	$D_7 = D$

Nibble Multiplexer

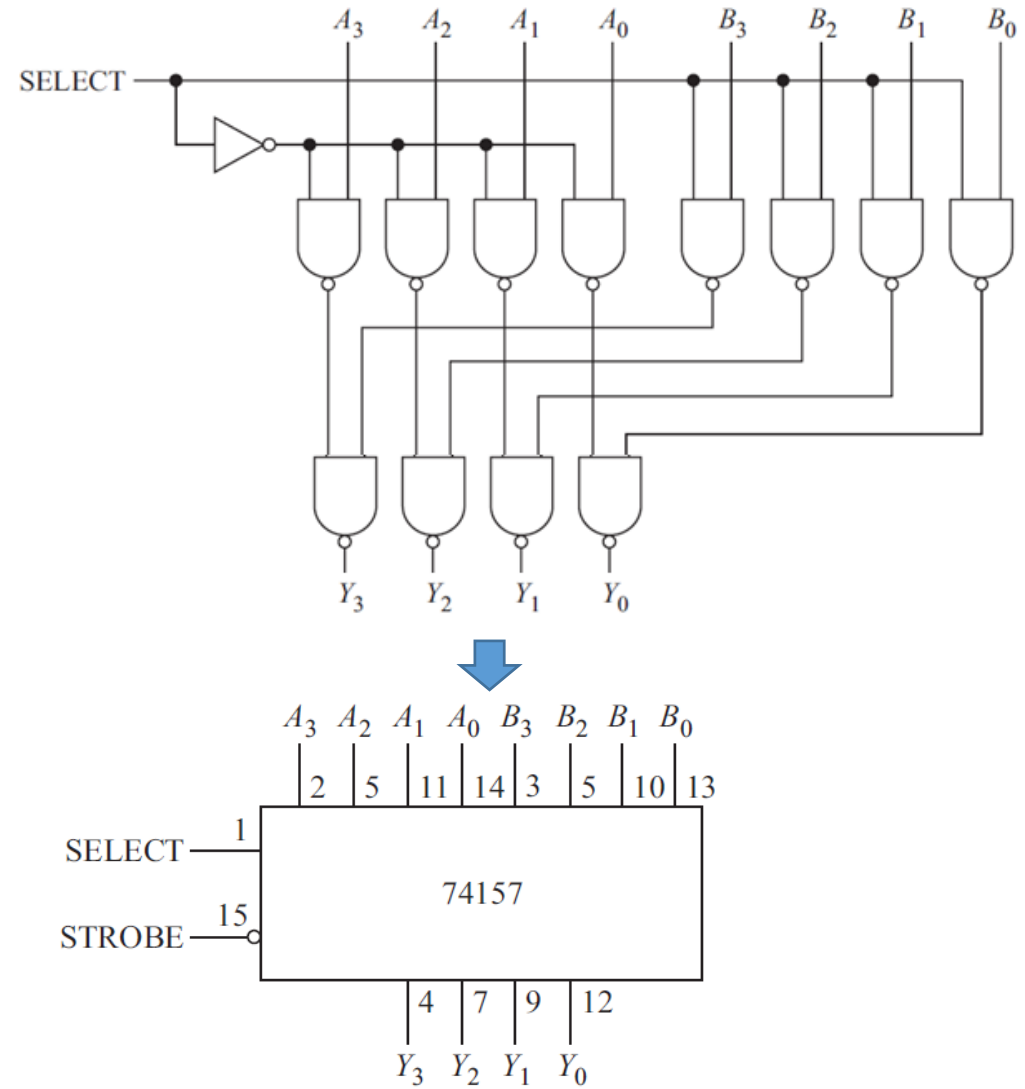 


Nibble Multiplexer with Tristated Output

 

OE'	SELECT	Y
H	X	High Z
L	L	A
L	H	B

IC 74257

BUS Architecture and Tristated Output

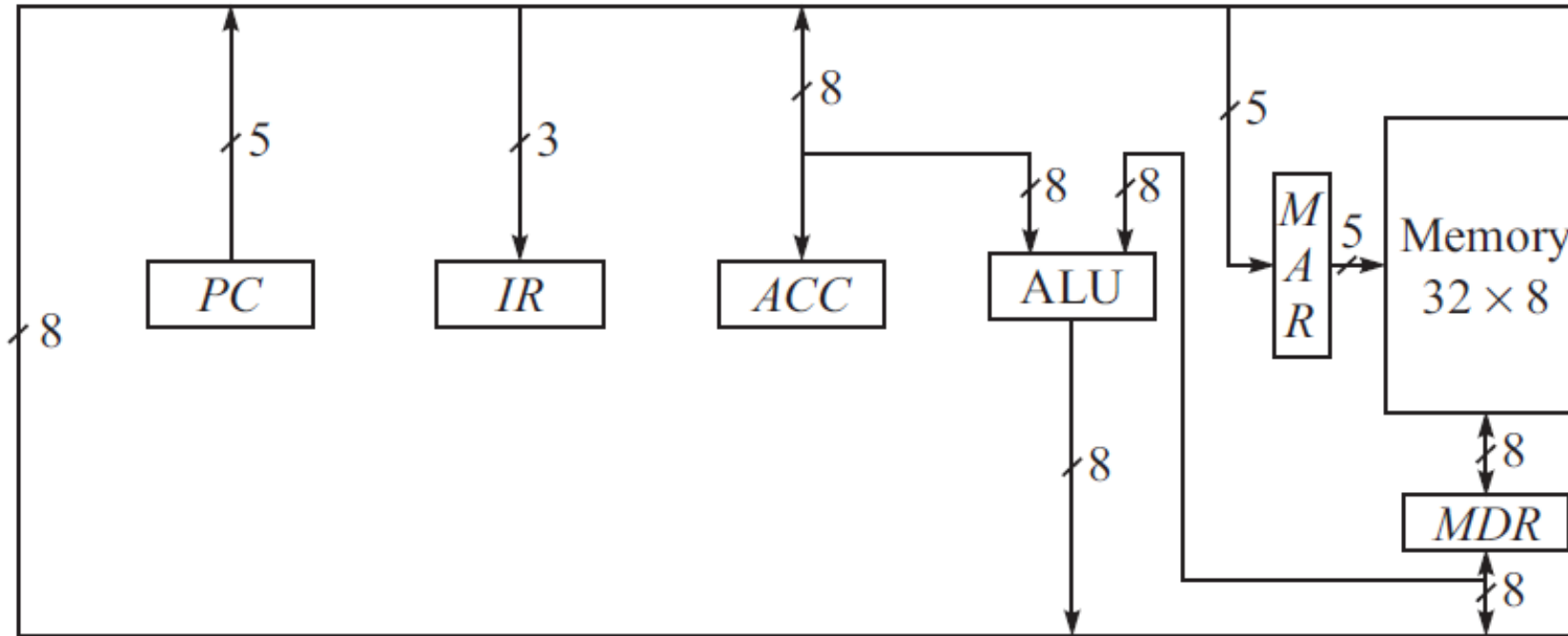

An Example

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill\
- ❑ Technical documents from <http://www.ti.com> accessed on Oct. 08, 2018