

# **Tutorial 2**

## **EC31003: Digital Electronic Circuits**

# Questions

1. Simplify the following Boolean functions using k-map:
  - a.  $Y(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$
  - b.  $Y(A, B, C, D) = \prod M(0, 1, 2, 5, 6, 8, 10, 13, 14)$
  - c.  $Y(A, B, C, D) = \sum m(2, 3, 4, 5) + \sum d(10, 11, 12, 13, 14, 15)$
  
2. Consider the function  $F(P, Q, R, S) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$   
Find the number of:
  - a. *Prime Implicants*
  - b. *Essential Prime Implicants*
  
3. A digital circuit with three inputs (a, b, and, c) performs the following function:  
 $F(a, b, c) = abc' + b'$ 
  - a. Find the min-terms of the output expression  $F(a, b, c)$ .
  - b. Find the min-terms of the expression  $F'(a, b, c)$ .

4. Consider the following truth tables for addition ('+'), multiplication ('x') and division('/') operation,

A+B

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

A x B

A	B	A x B
0	0	0
0	1	0
1	0	0
1	1	1

A/B

A	B	A/B
0	0	0
0	1	0
1	0	X (Don't care)
1	1	1


Find the Boolean logic (using k-map minimization) for the expression:  $F = (A + (B \times C)) / D$

5. Solve the POS function of 5 variable K-map using the following expression

$$f(P, Q, R, S, T) = \prod M(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$$

# Solution 1 (a)

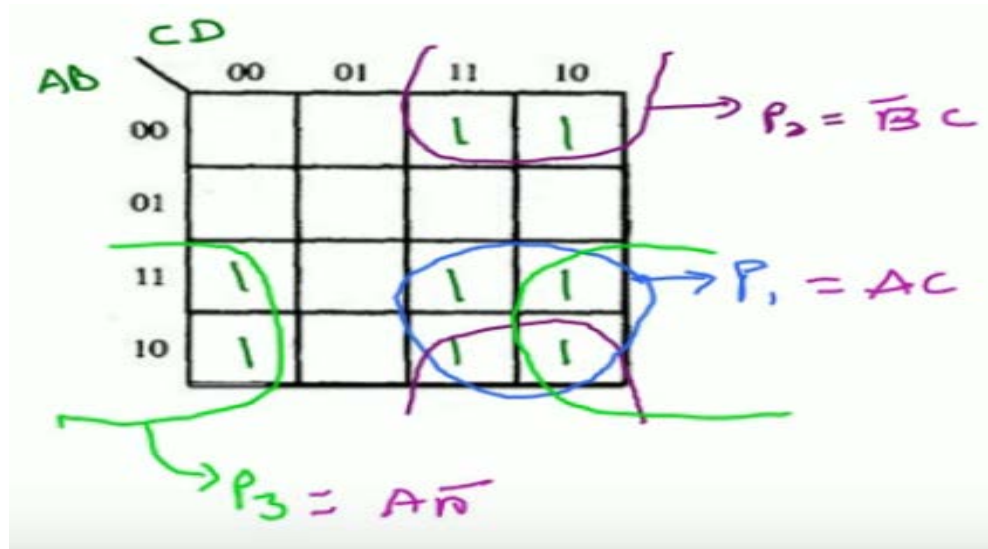1. a.  $Y(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$



$$Y = AD' + AC + B'C$$

# Solution 1(b)

1 b.  $Y(A, B, C, D) = \prod M(0,1,2,5,6,8,10,13,14)$

		CD				
			00	01	11	10
AB	00	0	0			0
	01		0			0
	11		0			0
	10	0				0

$$Y = (A+B+C)(B+D)(B'+C+D')(C'+D)$$

# Solution 1(c)


1.c  $Y(A, B, C, D) = \sum m(2, 3, 4, 5) + \sum d(10, 11, 12, 13, 14, 15)$

AB \ CD				
	00	01	11	10
00			1	1
01	1	1		
11	X	X	X	X
10			X	X

$$Y(A, B, C, D) = BC' + B'C = B \oplus C$$
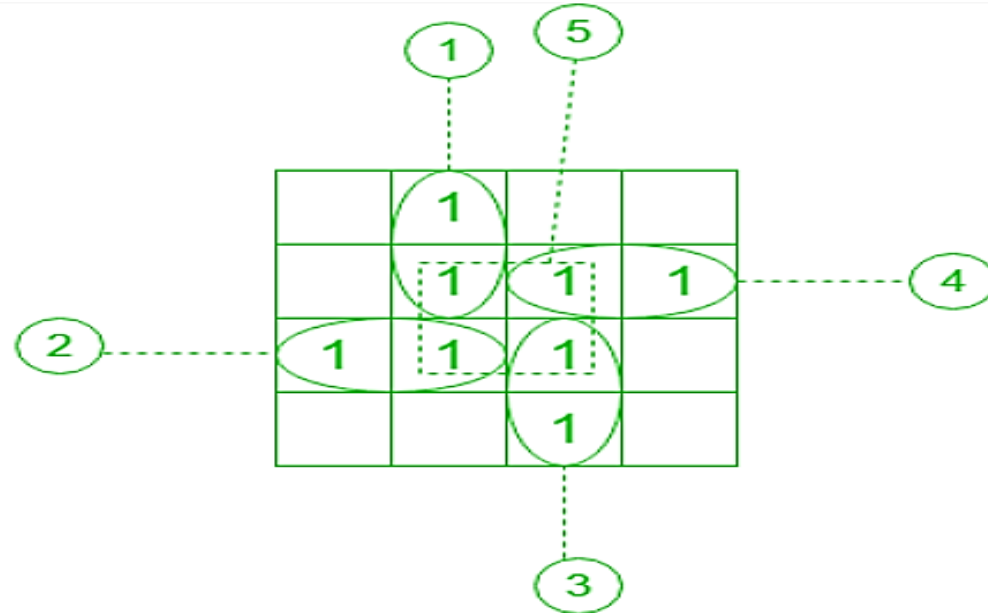
# Solution 2

$$F(P,Q,R,S) = \sum m(1,5,6,7,11,12,13,15)$$



a) No. of prime implicants = 5 (1,2,3,4,5) = ( $P'R'S$ ,  $PQR'$ ,  $PRS$ ,  $P'QR$ ,  $QS$ )

b) No. of essential prime implicants = 4 (1,2,3,4) = ( $P'R'S$ ,  $PQR'$ ,  $PRS$ ,  $P'QR$ )

# Solution 3

a)

$$F = abc' + b'$$

$$= abc' + b'(a + a')(c + c')$$

$$= abc' + (ab' + a'b')(c + c')$$

$$= abc' + ab'c + a'b'c + ab'c' + a'b'c'$$

$$= \Sigma(0, 1, 4, 5, 6)$$

b) One approach is to find out  $F'$  and do the same as above.

Alternative, simply minterm of  $F'$  is same as maxterm of  $F$ . So, minterm of  $F'$  is  $\Sigma(2, 3, 7)$



# Solution 4

Truth table for the given expression (F) is

A	B	C	D	BxC	A+(BxC)	(A+(BxC))/D
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	1	X
0	1	1	1	1	1	1
1	0	0	0	0	1	X
1	0	0	1	0	1	1
1	0	1	0	0	1	X
1	0	1	1	0	1	1
1	1	0	0	0	1	X
1	1	0	1	0	1	1
1	1	1	0	1	1	X
1	1	1	1	1	1	1



K-map minimization of minterms  
devised from Truth table

	C'D'	C'D	CD	CD'
A'B'				
A'B			1	X
AB	X	1	1	X
AB'	X	1	1	X

Hence, final answer is,  
 $F = A + BC$
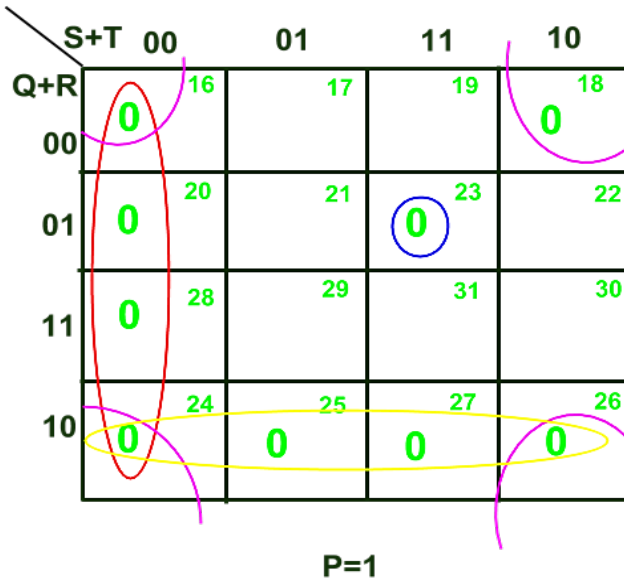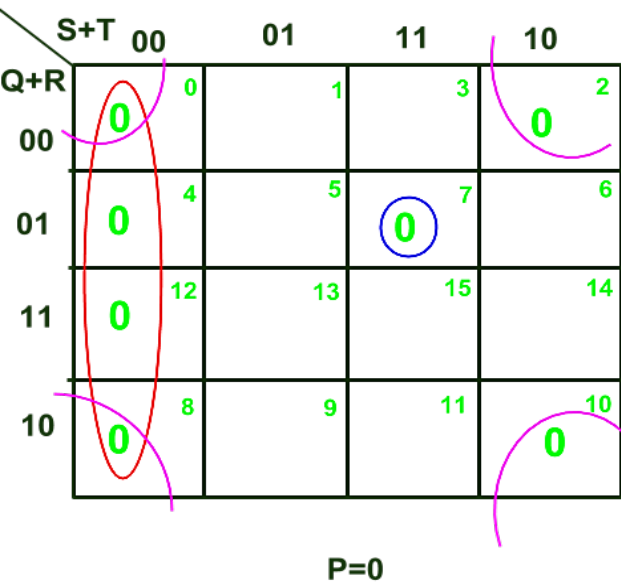
# Solution 5

5 variable POS function:  $f(P,Q,R,S,T) = \prod M(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$



In this K-Map we have 4 sub-cubes:

**Subcube 1:** The one marked in red comprises of cells ( 0, 4, 8, 12, 16, 20, 24, 28) =  $S+T$

**Subcube 2:** The one marked in blue comprises of cells (7, 23) =  $Q+R'+S'+T'$

**Subcube 3:** The one marked in pink comprises of cells ( 0, 2, 8, 10, 16, 18, 24, 26) =  $R+T$

**Subcube 4:** The one marked in yellow comprises of cells (24, 25, 26, 27) =  $P'+Q'+R$

Therefore the minimal expression of the given Boolean Function can be expressed as follows :

$$f(P,Q,R,S,T) = (S+T) \cdot (Q+R'+S'+T') \cdot (R+T) \cdot (P'+Q'+R)$$