

Tutorial 3


EC31003: Digital Electronic Circuits

1. Identify the type of hazard and show the corresponding hazard free implementation for the following Boolean expression $F(A,B,C,D) = (A+C)(A'+D')(B'+C'+D)$.
2.
 - a. Represent the following expression using two-input NAND gate: $Y = AB+B'C+CD'E+DEF'$
 - b. Find the total cost of the following expression?
 $Y = ((P+Q)' + (((R+S)')' + T)')'$
 - c. Find the value of Gate input cost G and GN from the following POS function:
 $F(A,B,C,D) = \prod M(0, 1, 4, 7).D(6, 11, 14, 15)$
3.
 - a. Draw the KMap for the function $F(A,B,C,D) = \prod M(2, 3, 6, 8, 9, 12, 13, 14)$
 - b. Determine the minimized function in product of sums form.
 - c. Are there any static-0 hazards in the minimized function? If yes, find them and eliminate them.


4. Write the truth table for the following Boolean expression , and realize it using only an 8:1 multiplexer.

$$F(A,B,C,D)=\overline{A}\overline{B} + BD + AB\overline{C}.$$

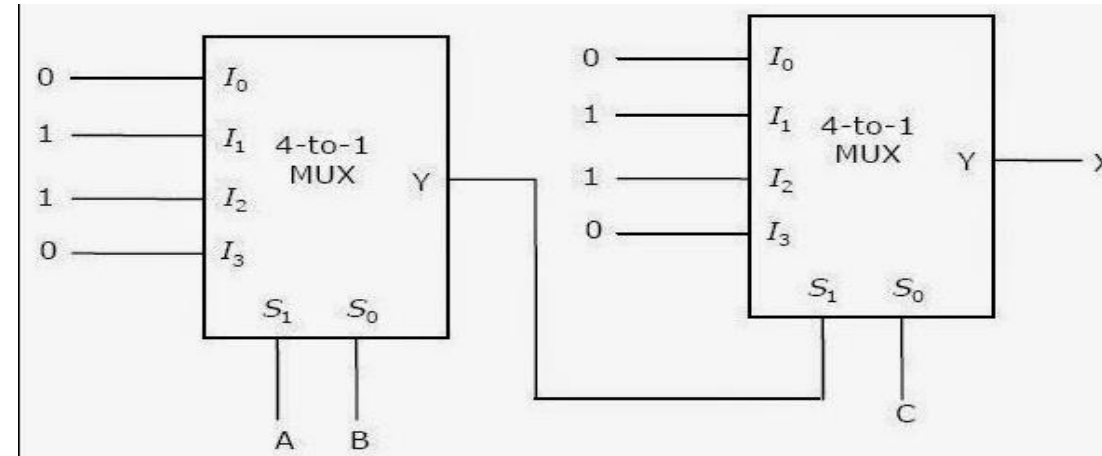
5. a. In the following circuit X is given by -



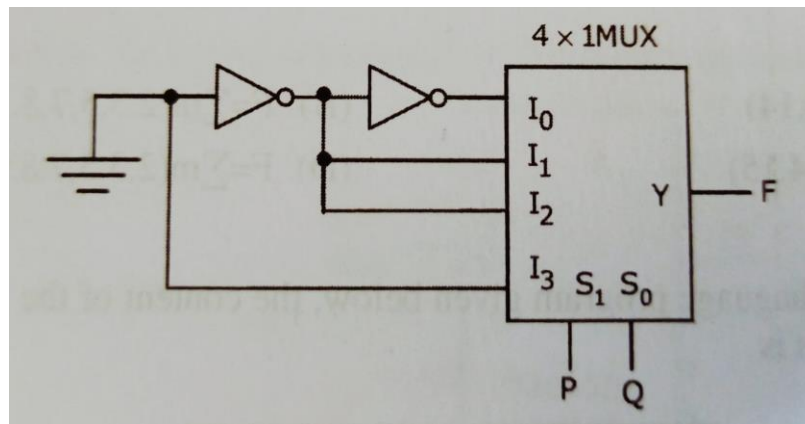- b. Find the logic function F implemented by the below multiplexer.




- c. Find the canonical POS form solution of the below diagram.

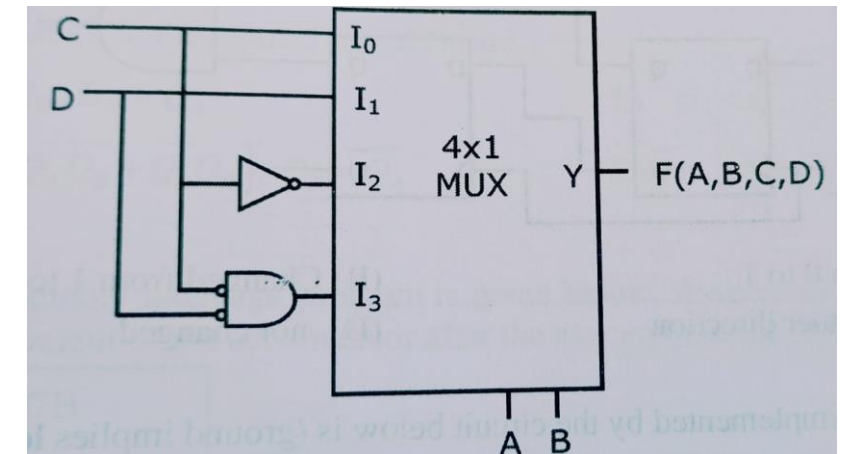

Solution 1

Static 0 hazard.

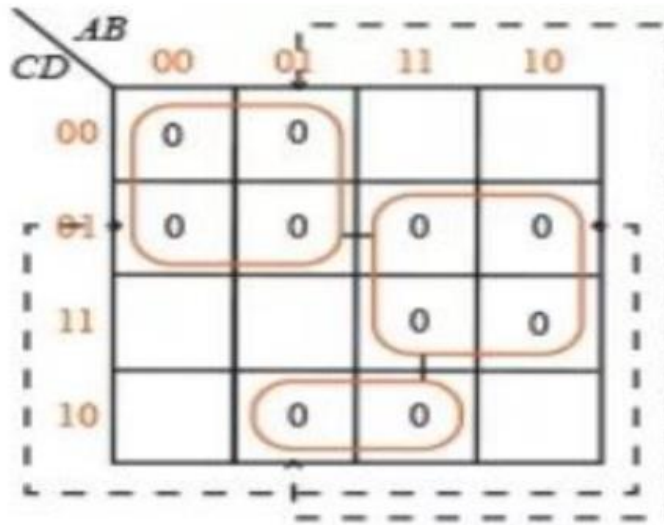
The K-map implementation for the expression is shown below. It has four pairs of adjacent 0's that are not covered by a common loop. The arrows indicate each 0 which is not being looped which causes a 0 hazard. If $A=0$, $B=1$, $D=0$ and C changes from 0 to 1, there is a chance that spike can appear at the output for any combination of gate delays.



Solution 1 (cont.)

Elimination of this hazard can be done using three additional loops in the K Map which includes the redundant terms and this will eliminate the 0-hazards,
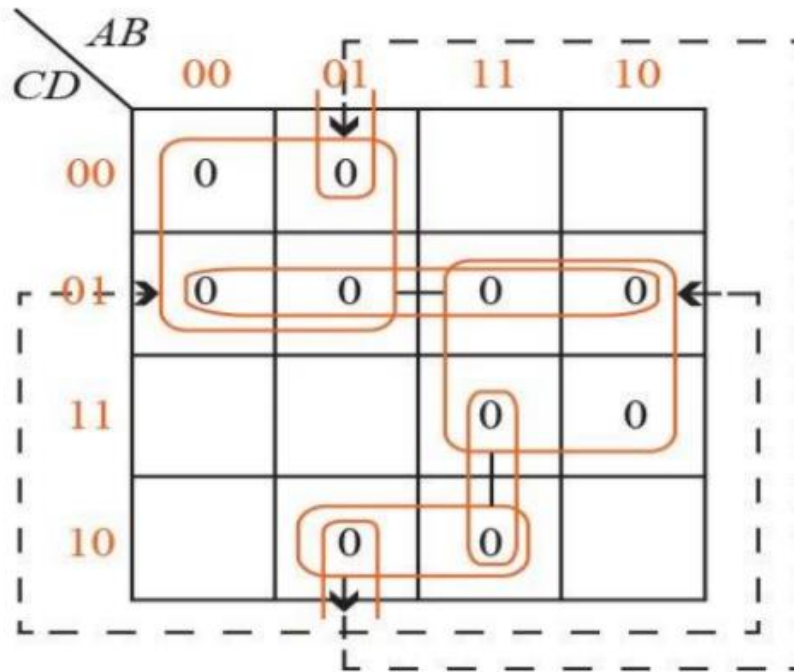
$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$



The final K Map

Solution 2 (a)

a. $Y = ((AB)'. (B'C)'. (((CD')')'E)'. (((DE)')'F')')'$

Solution 2 (b)

b. Total Cost(TC) = Number of gates +
Number of gate Inputs

$$= 5 + 10 = 15$$


Note: Here, we have considered 2-input NOR gate implementation. If we consider two-level with no restriction in fan-in of logic gates then the expression will be $(P+Q)(R+S+T)$ and number of gate inputs will be $5+2=7$. As, here we used two-input NOR gate implementation so the no. of gate inputs $= 5 \times 2 = 10$

a. b. $Y = ((P+Q)' + (((R+S)')' + T)')'$ (2-input NOR gate)

Total cost = Number of gates + Number of gate inputs

No. of gates = 5

No. of gate inputs = $(2 \times 5) = 10$

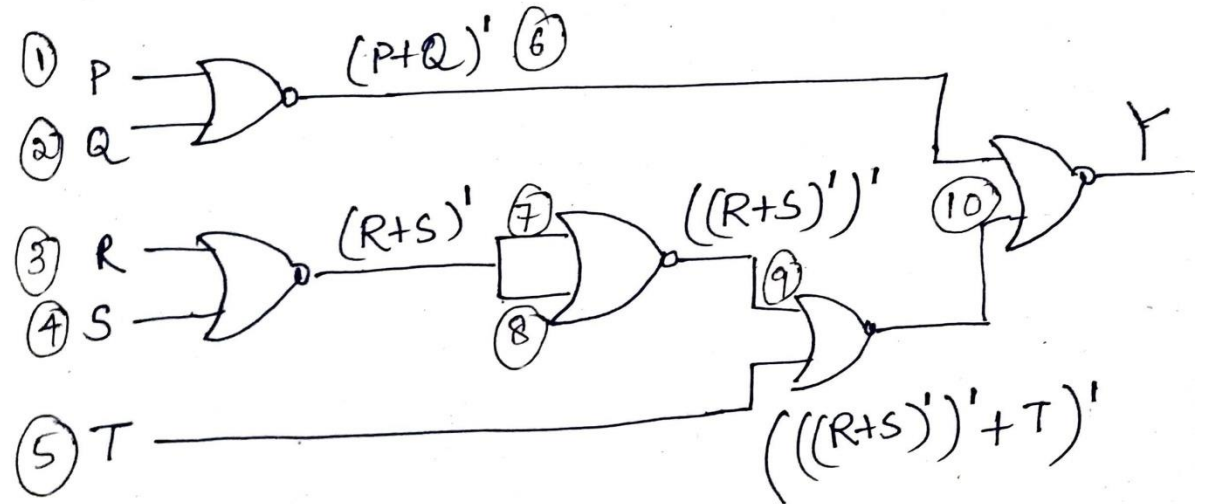

\therefore No. of gate inputs = 10

Total cost = $5 + 10 = 15$

Solution 2 (c)

2c. G (Gate input cost without counting NOT gates)

GN (Gate input cost counting NOT gates)

$$F = \prod M(0, 1, 4, 7) \cdot D(6, 11, 14, 15)$$

$$= (A+B+C)(A+C+D)(B'+C')$$

$$L = 8, T = 3, N = 2,$$

$$G = L+T = 11 \text{ and } GN = L+T+N=13$$


2.C

$$F(A, B, C, D) = \prod M(0, 1, 4, 7) \cdot D(6, 11, 14, 15)$$

CD \ AB	00	01	11	10
00	0	0		
01	0		0	X
11			X	X
10			X	

$$F(A, B, C, D) = (A+B+C)(A+C+D)(\overline{B}+\overline{C})$$

Solution 3

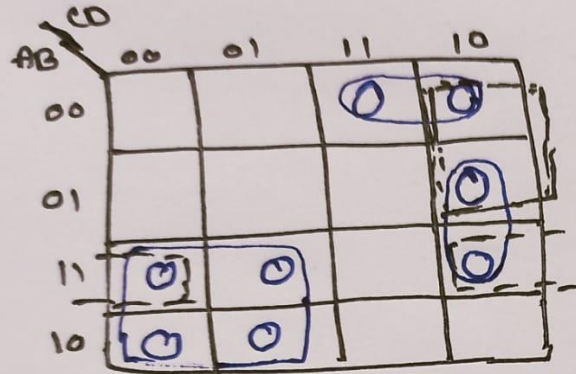

→ $(A+B+C')(B'+C'+D)(A'+C)$ → Minimized POS

→ $(A+B+C')(B'+C'+D)(A'+C) \underbrace{(A+C'+D)(A'+B'+D)}_{\text{Hazard free}}$

Solution 4

Given function is

$$\begin{aligned} f &= \overline{A}\overline{B} + BD + AB\overline{C} \\ &= \overline{A} + (\overline{B} + B)(\overline{B} + D) + AB\overline{C} \\ &= \overline{A} + \overline{B} + D + AB\overline{C} \end{aligned}$$

Truth table for the given function f is

A	B	C	D	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1


k-map

CD \ AB	00	01	11	10
00	1 ₀	1 ₁	1 ₃	1 ₂
01	1 ₄	1 ₅	1 ₇	1 ₆
11	1 ₁₂	1 ₁₃	1 ₁₅	0 ₁₄
10	1 ₈	1 ₉	1 ₁₁	1 ₁₀

realization of given function using 8×1 MUX

		BCD							
A		I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
0		(0)	(1)	(2)	(3)	(4)	(5)	(6)	(7)
1		(8)	(9)	(10)	(11)	(12)	(13)	14	(16)
		1	1	1	1	1	1	0	1

\downarrow
 \overline{A}

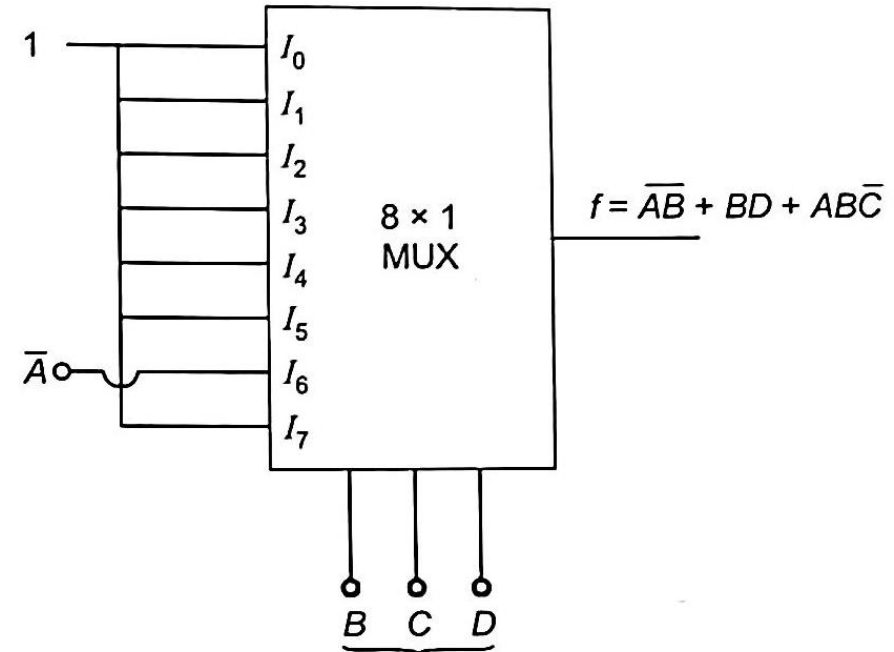

Solution 5 (a)

MUX 1

$$Y = A'B'.0 + A'B.1 + AB'.1 + AB.0$$

$$Y = A'B + AB'$$

MUX 2

$$X = Y'C'.0 + Y'C.1 + YC'.1 + YC.0$$

$$X = Y'C + YC'$$

$$X = (A'B' + AB)C + (A'B + AB')C'$$

$$X = A'B'C + ABC + A'BC' + AB'C'$$

Solution 5 (b) & (c)

Sol. 5 (b) - Output is 1 only when the select lines are PQ' or $P'Q$.

Hence,

$$F = P'Q + PQ' \rightarrow \text{XOR}(P, Q)$$

Sol. 5 (c) -

→

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

→

AB	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	1	0	0	0
10	1	1	0	0

$Y = \sum m(2, 3, 5, 7, 8, 9, 12)$

$\Rightarrow \prod M(0, 1, 4, 6, 10, 11, 13, 14, 15)$