

Digital Electronic Circuits

Section 1 (EE, IE)


Lecture 25

Counter Basics

- A counter keeps a record of the number of times a particular event has occurred by advancing its state.
- In counter, a unique state of the digital circuit is associated with a particular count.
- With every trigger, the state advancement can be
 - in any random order
 - a sequential increase (up counter)
 - a sequential decrease from a pre-defined value (down counter)
- All the flip-flops defining the state of the count get the trigger:
 - simultaneously in synchronous counter
 - at different point of time in asynchronous counter
- A modulo- n or mod- n counter has n different states. It returns to initial value after n triggers. For m flip-flops used in counter design, $2^m \geq n$.
- Usually, clock is given as input trigger. Mod- n counter is also called divided-by- n counter.

Asynchronous Up Counter



Also, called
Ripple Counter

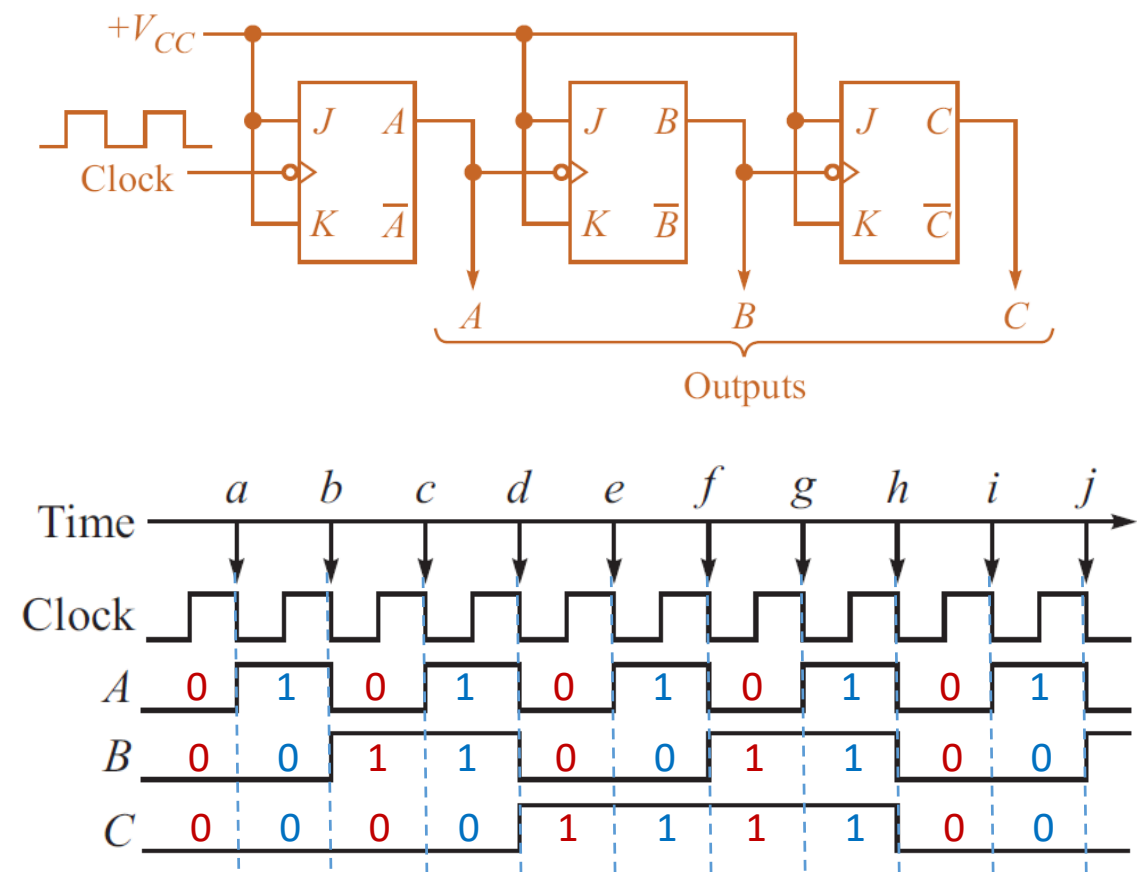

CLK↓	C	B	A	Count
-	0	0	0	0
a	0	0	1	1
b	0	1	0	2
c	0	1	1	3
d	1	0	0	4
e	1	0	1	5
f	1	1	0	6
g	1	1	1	7
h	0	0	0	0

- $f_A = f_{Clock} / 2$
- $f_B = f_{Clock} / 4$
- $f_C = f_{Clock} / 8$


Cumulative Delay

 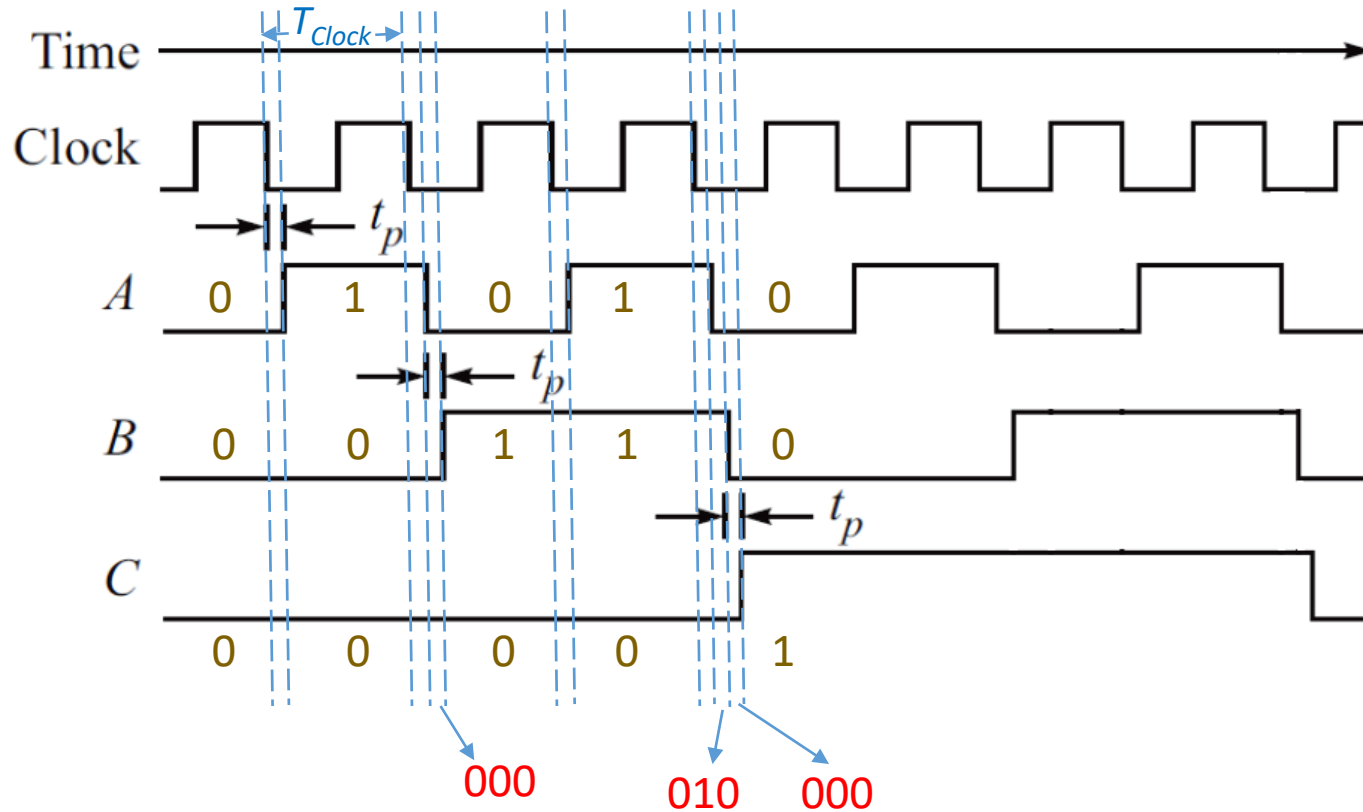

For n flip-flops, the delay is $n\tau$ where τ is propagation delay of each flip-flop.

- No miss till $n\tau < T_{clock}$
- Glitch

Asynchronous Down Counter

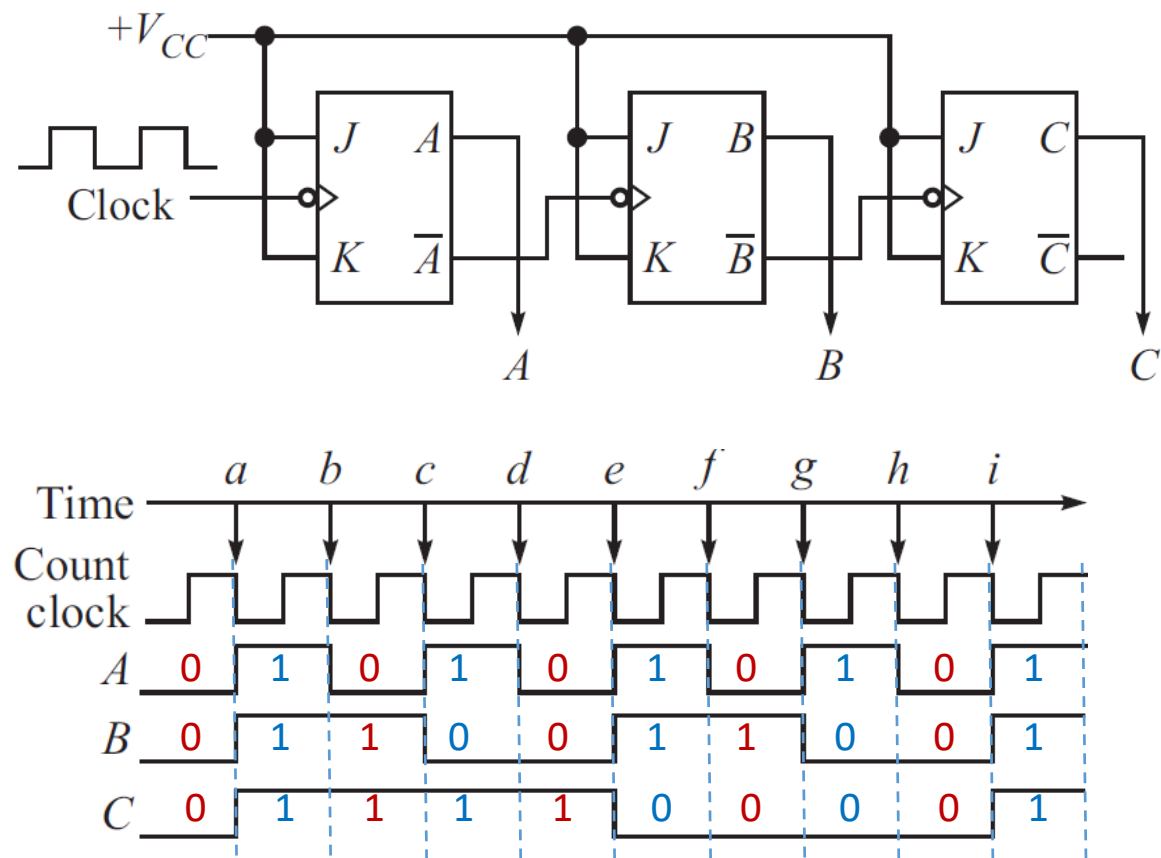


CLK↓	C	B	A	Count
-	0	0	0	0
a	1	1	1	7
b	1	1	0	6
c	1	0	1	5
d	1	0	0	4
e	0	1	1	3
f	0	1	0	2
g	0	0	1	1
h	0	0	0	0

Here, if output as $C'B'A'$, then up counter

Similarly, previous up counter circuit gives down count at its inverted outputs.

Asynchronous Up – Down Counter

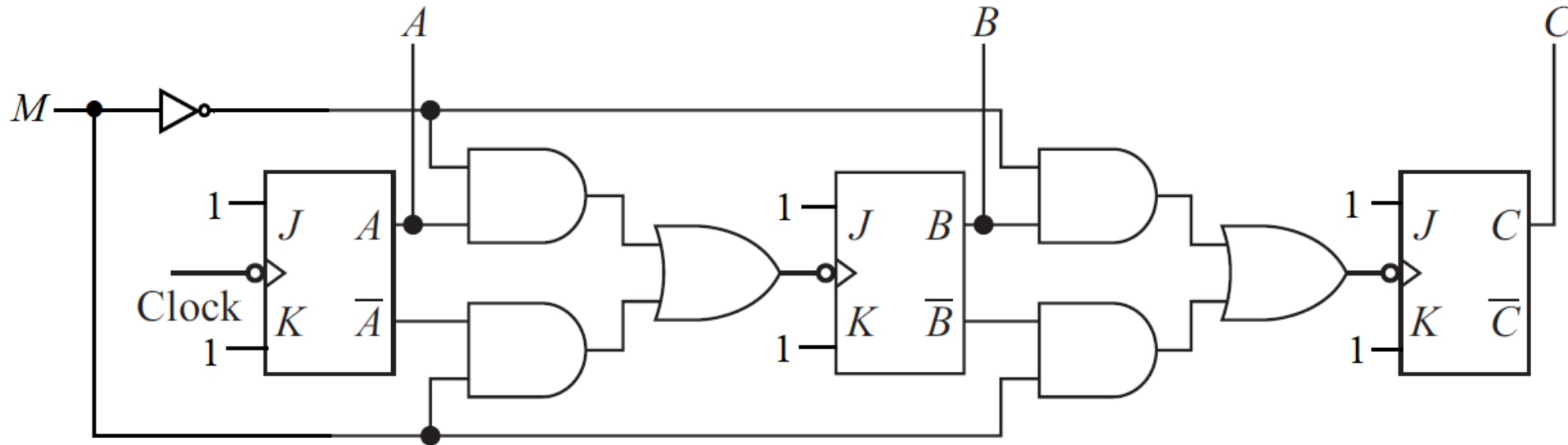


Mode, $M = 0$: Up counter

$M = 1$: Down counter

IC 7493

4-bit Asynchronous Binary Up Counter

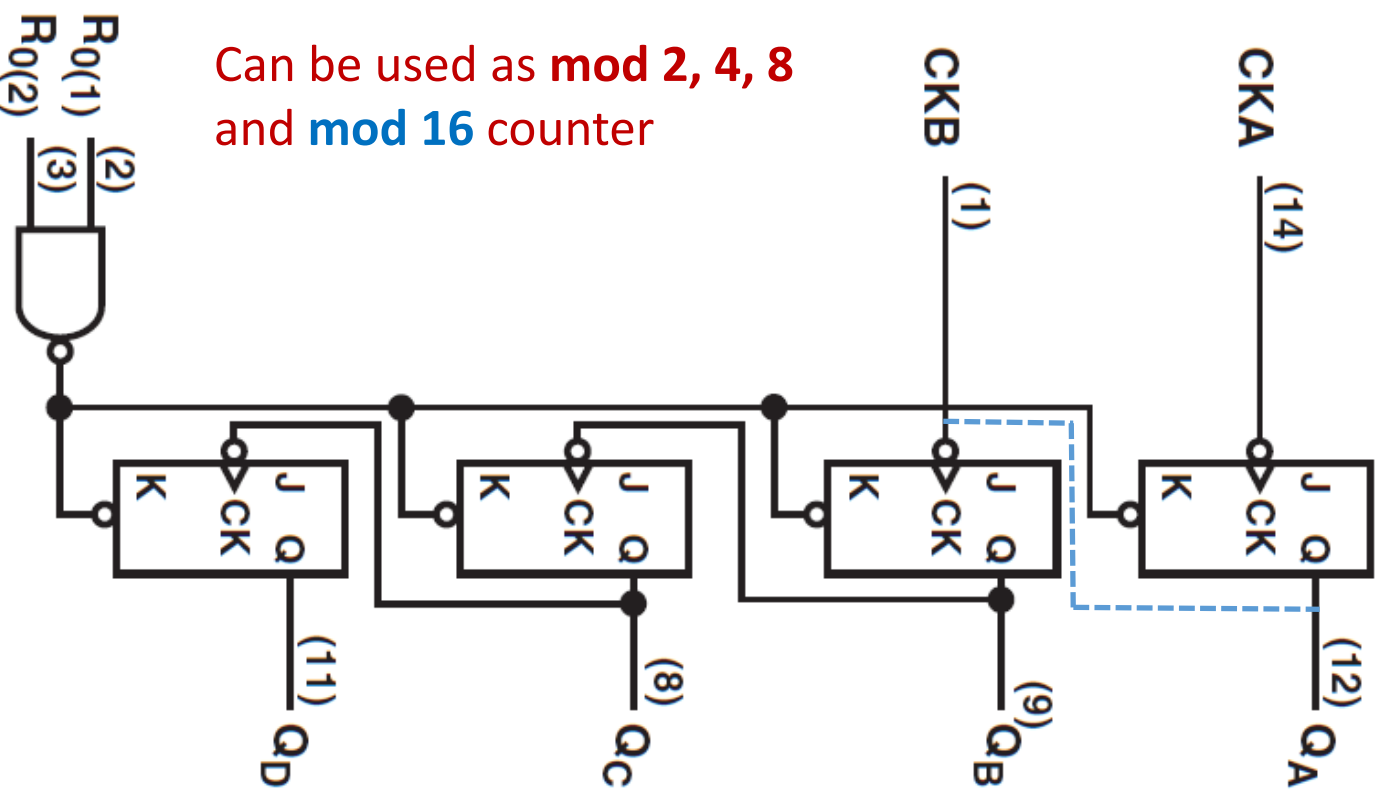

Can be used as **mod 2, 4, 8**
and **mod 16** counter


RESET/COUNT

RESET INPUTS		OUTPUTS			
R0(1)	R0(2)	Q _D	Q _C	Q _B	Q _A
H	H	L	L	L	L
L	X	COUNT			
X	L	COUNT			


Mod 8: CKA unused, CKB triggered

----- External connection (Q_A to CKB)
when used as mod 16 and
CKA triggered.




Decoding Counter State

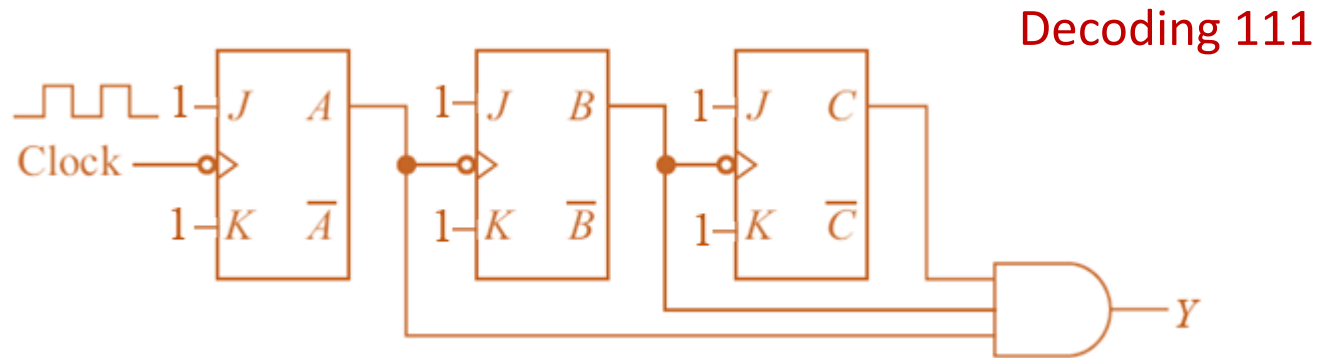

 Once in every 8 clock cycles, $Y = 1$ for 1 clock cycle whenever the state of the counter, $CBA = 111$



Decoding Logic

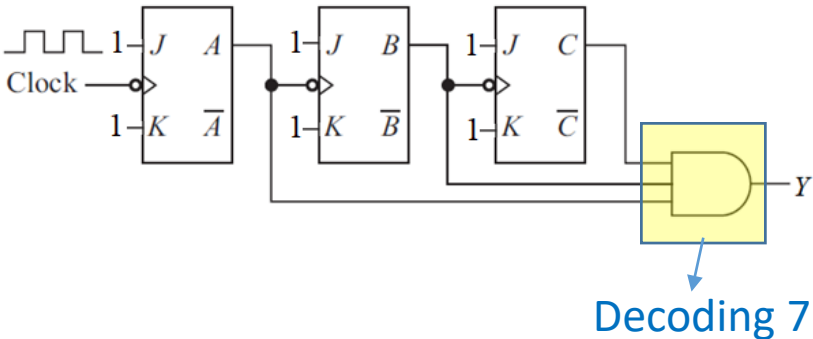 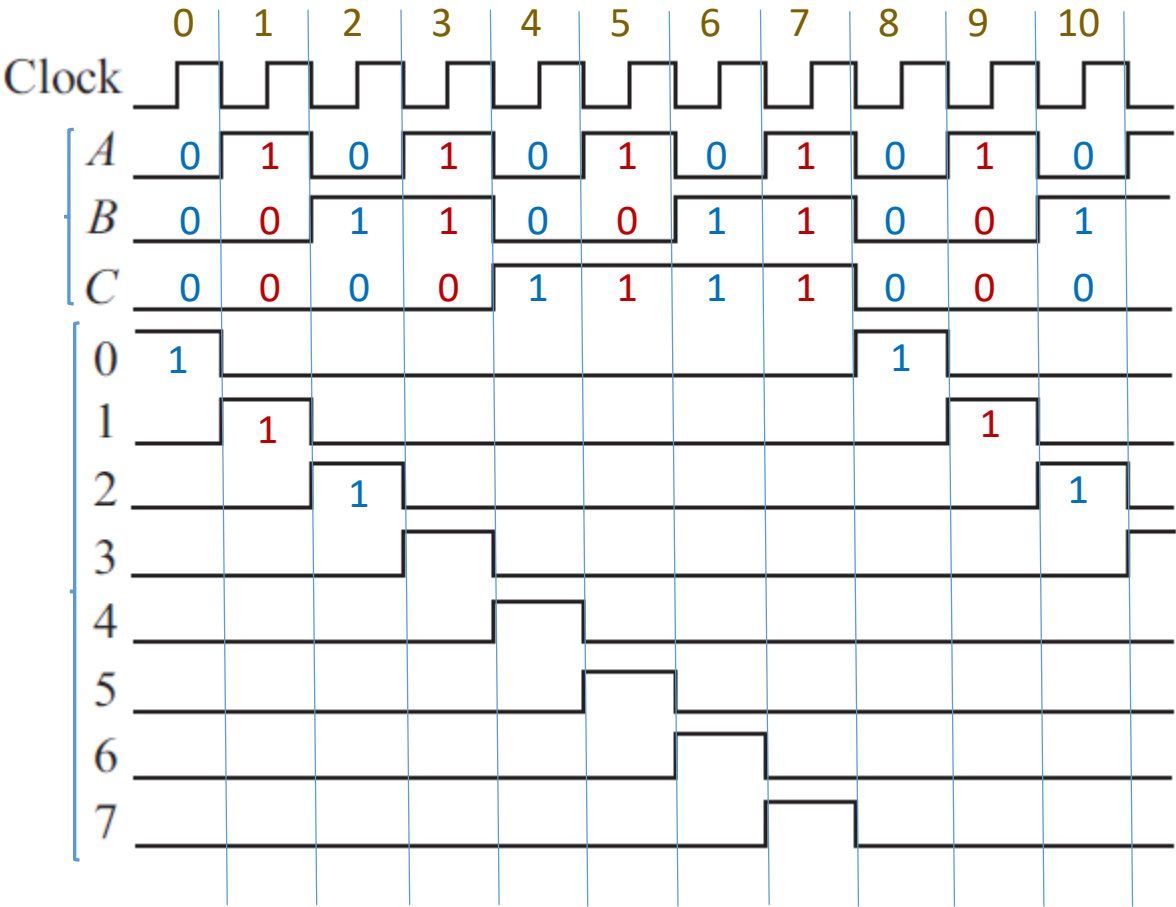



A decoding gate connected to the outputs of a counter is activated **only when the counter content is equal to a given state.**

Mod-16 Counter:
4-input logic gate
for decoding


Glitch and Strobed Decoding Gate

t_p = FF Propagation delay

 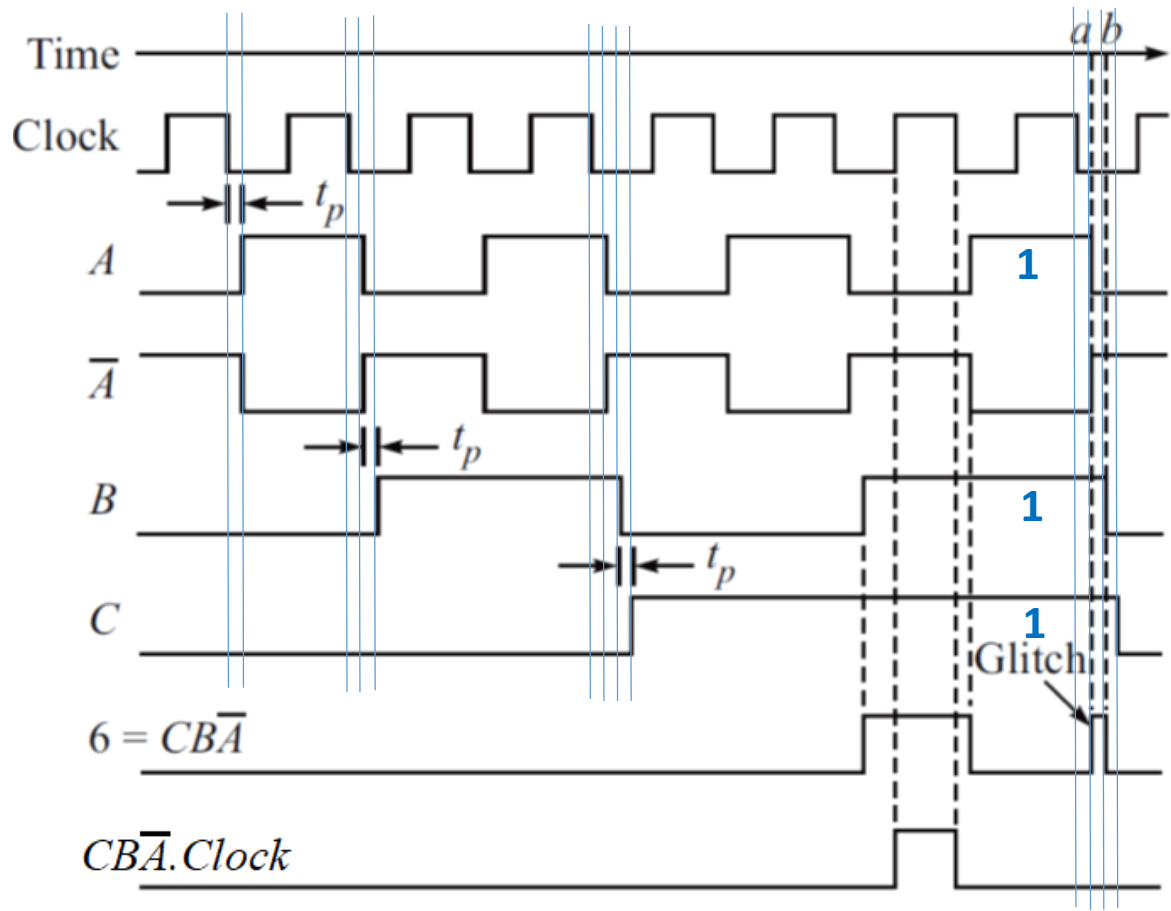Note that the basic gate delay for the decoding logic which is smaller than FF, is not shown in diagram .



 $111 \rightarrow 000$
 $111 \rightarrow (110) \rightarrow (100) \rightarrow 000$





Strobed gate

T_{Clock} usually much larger than t_p

Glitch between a and b



Glitch removed

Synchronous Up Counter

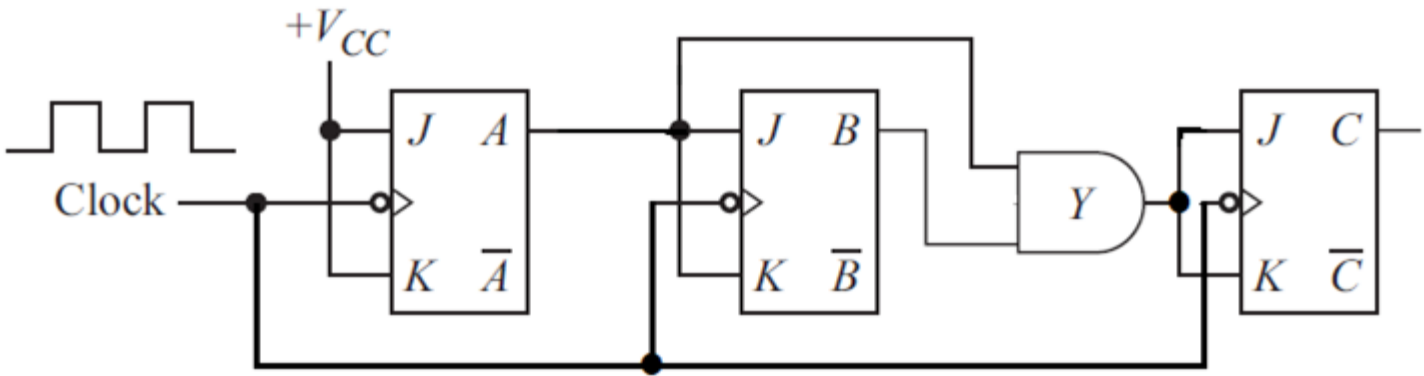 

C	B	A	Count
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7
0	0	0	0

Timing Diagram

 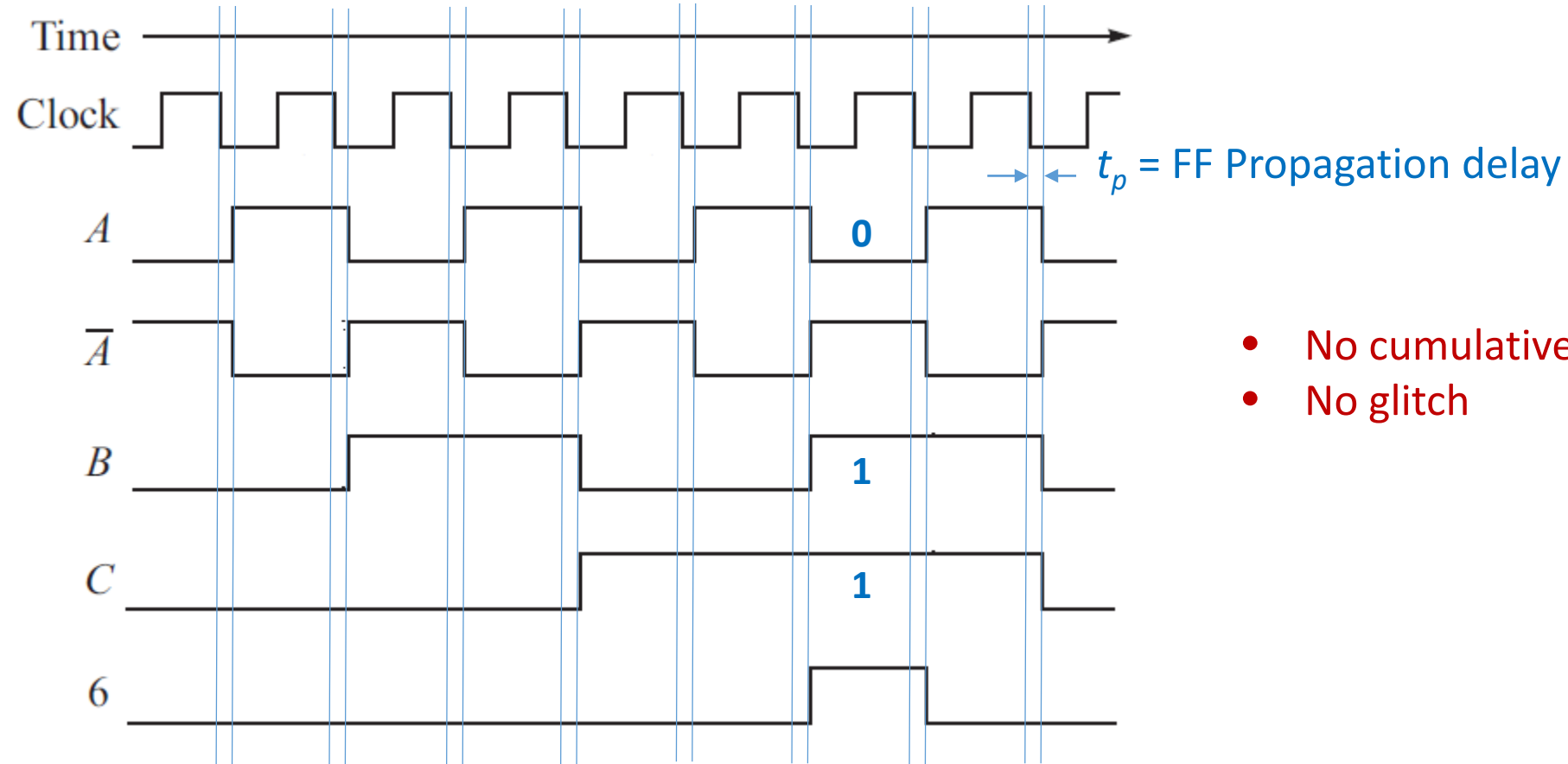


Decoding 6

- No cumulative delay
- No glitch


Synchronous Down Counter

C	B	A	Count
0	<u>0</u>	<u>0</u>	0
1	1	1	7
1	1	<u>0</u>	6
1	0	1	5
1	<u>0</u>	<u>0</u>	4
0	1	1	3
0	1	<u>0</u>	2
0	0	1	1
0	<u>0</u>	<u>0</u>	0
1	1	1	7

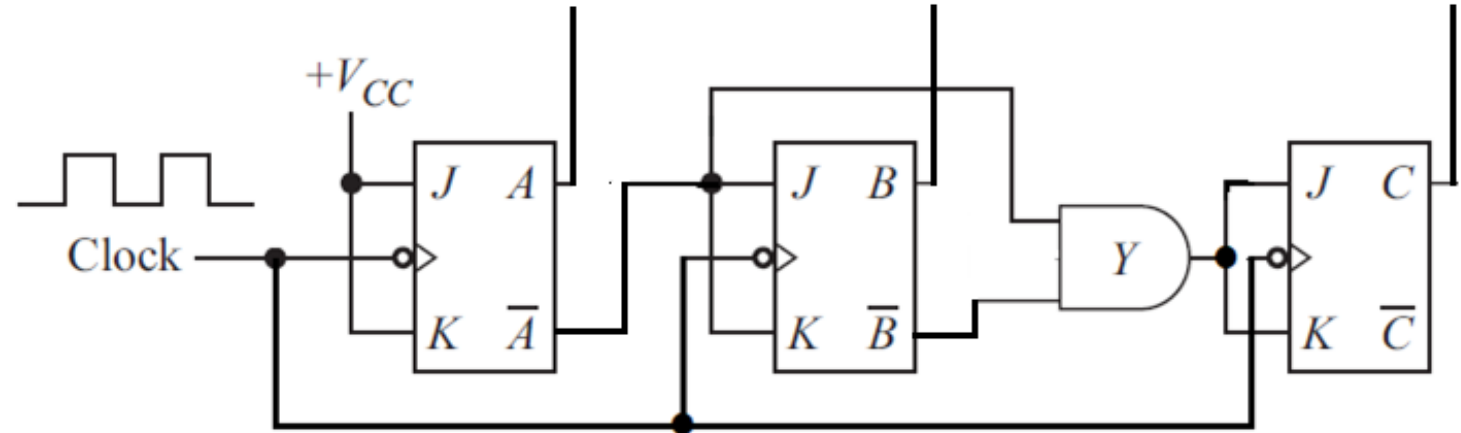


Synchronous Up-Down Counter

Count states: *DCBA*

 

Up Counter: Clock to 'Count up' while 'Count down' held at 0.

 Down Counter: Clock to 'Count down' while 'Count up' held at 0.



M is mode of counter

***M* = 0: Up**

***M* = 1: Down**

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ Texas Instrument's Digital Logic Pocket Data Book (2007)