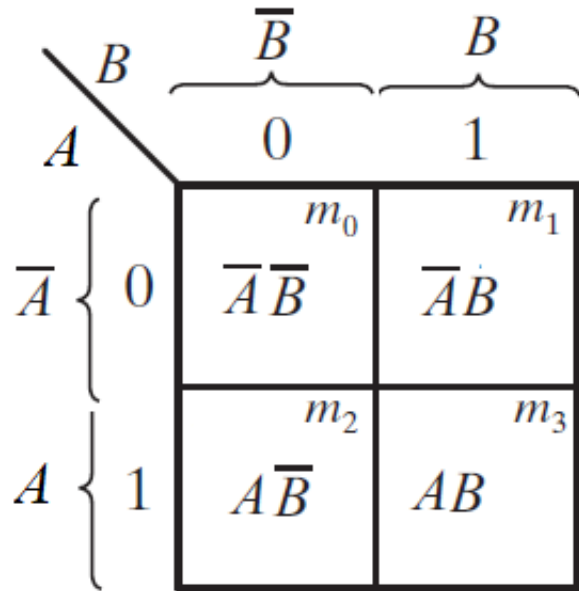


Digital Electronic Circuits

Section 1 (EE, IE)

Lecture 6

Two-Variable Karnaugh Map



$$Y = F(A,B) = \sum m(2,3)$$

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	1

	\bar{B}	B
\bar{A}	0	0
A	1	1

$$Y = A$$

$$Y = F(A,B) = \sum m(1,2,3)$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

	\bar{B}	B
\bar{A}	0	1
A	1	1

$$Y = A + B$$

SOP: Simplification

Three Variable Karnaugh Map

- Largest logically adjacent group of size 2^i
- Minimum no. of groups to cover all 1s
- Each group gives one product term
- Variables remaining constant form product term (1:unprimed, 0:primed)
- All product terms are summed.

		\bar{C}	C
		0	1
$\bar{A}\bar{B}$	00	0	1
$\bar{A}B$	01	2	3
AB	11	6	7
$A\bar{B}$	10	4	5

$F(A,B,C)$
minterm
numbers

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$Y = F(A,B,C)$$

$$= \sum m(2,4,5,6,7)$$

	\bar{C}	C	
$\bar{A}\bar{B}$	0	0	$B.C'$
$\bar{A}B$	1	0	
AB	1	1	A
$A\bar{B}$	1	1	

$$Y = A + B.C'$$

Four-Variable Karnaugh Map

		$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
		00	01	11	10
$\overline{A}\overline{B}$	00	0	1	3	2
$\overline{A}B$	01	4	5	7	6
AB	11	12	13	15	14
$A\overline{B}$	10	8	9	11	10

$F(A,B,C,D)$
minterm numbers

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$Y = F(A,B,C,D)$$

$$= \sum m(0,1,2,6,8,10,13,14)$$


$$= B'D' + CD' + A'B'C' + ABC'D$$

The Karnaugh map shows the following groupings:

- $B'D'$** : A red circle grouping the 1s at (0,0,0,0), (0,0,0,1), (1,0,0,0), and (1,0,0,1).
- CD'** : A blue circle grouping the 1s at (0,0,0,0), (0,0,1,0), (1,0,0,0), and (1,0,1,0).
- $A'B'C'$** : A yellow circle grouping the 1s at (0,0,0,0) and (0,0,0,1).
- $ABC'D$** : A green circle grouping the 1s at (1,0,0,0) and (1,0,0,1).

Don't Care in Karnaugh Map

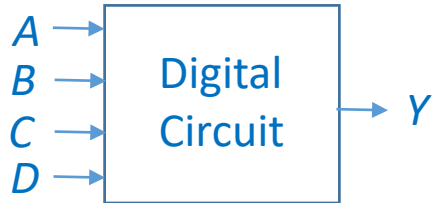Design: Y is H when BCD (Binary Coded Decimal) input is odd.



$$Y = F(A, B, C, D)$$

$$= \sum m(1, 3, 5, 7, 9) +$$

$$d(10, 11, 12, 13, 14, 15)$$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

Not considering X

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	1	1	0
$\overline{A}B$	0	1	1	0
AB	x	x	x	x
$A\overline{B}$	0	1	x	x

$$Y = A'D + B'C'D$$

- If not considered, X = 0.
- If considered, X = 1.
- Consideration wherever helps.

Considering X

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	1	1	0
$\overline{A}B$	0	1	1	0
AB	x	x	x	x
$A\overline{B}$	0	1	x	x

$$Y = D$$

Karnaugh Map: POS

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned}
 Y &= F(A,B,C) \\
 &= \sum m(2,4,5,6,7) \\
 &= \prod M(0,1,3)
 \end{aligned}$$

AB \ C		0	1
00	0	0	
01	1		0
11	1	1	
10	1	1	

$$Y = (A + B).(A + C')$$

Distributive

↓

$$Y = A + B.C' \quad \text{SOP Simplification}$$

$$\begin{aligned}
 Y &= F(A,B,C,D) \\
 &= \prod M(0,2,4,6,8).D(10, \\
 &\quad 11,12,13,14,15)
 \end{aligned}$$

CD	00	01	11	10
AB				
00	0	1	1	0
01	0	1	1	0
11	x	x	x	x
10	0	1	x	x


$$Y = D$$

- To cover all 0s
- Variables remaining constant form sum term (1:primed, 0:unprimed)
- Product of all sum terms generate output
- X is considered 0 wherever helps

Dual Circuit


	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	1	1	1
$\overline{A}B$	0	0	0	0
AB	1	1	1	1
$A\overline{B}$	0	0	1	1

Y



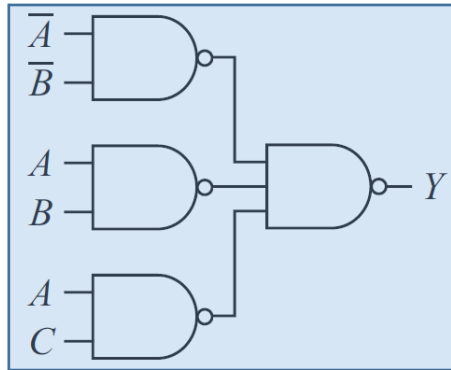


	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	0	0	0
$\overline{A}B$	1	1	1	1
AB	0	0	0	0
$A\overline{B}$	1	1	0	0

\overline{Y}

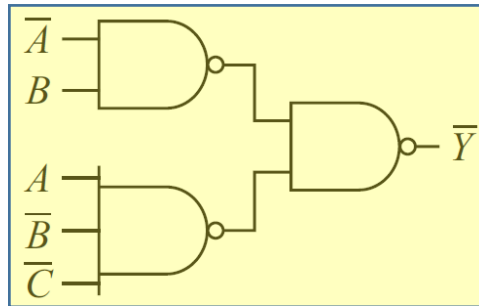
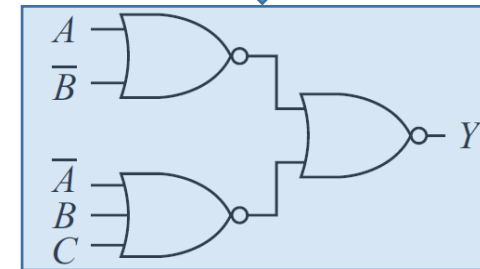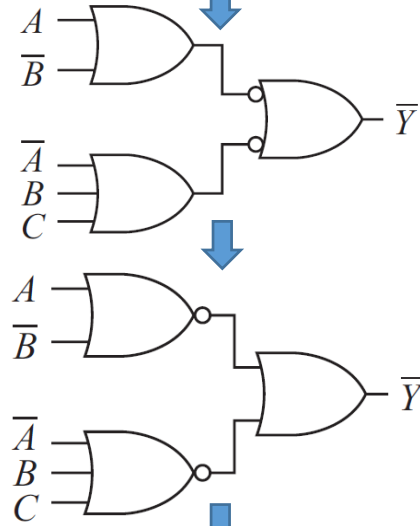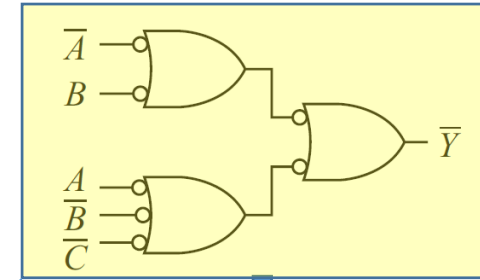
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



- **NAND \rightarrow NOR,**
NOR \rightarrow NAND,
Complement all
input and output
- **AND \rightarrow OR,**
OR \rightarrow AND,
Complement all
input and output

Self-Dual Function

Consider, $F(A,B) = A.B' + A'.B$

Its dual, $F_D(A,B) = (A+B').(A'+B)$

(on simplification) $= A'.B' + A.B$

$$F(A,B) \neq F_D(A,B)$$

Consider, $F(A,B,C) = A.B + B.C + C.A$

Then, $F_D(A,B,C) = (A+B).(B+C).(C+A)$

(on simplification) $= A.B + B.C + C.A$

$$F(A,B) = F_D(A,B) : \text{Self-dual}$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$A'.B$

$A.B'$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$A'.B.C$

$A.B'.C$

$A.B.C'$

$A.B.C$

Conditions:

- Neutral: No. of minterms is same as no. of Maxterms
- Function not to contain any mutually exclusive minterm

$A.B.C \longleftrightarrow A'.B'.C'$
mutually exclusive

References:

- ❑ Donald P. Leach, Albert P. Malvino, and Goutam Saha, Digital Principles & Applications 8e, McGraw Hill
- ❑ M. Morris Mano, and Michael D. Ciletti, Digital Design 5e, Pearson